

UNIT 2

CURRENT ELECTRICITY

We will make electricity so cheap that only the rich will burn candles
– Thomas A. Edison

LEARNING OBJECTIVES

In this unit, the student is exposed to

- Flow of charges in a metallic conductor
- Ohm's law, electrical resistance, V-I characteristics
- Carbon resistors and combination of resistors
- Kirchhoff's laws - Wheatstone's bridge and its applications
- Electric power and Electric energy
- Heating effect - Joule's law – Experimental verification and applications
- Thermoelectric effects – Seebeck effect – Peltier effect – Thomson effect



INTRODUCTION



In unit 1, we studied the properties of charges when it is at rest. In reality, the charges are always moving within the materials. For example, the electrons in a copper wire are never at rest and are continuously in random motion. Therefore it is important to analyse the behaviour of charges when it is at motion. The motion of charges is called 'electric current'. Current electricity is the study of flow of electric charges. It owes its origin to Alessandro Volta (1745-1827), who invented the electric battery which produced the first steady flow of electric current. Modern world depends heavily on the use of electricity. It is used to operate machines, communication systems, electronic devices, home appliances etc., In this unit, we will study about the electric current, resistance and related phenomenon in materials.

2.1

ELECTRIC CURRENT

Matter is made up of atoms. Each atom consists of a positively charged nucleus with negatively charged electrons moving around the nucleus. Atoms in metals have one or more electrons which are loosely bound to the nucleus. These electrons are called free electrons and can be easily detached from the atoms. The substances which have an abundance of these free electrons are called conductors. These free electrons move at random throughout the conductor at a given temperature. In general due to this random motion, there is no net transfer of

charges from one end of the conductor to other end and hence no current. When a potential difference is applied by the battery across the ends of the conductor, the free electrons drift towards the positive terminal of the battery, producing a net electric current. This is easily understandable from the analogy given in the Figure 2.1.

In the XI Volume 2, unit 6, we studied, that the mass move from higher gravitational potential to lower gravitational potential. Likewise, positive charge flows from higher electric potential to lower electric potential and negative charge flows from lower electric potential to higher electric potential. So battery or electric cell simply creates potential difference across the conductor.

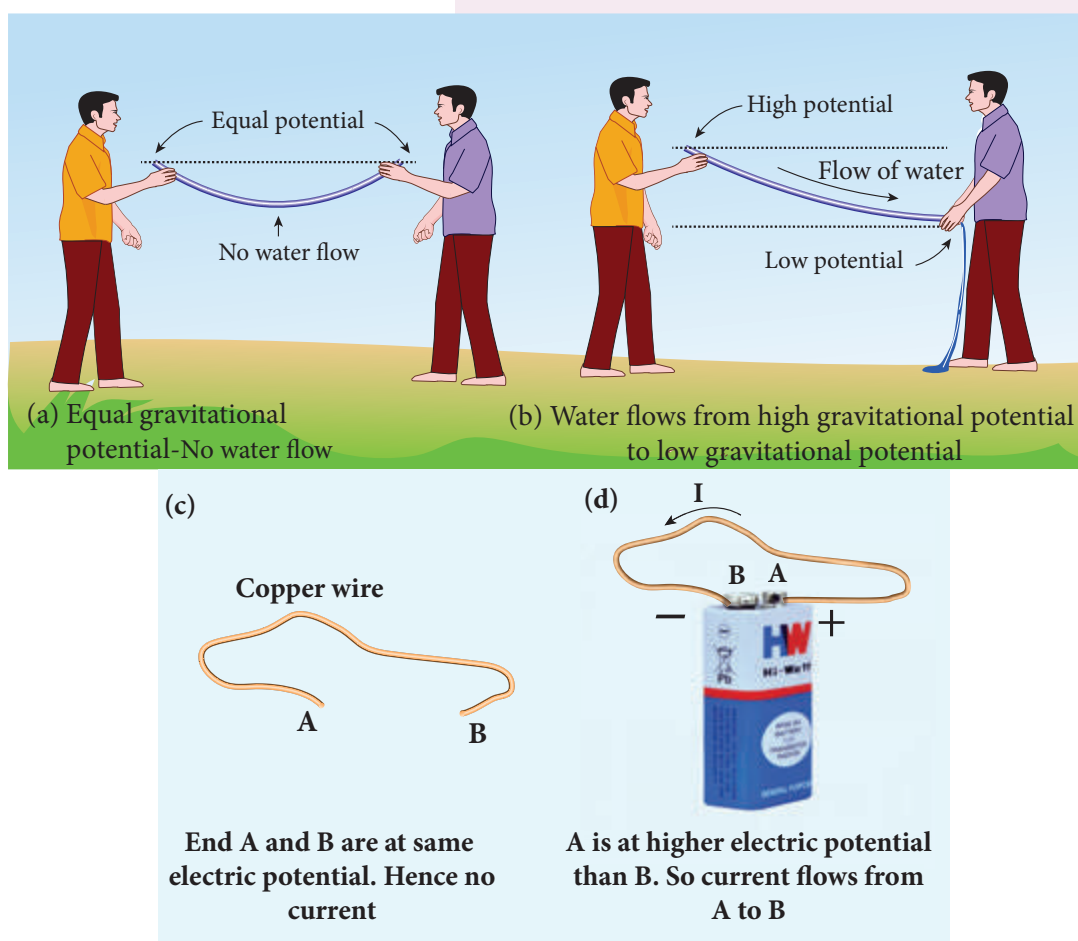


Figure 2.1 Water current and Electric current

The electric current in a conductor is defined as the rate of flow of charges through a given cross-sectional area A . It is shown in the Figure 2.2.

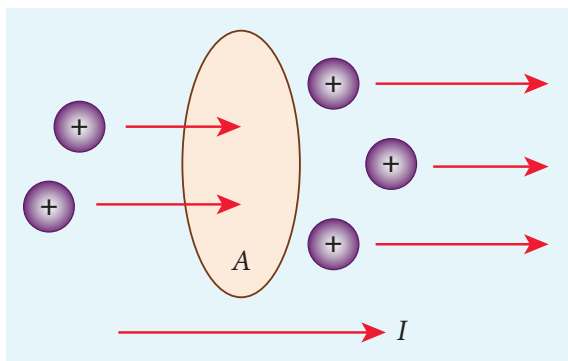


Figure 2.2 Charges flow across the area A

If a net charge Q passes through any cross section of a conductor in time t , then the current is defined as $I = \frac{Q}{t}$. But charge flow is not always constant. Hence current can more generally be defined as

$$I_{avg} = \frac{\Delta Q}{\Delta t} \quad (2.1)$$

Where ΔQ is the amount of charge that passes through the conductor at any cross section during the time interval Δt . If the rate at which charge flows changes in time, the current also changes. The instantaneous current I is defined as the limit of the average current, as $\Delta t \rightarrow 0$

$$I = \lim_{\Delta t \rightarrow 0} \frac{\Delta Q}{\Delta t} = \frac{dQ}{dt} \quad (2.2)$$

The SI unit of current is the **ampere** (A)

$$1A = \frac{1C}{1s}$$

That is, 1A of current is equivalent to 1 Coulomb of charge passing through a perpendicular cross section in 1second. The electric current is a scalar quantity.

EXAMPLE 2.1

Compute the current in the wire if a charge of 120 C is flowing through a copper wire in 1 minute.

Solution

The current (rate of flow of charge) in the wire is

$$I = \frac{Q}{t} = \frac{120}{60} = 2A$$

2.1.1 Conventional Current

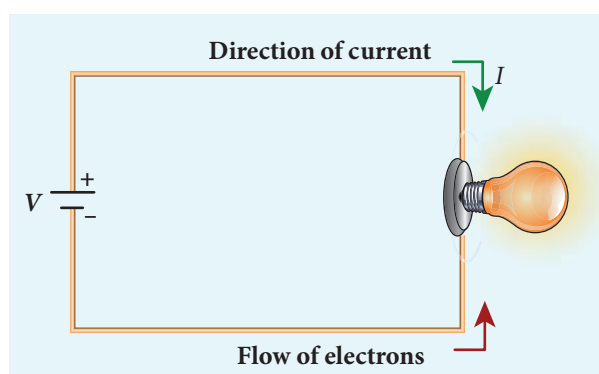


Figure 2.3 Direction of conventional current and electron flow

In an electric circuit, arrow heads are used to indicate the direction of flow of current. By convention, this flow in the circuit should be from the positive terminal of the battery to the negative terminal. This current is called the conventional current or simply current and is in the direction in which a positive test charge would move. In typical circuits the charges that flow are actually electrons, from the negative terminal of the battery to the positive. As a result, the flow of electrons and the direction of conventional current points in opposite direction as shown in Figure 2.3. Mathematically, a transfer of positive charge



is the same as a transfer of negative charge in the opposite direction.



Electric current is not only produced by batteries. In nature, lightning bolt produces enormous electric current in a short time. During lightning, very high potential difference is created between the clouds and ground so charges flow between the clouds and ground.

2.1.2 Drift velocity

In a conductor the charge carriers are free electrons. These electrons move freely through the conductor and collide repeatedly with the positive ions. If there is no electric field, the electrons move in random directions, so the directions of their velocities are also completely random direction. On an average, the number of electrons travelling in any direction will be equal to the number of electrons travelling in the opposite direction. As a result, there is no net flow of electrons in any direction and hence there will not be any current.

Suppose a potential difference is set across the conductor by connecting a battery, an electric field \vec{E} is created in the conductor. This electric field exerts a force on the electrons, producing a current. The

electric field accelerates the electrons, while ions scatter the electrons and change the direction of motion. Thus, we have zigzag paths of electrons. In addition to the zigzag motion due to the collisions, the electrons move slowly along the conductor in a direction opposite to that of \vec{E} as shown in the Figure 2.4.

Ions

Any material is made up of neutral atoms with equal number of electrons and protons. If the outermost electrons leave the atoms, they become free electrons and are responsible for electric current. The atoms after losing their outer most electrons will have more positive charges and hence are called positive ions. These ions will not move freely within the material like the free electrons. Hence the positive ions will not give rise to current.

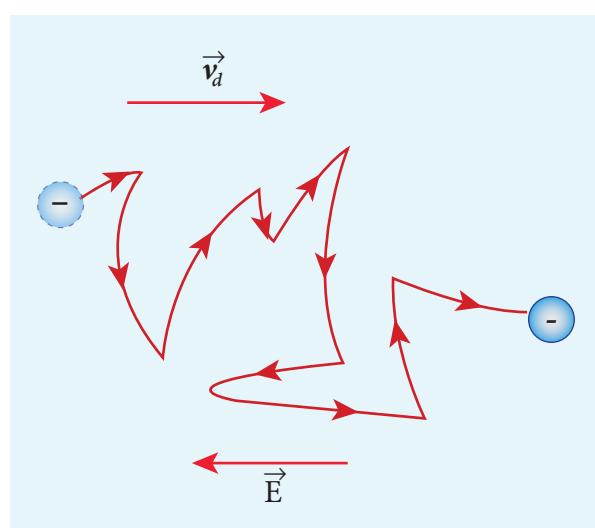


Figure 2.4 Electric current

This velocity is called drift velocity \vec{v}_d . The drift velocity is the average velocity acquired by the electrons inside the conductor when

it is subjected to an electric field. The average time between successive collisions is called the mean free time denoted by τ . The acceleration \vec{a} experienced by the electron in an electric field \vec{E} is given by

$$\vec{a} = \frac{-e\vec{E}}{m} \quad (\text{since } \vec{F} = -e\vec{E}) \quad (2.3)$$

The drift velocity \vec{v}_d is given by

$$\vec{v}_d = \vec{a} \tau$$

$$\vec{v}_d = -\frac{e\tau}{m} \vec{E} \quad (2.4)$$

$$\vec{v}_d = -\mu \vec{E} \quad (2.5)$$

Here $\mu = \frac{e\tau}{m}$ is the mobility of the electron and it is defined as the magnitude of the drift velocity per unit electric field.

$$\mu = \frac{|\vec{v}_d|}{|\vec{E}|} \quad (2.6)$$

The SI unit of mobility is $\frac{m^2}{V s}$.

Note

The typical drift velocity of electrons in the wire is 10^{-4} m s^{-1} . If an electron drifts with this speed, then the electrons leaving the battery will take hours to reach the light bulb. Then how electric bulbs glow as soon as we switch on the battery? When battery is switched on, the electrons begin to move away from the negative terminal of the battery and this electron exerts force on the nearby electrons. This process creates a propagating influence (electric field) that travels through the wire at the speed of light. In other words, the energy is transported from the battery to light bulb at the speed of light through propagating influence (electric field). Due to this reason, the light bulb glows as soon as the battery is switched on.

EXAMPLE 2.2

If an electric field of magnitude 570 N C^{-1} , is applied in the copper wire, find the acceleration experienced by the electron.

Solution:

$E = 570 \text{ N C}^{-1}$, $e = 1.6 \times 10^{-19} \text{ C}$,
 $m = 9.11 \times 10^{-31} \text{ kg}$ and $a = ?$

$$F = ma = eE$$

$$a = \frac{eE}{m} = \frac{570 \times 1.6 \times 10^{-19}}{9.11 \times 10^{-31}}$$

$$= \frac{912 \times 10^{-19} \times 10^{31}}{9.11}$$

$$= 1.001 \times 10^{14} \text{ m s}^{-2}$$

Misconception

- (i) There is a common misconception that the battery is the source of electrons. It is not true. When a battery is connected across the given wire, the electrons in the closed circuit resulting the current. Battery sets the potential difference (electrical energy) due to which these electrons in the conducting wire flow in a particular direction. The resulting electrical energy is used by electric bulb, electric fan etc. Similarly the electricity board is supplying the electrical energy to our home.
- (ii) We often use the phrases like 'charging the battery in my mobile' and 'my mobile phone battery has no charge' etc. These sentences are not correct.



When we say 'battery has no charge,' it means, that the battery has lost ability to provide energy or provide potential difference to the electrons in the circuit. When we say 'mobile is charging,' it implies that the battery is receiving energy from AC power supply and not electrons.

2.1.3 Microscopic model of current

Consider a conductor with area of cross section A and an electric field \vec{E} applied from right to left. Suppose there are n electrons per unit volume in the conductor and assume that all the electrons move with the same drift velocity \vec{v}_d as shown in Figure 2.5.

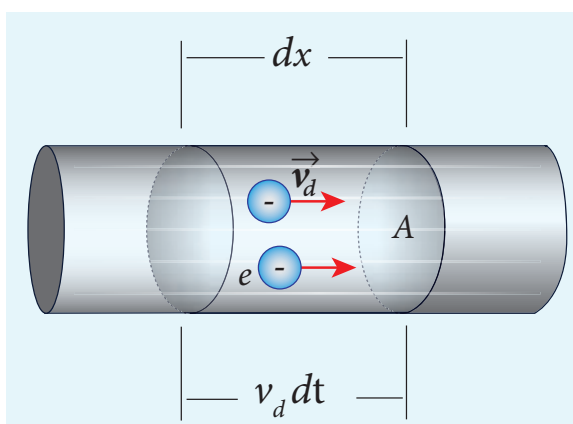


Figure 2.5 Microscopic model of current

The drift velocity of the electrons = v_d

The electrons move through a distance dx within a small interval of dt

$$v_d = \frac{dx}{dt}; \quad dx = v_d dt \quad (2.7)$$

Since A is the area of cross section of the conductor, the electrons available in the volume of length dx is

= volume \times number per unit volume

$$= A dx \times n \quad (2.8)$$

Substituting for dx from equation (2.7) in (2.8)

$$= (A v_d dt) n$$

Total charge in volume element $dQ =$ (charge) \times (number of electrons in the volume element)

$$dQ = (e)(A v_d dt) n$$

$$\text{Hence the current } I = \frac{dQ}{dt} = \frac{neAv_d dt}{dt}$$

$$I = neAv_d \quad (2.9)$$

Current density (J)

The current density (J) is defined as the current per unit area of cross section of the conductor.

$$J = \frac{I}{A}$$

The S.I unit of current density is $\frac{A}{m^2}$ (or) $A m^{-2}$

$$J = \frac{neAv_d}{A} \quad (\text{from equation 2.9})$$

$$J = nev_d \quad (2.10)$$

The above expression is valid only when the direction of the current is perpendicular to the area A . In general, the current density is a vector quantity and it is given by

$$\vec{J} = ne\vec{v}_d$$

Substituting \vec{v}_d from equation (2.4)

$$\vec{J} = -\frac{n \cdot e^2 \tau}{m} \vec{E} \quad (2.11)$$

$$\vec{J} = -\sigma \vec{E}$$

But conventionally, we take the direction of (conventional) current density as the direction of electric field. So the above equation becomes

$$\vec{J} = \sigma \vec{E} \quad (2.12)$$

where $\sigma = \frac{ne^2 \tau}{m}$ is called conductivity.

The equation 2.12 is called microscopic form of ohm's law.

The inverse of conductivity is called resistivity (ρ) [Refer section 2.2.1].

$$\rho = \frac{1}{\sigma} = \frac{m}{ne^2\tau} \quad (2.13)$$

EXAMPLE 2.3

A copper wire of cross-sectional area 0.5 mm^2 carries a current of 0.2 A . If the free electron density of copper is $8.4 \times 10^{28} \text{ m}^{-3}$ then compute the drift velocity of free electrons.

Solution

The relation between drift velocity of electrons and current in a wire of cross-sectional area A is

$$v_d = \frac{I}{neA} = \frac{0.2}{8.4 \times 10^{28} \times 1.6 \times 10^{-19} \times 0.5 \times 10^{-6}}$$

$$v_d = 0.03 \times 10^{-3} \text{ m s}^{-1}$$

Note

Why current density is a vector but current is a scalar?

In general, the current I is defined as the scalar product of the current density and area vector in which the charges cross.

$$I = \vec{j} \cdot \vec{A}$$

The current I can be positive or negative depending on the choice of the unit vector normal to the surface area A .

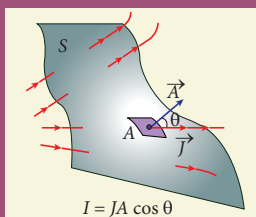


Figure 2.6 Current is a scalar

EXAMPLE 2.4

Determine the number of electrons flowing per second through a conductor, when a current of 32 A flows through it.

Solution

$$I = 32 \text{ A}, t = 1 \text{ s}$$

$$\text{Charge of an electron, } e = 1.6 \times 10^{-19} \text{ C}$$

The number of electrons flowing per second, $n = ?$

$$I = \frac{q}{t} = \frac{ne}{t}$$

$$n = \frac{It}{e}$$

$$n = \frac{32 \times 1}{1.6 \times 10^{-19} \text{ C}}$$

$$n = 20 \times 10^{19} = 2 \times 10^{20} \text{ electrons}$$

2.2

OHM'S LAW

The ohm's law can be derived from the equation $J = \sigma E$. Consider a segment of wire of length l and cross sectional area A as shown in Figure 2.7.

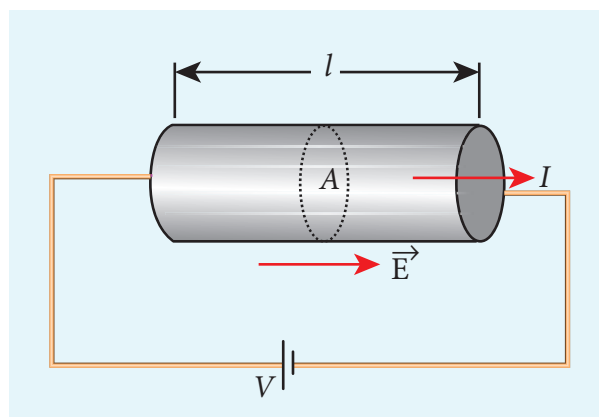


Figure 2.7 Current through the conductor

When a potential difference V is applied across the wire, a net electric field is created in the wire which constitutes the current. For simplicity, we assume that the electric field is uniform in the entire length of the wire, the potential difference (voltage V) can be written as

$$V = El$$

As we know, the magnitude of current density

$$J = \sigma E = \sigma \frac{V}{l} \quad (2.14)$$

But $J = \frac{I}{A}$, so we write the equation (2.14) as

$$\frac{I}{A} = \sigma \frac{V}{l}$$

By rearranging the above equation, we get

$$V = I \left(\frac{l}{\sigma A} \right) \quad (2.15)$$

The quantity $\frac{l}{\sigma A}$ is called resistance of the conductor and it is denoted as R . Note that the resistance is directly proportional to the length of the conductor and inversely proportional to area of cross section.

Therefore, the macroscopic form of ohm's law can be stated as

$$V = IR \quad (2.16)$$

From the above equation, **the resistance is the ratio of potential difference across the given conductor to the current passing through the conductor.**

$$R = \frac{V}{I} \quad (2.17)$$

The SI unit of resistance is ohm (Ω). From the equation (2.16), we infer that the graph between current versus voltage is straight line with a slope equal to the inverse

of resistance R of the conductor. It is shown in the Figure 2.8 (a).

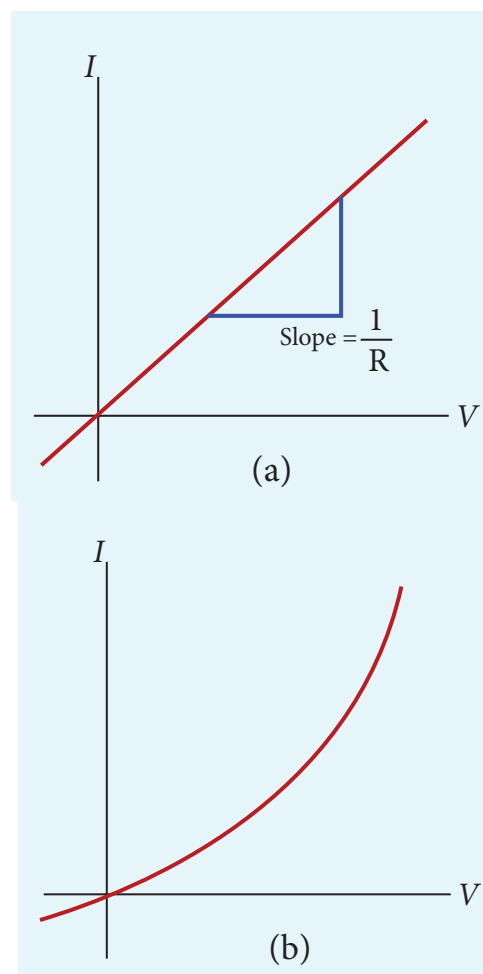



Figure 2.8 Current against voltage for (a) a conductor which obey Ohm's law and (b) for a non-ohmic device (Diode given in XII physics, unit 9 is an example of a non-ohmic device)

Materials for which the current against voltage graph is a straight line through the origin, are said to obey Ohm's law and their behaviour is said to be ohmic as shown in Figure 2.8(a). Materials or devices that do not follow Ohm's law are said to be non-ohmic. These materials have more complex relationships between voltage and current. A plot of I against V for a non-ohmic material is non-linear and they do not have a constant resistance (Figure 2.8(b)).

EXAMPLE 2.5

A potential difference across 24Ω resistor is 12 V . What is the current through the resistor?

Solution

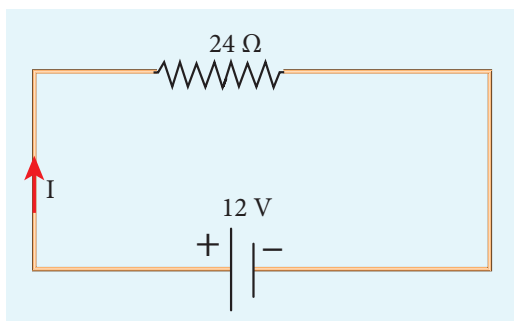

$$V = 12 \text{ V and } R = 24 \Omega$$

Current, $I = ?$

$$\text{From Ohm's law, } I = \frac{V}{R} = \frac{12}{24} = 0.5 \text{ A}$$

2.2.1 Resistivity

In the previous section, we have seen that the resistance R of any conductor is given by

$$R = \frac{l}{\sigma A} \quad (2.18)$$

where σ is called the conductivity of the material and it depends only on the type of the material used and not on its dimension.

The resistivity of a material is equal to the reciprocal of its conductivity.

$$\rho = \frac{1}{\sigma} \quad (2.19)$$

Now we can rewrite equation (2.18) using equation (2.19)

$$R = \rho \frac{l}{A} \quad (2.20)$$

The resistance of a material is directly proportional to the length of the conductor and inversely proportional to the area of cross section of the conductor. The

proportionality constant ρ is called the resistivity of the material.

If $l = 1 \text{ m}$ and $A = 1 \text{ m}^2$, then the resistance $R = \rho$. In other words, the **electrical resistivity of a material is defined as the resistance offered to current flow by a conductor of unit length having unit area of cross section**. The SI unit of ρ is ohm-metre ($\Omega \text{ m}$). Based on the resistivity, materials are classified as conductors, insulators and semiconductors. The conductors have lowest resistivity, insulators have highest resistivity and semiconductors have resistivity greater than conductors but less than insulators. The typical resistivity values of some conductors, insulators and semiconductors are given in the Table 2.1

Table 2.1 Resistivity for various materials

Material	Resistivity, ρ ($\Omega \text{ m}$) at 20°C
Insulators	
Pure Water	2.5×10^5
Glass	$10^{10} - 10^{14}$
Hard Rubber	$10^{13} - 10^{16}$
NaCl	$- 10^{14}$
Fused Quartz	$- 10^{16}$
Semiconductors	
Germanium	0.46
Silicon	640
Conductors	
Silver	1.6×10^{-8}
Copper	17×10^{-8}
Aluminium	2.7×10^{-8}
Tungsten	5.6×10^{-8}
Iron	10×10^{-8}

EXAMPLE 2.6

The resistance of a wire is 20Ω . What will be new resistance, if it is stretched uniformly 8 times its original length?

Solution

$$R_1 = 20 \Omega, R_2 = ?$$

Let the original length (l_1) be l .

The new length, $l_2 = 8l_1$ (i.e.) $l_2 = 8l$

The original resistance, $R_1 = \rho \frac{l_1}{A_1}$

The new resistance $R_2 = \rho \frac{l_2}{A_2} = \frac{\rho(8l)}{A_2}$

Though the wire is stretched, its volume is unchanged.

Initial volume = Final volume

$$A_1 l_1 = A_2 l_2, \quad A_1 l = A_2 8l$$

$$\frac{A_1}{A_2} = \frac{8l}{l} = 8$$

By dividing equation R_2 by equation R_1 , we get

$$\frac{R_2}{R_1} = \frac{\rho(8l)}{A_2} \times \frac{A_1}{\rho l}$$

$$\frac{R_2}{R_1} = \frac{A_1}{A_2} \times 8$$

Substituting the value of $\frac{A_1}{A_2}$, we get


$$\frac{R_2}{R_1} = 8 \times 8 = 64$$

$$R_2 = 64 \times 20 = 1280 \Omega$$

Hence, stretching the length of the wire has increased its resistance.

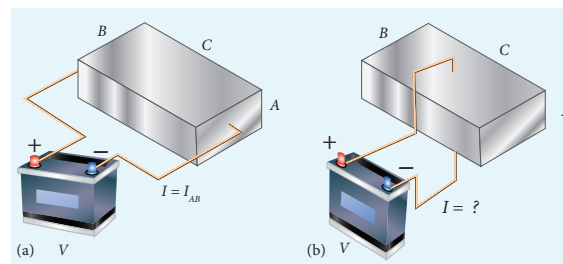EXAMPLE 2.7

Consider a rectangular block of metal of height A , width B and length C as shown in the figure.



If a potential difference of V is applied between the two faces A and B of the block (figure (a)), the current I_{AB} is observed. Find the current that flows if the same potential difference V is applied between the two faces B and C of the block (figure (b)). Give your answers in terms of I_{AB} .

Solution

In the first case, the resistance of the block

$$R_{AB} = \rho \frac{\text{length}}{\text{Area}} = \rho \frac{C}{AB}$$

$$\text{The current } I_{AB} = \frac{V}{R_{AB}} = \frac{V}{\rho} \cdot \frac{AB}{C} \quad (1)$$

In the second case, the resistance of the block $R_{BC} = \rho \frac{A}{BC}$

$$\text{The current } I_{BC} = \frac{V}{R_{BC}} = \frac{V}{\rho} \cdot \frac{BC}{A} \quad (2)$$

To express I_{BC} in terms of I_{AB} , we multiply and divide equation (2) by AC , we get

$$I_{BC} = \frac{V}{\rho} \cdot \frac{BC}{A} \cdot \frac{AC}{AC} = \left(\frac{V}{\rho} \cdot \frac{AB}{C} \right) \cdot \frac{C^2}{A^2} = \frac{C^2}{A^2} \cdot I_{AB}$$

Since $C > A$, the current $I_{BC} > I_{AB}$



The human body contains a large amount of water which has low resistance of around 200Ω and the dry skin has high resistance of around $500 \text{ k}\Omega$. But when the skin is wet, the resistance is reduced to around 1000Ω . This is the reason, repairing the electrical connection with the wet skin is always dangerous.

2.2.2 Resistors in series and parallel

An electric circuit may contain a number of resistors which can be connected in different ways. For each type of circuit, we can calculate the equivalent resistance produced by a group of individual resistors.

Resistors in series

When two or more resistors are connected end to end, they are said to be in series. The resistors could be simple resistors or bulbs or heating elements or other devices. Figure 2.9 (a) shows three resistors R_1 , R_2 and R_3 connected in series.

The amount of charge passing through resistor R_1 must also pass through resistors R_2

and R_3 since the charges cannot accumulate anywhere in the circuit. Due to this reason, the current I passing through all the three resistors is the same. According to Ohm's law, if same current pass through different resistors of different values, then the potential difference across each resistor must be different. Let V_1 , V_2 and V_3 be the potential difference (voltage) across each of the resistors R_1 , R_2 and R_3 respectively, then we can write $V_1 = IR_1$, $V_2 = IR_2$ and $V_3 = IR_3$. But the total voltage V is equal to the sum of voltages across each resistor.

$$V = V_1 + V_2 + V_3 = IR_1 + IR_2 + IR_3 \quad (2.21)$$

$$V = I(R_1 + R_2 + R_3)$$

$$V = I.R_s \quad (2.22)$$

where R_s is the equivalent resistance,

$$R_s = R_1 + R_2 + R_3 \quad (2.23)$$

When several resistances are connected in series, the total or equivalent resistance is the sum of the individual resistances as shown in the Figure 2.9 (b).

Note: The value of equivalent resistance in series connection will be greater than each individual resistance.

EXAMPLE 2.8

Calculate the equivalent resistance for the circuit which is connected to 24 V battery and also find the potential difference across 4 Ω and 6 Ω resistors in the circuit.


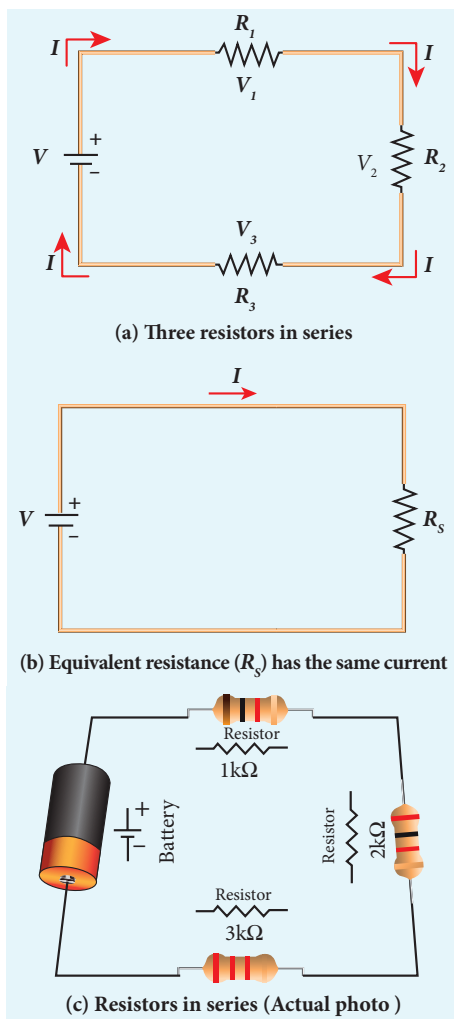


Figure 2.9 Resistors in series

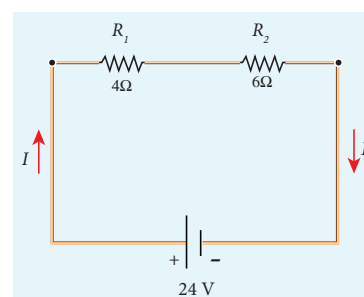

Solution

Since the resistors are connected in series, the effective resistance in the circuit

$$= 4 \Omega + 6 \Omega = 10 \Omega$$

$$\text{The Current } I \text{ in the circuit} = \frac{V}{R_{eq}} = \frac{24}{10} = 2.4 \text{ A}$$

Voltage across 4Ω resistor

$$V_1 = IR_1 = 2.4 \text{ A} \times 4 \Omega = 9.6 \text{ V}$$

Voltage across 6Ω resistor

$$V_2 = IR_1 = 2.4 \text{ A} \times 6 \Omega = 14.4 \text{ V}$$

Resistors in parallel

Resistors are in parallel when they are connected across the same potential difference as shown in Figure 2.10 (a).

In this case, the total current I that leaves the battery is split into three separate paths. Let I_1 , I_2 and I_3 be the current through the resistors R_1 , R_2 and R_3 respectively. Due to the conservation of charge, total current in the circuit I is equal to sum of the currents through each of the three resistors.

$$I = I_1 + I_2 + I_3 \quad (2.24)$$

Since the voltage across each resistor is the same, applying Ohm's law to each resistor, we have

$$I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}, I_3 = \frac{V}{R_3} \quad (2.25)$$

Substituting these values in equation (2.24), we get

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$I = \frac{V}{R_p}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad (2.26)$$

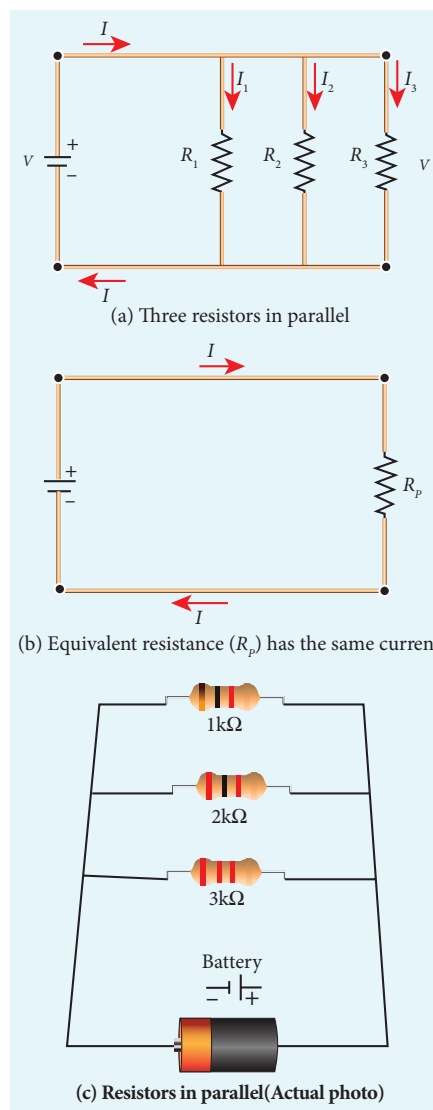


Figure 2.10 Resistors in parallel


Here R_p is the equivalent resistance of the parallel combination of the resistors. Thus, when a number of resistors are connected in parallel, the sum of the reciprocal of the values of resistance of the individual resistor is equal to the reciprocal of the effective resistance of the combination as shown in the Figure 2.10 (b)

Note: The value of equivalent resistance in parallel connection will be lesser than each individual resistance.

House hold appliances are always connected in parallel so that even if one is switched off, the other devices could function properly.

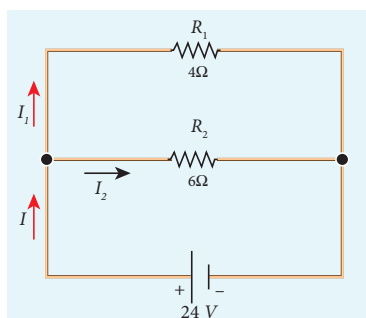EXAMPLE 2.9

Calculate the equivalent resistance in the following circuit and also find the current I , I_1 and I_2 in the given circuit.



Solution

Since the resistances are connected in parallel, therefore, the equivalent resistance in the circuit is

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{4} + \frac{1}{6}$$
$$\frac{1}{R_p} = \frac{5}{12} \Omega \quad \text{or } R_p = \frac{12}{5} \Omega$$

The resistors are connected in parallel, the potential (voltage) across each resistor is the same.

$$I_1 = \frac{V}{R_1} = \frac{24V}{6\Omega} = 4A$$
$$I_2 = \frac{V}{R_2} = \frac{24}{6} = 4A$$

The current I is the total of the currents in the two branches. Then,

$$I = I_1 + I_2 = 6A + 4A = 10A$$

EXAMPLE 2.10

When two resistances connected in series and parallel their equivalent resistances are 15Ω and $\frac{56}{15} \Omega$ respectively. Find the individual resistances.

Solution

$$R_s = R_1 + R_2 = 15 \Omega \quad (1)$$

$$R_p = \frac{R_1 R_2}{R_1 + R_2} = \frac{56}{15} \Omega \quad (2)$$

From equation (1) substituting for $R_1 + R_2$ in equation (2)

$$\frac{R_1 R_2}{15} = \frac{56}{15} \Omega$$

$$\therefore R_1 R_2 = 56$$

$$R_2 = \frac{56}{R_1} \Omega \quad (3)$$

Substituting for R_2 in equation (1) from equation (3)

$$R_1 + \frac{56}{R_1} = 15$$

$$\text{Then, } \frac{R_1^2 + 56}{R_1} = 15$$

$$R_1^2 + 56 = 15 R_1$$

$$R_1^2 - 15 R_1 + 56 = 0$$

The above equation can be solved using factorisation.

$$R_1^2 - 8 R_1 - 7 R_1 + 56 = 0$$

$$R_1 (R_1 - 8) - 7 (R_1 - 8) = 0$$

$$(R_1 - 8) (R_1 - 7) = 0$$

$$\text{If } (R_1 = 8 \Omega)$$

using in equation (1)

$$8 + R_2 = 15$$

$$R_2 = 15 - 8 = 7 \Omega,$$

$$R_2 = 7 \Omega \text{ i.e., (when } R_1 = 8 \Omega; R_2 = 7 \Omega)$$

$$\text{If } (R_1 = 7 \Omega)$$


Substituting in equation (1)

$$7 + R_2 = 15$$

$$R_2 = 8 \Omega, \text{ i.e., (when } R_1 = 8 \Omega; R_2 = 7 \Omega)$$

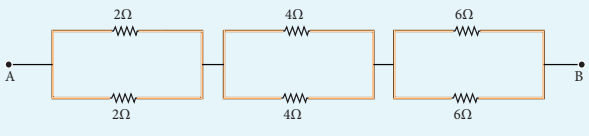EXAMPLE 2.11

Calculate the equivalent resistance between A and B in the given circuit.




Solution

Parallel connection

Part I


$$\frac{1}{R_{p_1}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{p_1}} = \frac{1}{2} + \frac{1}{2} = \frac{2}{2} \quad R_{p_1} = 1\Omega$$

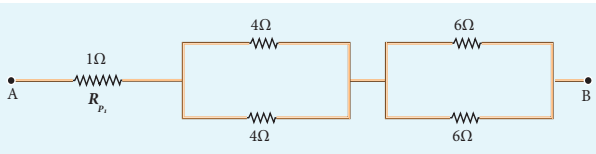

Part II

$$\frac{1}{R_{p_2}} = \frac{1}{4} + \frac{1}{4} = \frac{2}{4}, \quad \frac{1}{R_{p_2}} = \frac{1}{2}, \quad R_{p_2} = 2\Omega$$

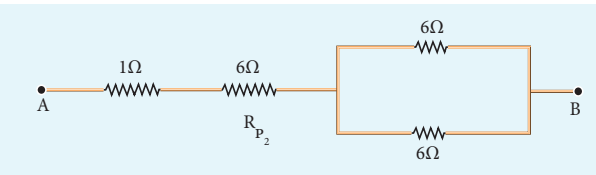

Part III


$$\frac{1}{R_{p_3}} = \frac{1}{6} + \frac{1}{6} = \frac{2}{6}$$

$$\frac{1}{R_{p_3}} = \frac{1}{3}, \quad R_{p_3} = 3\Omega$$


$$R = R_{p_1} + R_{p_2} + R_{p_3}$$

$$R = 1 + 2 + 3 \quad R = 6\Omega$$

The circuit became:

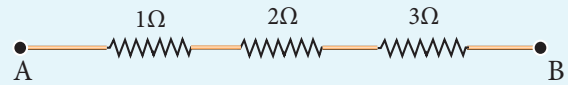


Equivalent resistance between A and B is

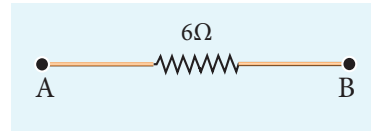

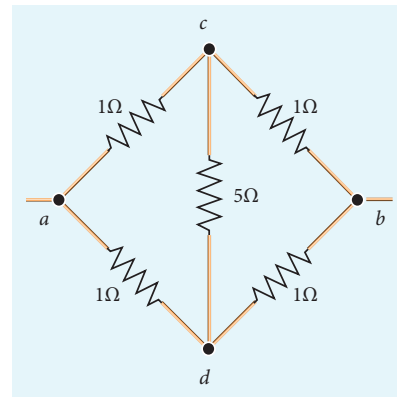EXAMPLE 2.12


Five resistors are connected in the configuration as shown in the figure. Calculate the equivalent resistance between the points a and b.



Solution

Case (a)

To find the equivalent resistance between the points a and b, we assume that current is entering the junction a. Since all the resistances in the outside loop are the same (1Ω), the current in the branches ac and ad must be equal. So the electric potential at the point c and d is the same hence no current flows into 5Ω resistance. It implies that the 5Ω has no role in determining the equivalent resistance and it can be removed. So the circuit is simplified as shown in the figure.

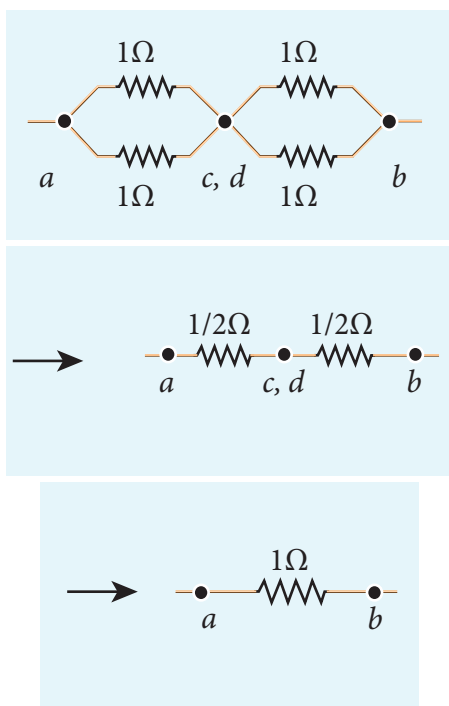

The equivalent resistance of the circuit between a and b is $R_{eq} = 1\Omega$

2.2.3 Color code for Carbon resistors



Figure 2.11 Resistance used in our laboratory

Carbon resistors consists of a ceramic core, on which a thin layer of crystalline carbon is deposited as shown in Figure 2.11. These resistors are inexpensive, stable and compact in size. Color rings are used to indicate the value of the resistance according to the rules given in the Table 2.2.

Three coloured rings are used to indicate the values of a resistor: the first two rings are significant figures of resistances, the third ring indicates the decimal multiplier after them. The fourth color, silver or gold,

Table 2.2 Color Coding for Resistors

Color	Number	Multiplier	Tolerance
Black	0	1	
Brown	1	10^1	
Red	2	10^2	
Orange	3	10^3	
Yellow	4	10^4	
Green	5	10^5	
Blue	6	10^6	
Violet	7	10^7	
Gray	8	10^8	
White	9	10^9	
Gold		10^{-1}	5%
Sliver		10^{-2}	10%
Colorless			20%

shows the tolerance of the resistor at 10% or 5% as shown in the Figure 2.12. If there is no fourth ring, the tolerance is 20%.

For the resistor shown in Figure 2.12, the first digit = 5 (green), the second digit = 6 (blue), decimal multiplier = 10^3 (orange) and tolerance = 5% (gold). The value of resistance = $56 \times 10^3 \Omega$ or 56 k Ω with the tolerance value 5%.

Note While reading the colour code, hold the resistor with colour bands to your left. Resistors never start with a metallic band on the left.

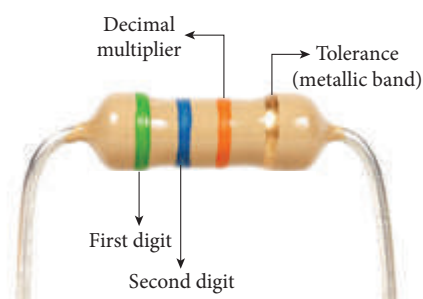


Figure 2.12 Resistor color coding



Measuring current



Measuring resistance



Measuring voltage

A multimeter is a very useful electronic instrument used to measure voltage, current, resistance and capacitance. In fact, it can also measure AC voltage and AC current. The circular slider has to be kept in appropriate position to measure each electrical quantity.

2.2.4 Temperature dependence of resistivity

The resistivity of a material is dependent on temperature. It is experimentally found that for a wide range of temperatures, the resistivity of a conductor increases with

increase in temperature according to the expression,

$$\rho_T = \rho_o [1 + \alpha(T - T_o)] \quad (2.27)$$

where ρ_T is the resistivity of a conductor at $T^\circ\text{C}$, ρ_o is the resistivity of the conductor at some reference temperature T_o (usually at 20°C) and α is the temperature coefficient of resistivity. **It is defined as the ratio of increase in resistivity per degree rise in temperature to its resistivity at T_o .**

From the equation (2.27), we can write

$$\begin{aligned} \rho_T - \rho_o &= \alpha \rho_o (T - T_o) \\ \therefore \alpha &= \frac{\rho_T - \rho_o}{\rho_o (T - T_o)} = \frac{\Delta \rho}{\rho_o \Delta T} \end{aligned}$$

where $\Delta \rho = \rho_T - \rho_o$ is change in resistivity for a change in temperature $\Delta T = T - T_o$. Its unit is per $^\circ\text{C}$.

α of conductors

For conductors α is positive. If the temperature of a conductor increases, the average kinetic energy of electrons in the conductor increases. This results in more frequent collisions and hence the resistivity increases. The graph of the equation (2.27) is shown in Figure 2.13

Even though, the resistivity of conductors like metals varies linearly for wide range of temperatures, there also exists a non-linear region at very low temperatures. The resistivity approaches some finite value as the temperature approaches absolute zero as shown in Figure 2.13(b).

As the resistance is directly proportional to resistivity of the material, we can also write the resistance of a conductor at temperature $T^\circ\text{C}$ as

$$R_T = R_o [1 + \alpha(T - T_o)] \quad (2.28)$$

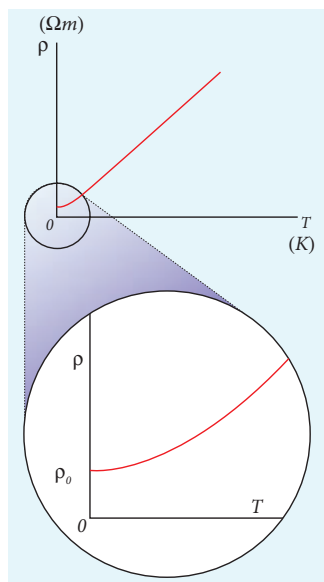


Figure 2.13 (a) Temperature dependence of resistivity for a conductor
(b) Non linear region at low temperature

The temperature coefficient can be also be obtained from the equation (2.28),

$$R_T - R_0 = \alpha R_0 (T - T_0)$$

$$\therefore \alpha = \frac{R_T - R_0}{R_0 (T - T_0)} = \frac{1}{R_0} \frac{\Delta R}{\Delta T}$$

$$\alpha = \frac{1}{R_0} \frac{\Delta R}{\Delta T} \quad (2.29)$$

where $\Delta R = R_T - R_0$ is change in resistance during the change in temperature $\Delta T = T - T_0$.

α of semiconductors

For semiconductors, the resistivity decreases with increase in temperature. As the temperature increases, more electrons will be liberated from their atoms (Refer unit 9 for conduction in semi conductors). Hence the current increases and therefore the resistivity decreases as shown in Figure 2.14. A semiconductor with a negative temperature coefficient of resistance is called a thermistor.

The typical values of temperature coefficients of various materials are given in table 2.3.

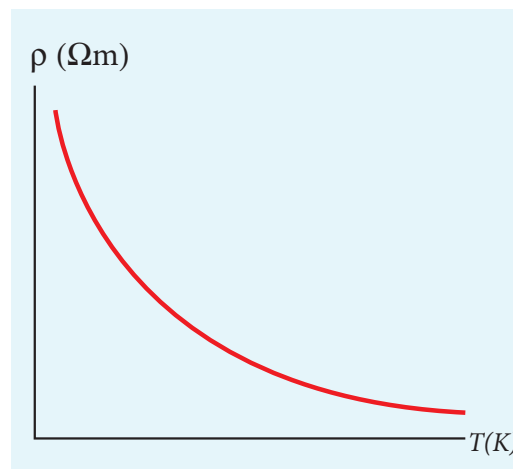


Figure 2.14 Temperature dependence of resistivity for a semiconductor

Table 2.3

Color	Temperature Coefficient α [$^{\circ}\text{C}^{-1}$]
Silver	3.8×10^{-3}
Copper	3.9×10^{-3}
Gold	3.4×10^{-3}
Aluminum	3.9×10^{-3}
Tungsten	4.5×10^{-3}
Iron	5.0×10^{-3}
Platinum	3.92×10^{-3}
Lead	3.9×10^{-3}
Nichrome	0.4×10^{-3}
Carbon	-0.5×10^{-3}
Germanium	-48×10^{-3}
Silicon	-75×10^{-3}

We can understand the temperature dependence of resistivity in the following way. In section 2.1.3, we have shown that the electrical conductivity, $\sigma = \frac{ne^2\tau}{m}$. As the resistivity is inverse of σ , it can be written as,

$$\rho = \frac{m}{ne^2\tau} \quad (2.30)$$

The resistivity of materials is

- i) inversely proportional to the number density (n) of the electrons
- ii) inversely proportional to the average time between the collisions (τ).

In metals, if the temperature increases, the average time between the collision (τ) decreases and n is independent of temperature. In semiconductors when temperature increases, n increases and τ decreases, but increase in n is dominant than decreasing τ , so that overall resistivity decreases.



The resistance of certain materials become zero below certain temperature T_c . This temperature is known as critical temperature or transition temperature. The materials which exhibit this property are known as superconductors. This phenomenon was first observed by Kammerlingh Onnes in 1911. He found that mercury exhibits superconductor behaviour at 4.2 K. Since $R = 0$, current once induced in a superconductor persists without any potential difference.

EXAMPLE 2.13

If the resistance of coil is 3Ω at 20°C and $\alpha = 0.004/^\circ\text{C}$ then determine its resistance at 100°C .

Solution

$$R_0 = 3 \Omega, \quad T = 100^\circ\text{C}, \quad T_0 = 20^\circ\text{C}$$

$$\alpha = 0.004/^\circ\text{C}, \quad R_T = ?$$

$$R_T = R_0(1 + \alpha(T - T_0))$$

$$R_{100} = 3(1 + 0.004 \times 80)$$

$$R_{100} = 3(1 + 0.32)$$

$$R_{100} = 3(1.32)$$

$$R_{100} = 3.96 \Omega$$

EXAMPLE 2.14

Resistance of a material at 10°C and 40°C are 45Ω and 85Ω respectively. Find its temperature co-efficient of resistance.

Solution

$$T_0 = 10^\circ\text{C}, \quad T = 40^\circ\text{C}, \quad R_0 = 45 \Omega, \quad R = 85 \Omega$$

$$\alpha = \frac{1}{R_0} \frac{\Delta R}{\Delta T}$$

$$\alpha = \frac{1}{45} \left(\frac{85 - 45}{40 - 10} \right) = \frac{1}{45} \left(\frac{40}{30} \right)$$

$$\alpha = 0.0296 \text{ per } ^\circ\text{C}$$

2.3

ENERGY AND POWER IN ELECTRICAL CIRCUITS

When a battery is connected between the ends of a conductor, a current is established. The battery is transporting energy to the device which is connected in the circuit. Consider a circuit in which a battery of voltage V is connected to the resistor as shown in Figure 2.15.

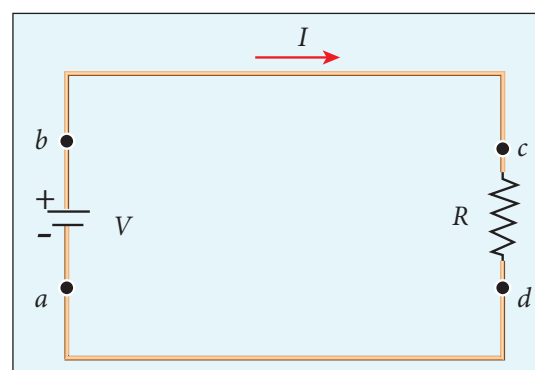


Figure 2.15 Energy given by the battery

Assume that a positive charge of dQ moves from point a to b through the battery and moves from point c to d through the resistor and back to point a . When the charge

moves from point a to b , it gains potential energy $dU = V.dQ$ and the chemical potential energy of the battery decreases by the same amount. When this charge dQ passes through resistor it loses the potential energy $dU = V.dQ$ due to collision with atoms in the resistor and again reaches the point a . This process occurs continuously till the battery is connected in the circuit. The rate at which the charge loses its electrical potential energy in the resistor can be calculated.

The electrical power P is the rate at which the electrical potential energy is delivered,

$$P = \frac{dV}{dt} = \frac{d}{dt}(V.dQ) = V \frac{dQ}{dt} \quad (2.31)$$

Since the electric current $I = \frac{dQ}{dt}$.

So the equation (2.31) can be rewritten as

$$P = VI \quad (2.32)$$

This expression gives the power delivered by the battery to any electrical system, where I is the current passing through it and V is the potential difference across it. The SI unit of electrical power is watt ($1W = 1 Js^{-1}$). Commercially, the electrical bulbs used in houses come with the power and voltage rating of 5W-220V, 30W-220V, 60W-220V etc. (Figure 2.16).



Figure 2.16 Electrical bulbs with power rating

Usually these voltage rating refers AC RMS voltages. For a given bulb, if the voltage drop across the bulb is greater than voltage rating, the bulb will fuse.

Using Ohm's law, power delivered to the resistance R is expressed in other forms

$$P = IV = I(IR) = I^2R \quad (2.33)$$

$$P = IV = \frac{V}{R}V = \frac{V^2}{R} \quad (2.34)$$



The electrical power produced (dissipated) by a resistor is I^2R . It depends on the square of the current. Hence, if current is doubled, the power will increase by four times. Similar explanation holds true for voltage also.

The total energy used by any device is obtained by multiplying the power and duration of the time when it is ON. If the power is in watts and the time is in seconds, the energy will be in joules. In practice, electrical energy is measured in kilowatt hour (kWh). $1 kWh$ is known as 1 unit of electrical energy.


$$(1 kWh = 1000 Wh = (1000 W) (3600 s) = 3.6 \times 10^6 J)$$



The Tamilnadu Electricity Board is charging for the amount of energy you use and not for the power. A current of 1A flowing through a potential difference of 1V produces a power of 1W.

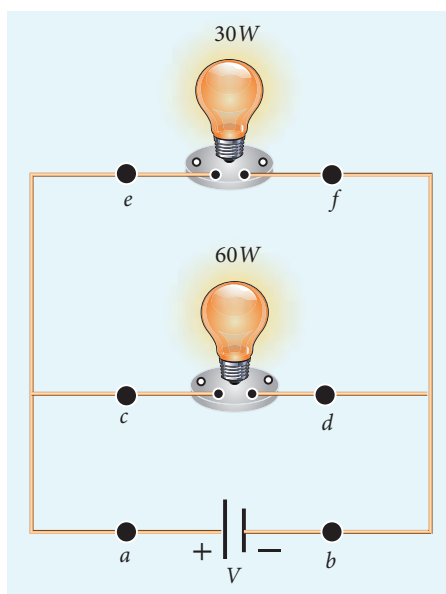EXAMPLE 2.15

A battery of voltage V is connected to 30 W bulb and 60 W bulb as shown in the figure. (a) Identify brightest bulb (b) which bulb has greater resistance? (c) Suppose the two bulbs are connected in series, which bulb will glow brighter?



Solution

- (a) The power delivered by the battery $P = VI$. Since the bulbs are connected in parallel, the voltage drop across each bulb is the same. If the voltage is kept fixed, then the power is directly proportional to current ($P \propto I$). So 60 W bulb draws twice as much as current as 30 W and it will glow brighter than others.
- (b) To calculate the resistance of the bulbs, we use the relation $P = \frac{V^2}{R}$. In both the bulbs, the voltage drop is the same, so the power is inversely proportional to the resistance or resistance is inversely proportional to the power $\left(R \propto \frac{1}{P}\right)$. It implies

that, the 30W has twice as much as resistance as 60 W bulb.

- (c) When these two bulbs are connected in series, the current passing through each bulb is the same. It is equivalent to two resistors connected in series. The bulb which has higher resistance has higher voltage drop. So 30W bulb will glow brighter than 60W bulb. So the higher power rating does not always imply more brightness and it depends whether bulbs are connected in series or parallel.

EXAMPLE 2.16

Two electric bulbs marked 20 W – 220 V and 100 W – 220 V are connected in series to 440 V supply. Which bulb will be fused?

Solution

To check which bulb will be fused, the voltage drop across each bulb has to be calculated.

The resistance of a bulb,

$$R = \frac{V^2}{P} = \frac{(\text{Rated voltage})^2}{\text{Rated power}}$$

For 20W-220V bulb,

$$R_1 = \frac{(220)^2}{20} \Omega = 2420 \Omega$$

For 100W-220V bulb,

$$R_2 = \frac{(220)^2}{100} \Omega = 484 \Omega$$



Both the bulbs are connected in series. So the current which passes through both the bulbs are same. The current that passes through the circuit, $I = \frac{V}{R_{tot}}$.

$$R_{tot} = (R_1 + R_2)$$

$$R_{tot} = (484 + 2420)\Omega = 2904\Omega$$

$$I = \frac{440V}{2904\Omega} \approx 0.151A$$

The voltage drop across the 20W bulb is

$$V_1 = IR_1 = \frac{440}{2904} \times 2420 \approx 366.6 V$$

The voltage drop across the 100W bulb is

$$V_2 = IR_2 = \frac{440}{2904} \times 484 \approx 73.3 V$$

The 20 W bulb will be fused because its voltage rating is only 220 V and 366.6 V is dropped across it.

is connected to a circuit, electrons flow from the negative terminal to the positive terminal through the circuit. By using chemical reactions, a battery produces potential difference across its terminals. This potential difference provides the energy to move the electrons through the circuit. Commercially available electric cells and batteries are shown in Figure 2.18



Figure 2.18 Electric cells and Batteries

2.4

ELECTRIC CELLS AND BATTERIES

An electric cell converts chemical energy into electrical energy to produce electricity. It contains two electrodes immersed in an electrolyte as shown in Figure 2.17.



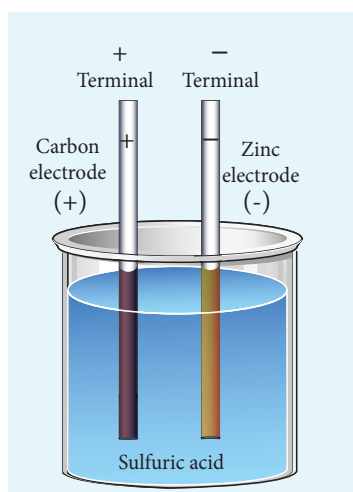


Figure 2.17 Simple electric cell

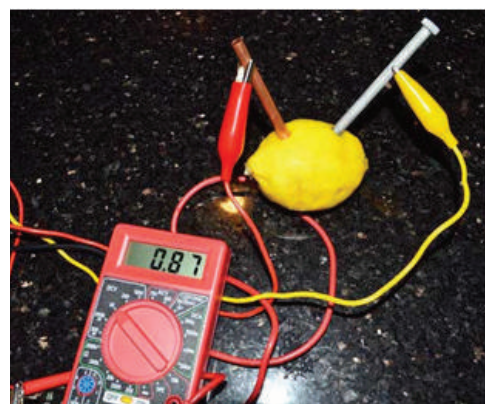Several electric cells connected together form a battery. When a cell or battery



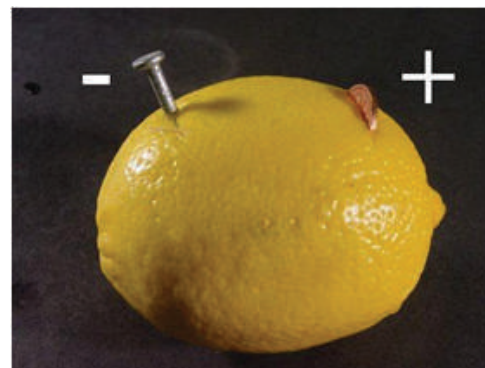If we connect copper and zinc rod in a lemon, it acts as an electric cell. The citric acid in the lemon acts as an electrolyte. The potential can be measured using a multimeter.



2.4.1 Electromotive force and internal resistance

A battery or cell is called a source of electromotive force (emf). The term ‘electromotive force’ is a misnomer since it does not really refer to a force but describes a potential difference in volts. The emf of a battery or cell is the voltage provided by the battery when no current flows in the external circuit. It is shown in Figure 2.19.



Figure 2.19 Measuring the emf of a cell

Electromotive force determines the amount of work a battery or cell does to move a certain amount of charge around the circuit. It is denoted by the symbol ξ and to be pronounced as ‘xi’. An ideal battery has zero internal resistance and the potential difference (terminal voltage) across the battery equals to its emf. But a real battery is made of electrodes and electrolyte, there is resistance to the flow of charges within the battery. This resistance is called internal resistance r . For a real battery, the terminal voltage is not equal to the emf of the battery. A freshly prepared cell has low internal resistance and it increases with ageing.

2.4.2 Determination of internal resistance

The circuit connections are made as shown in Figure 2.20.

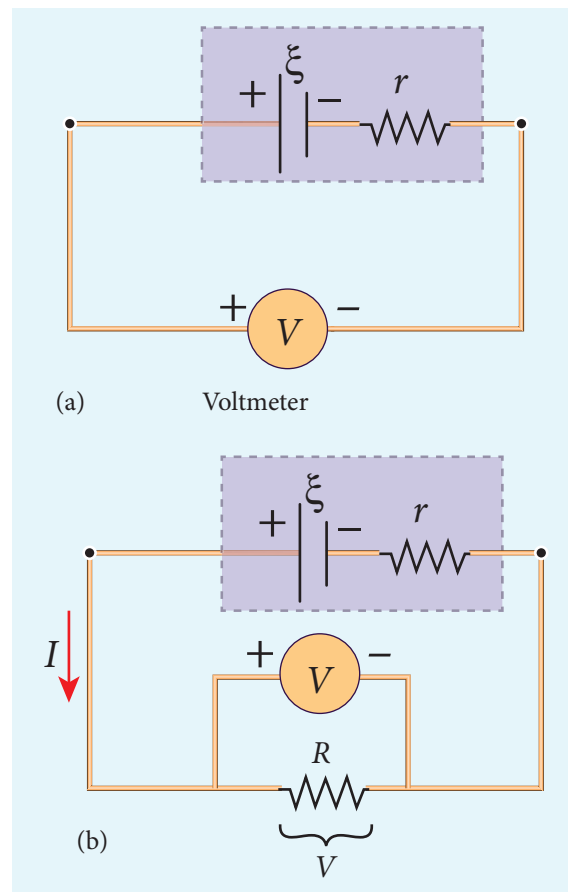


Figure 2.20 Internal resistance of the cell

The emf of cell ξ is measured by connecting a high resistance voltmeter across it without connecting the external resistance R as shown in Figure 2.20(a). Since the voltmeter draws very little current for deflection, the circuit may be considered as open. Hence the voltmeter reading gives the emf of the cell. Then, external resistance R is included in the circuit and current I is established in the circuit. The potential difference across R is equal to the potential difference across the cell (V) as shown in Figure 2.20(b).

The potential drop across the resistor R is

$$V = IR \quad (2.35)$$

Due to internal resistance r of the cell, the voltmeter reads a value V , which is less than the emf of cell ξ . It is because, certain

amount of voltage (Ir) has dropped across the internal resistance r .

Then $V = \xi - Ir$

$$Ir = \xi - V \quad (2.36)$$

Dividing equation (2.36) by equation (2.35), we get

$$\frac{Ir}{IR} = \frac{\xi - V}{V}$$

$$r = \left[\frac{\xi - V}{V} \right] R \quad (2.37)$$

Since ξ , V and R are known, internal resistance r can be determined. We can also find the total current that flows in the circuit.

Due to this internal resistance, the power delivered to the circuit is not equal to power rating mentioned in the battery. For a battery of emf ξ , with an internal resistance r , the power delivered to the circuit of resistance R is given by

$$P = I\xi = I(V + Ir) \quad (\text{from equation 2.36})$$

Here V is the voltage drop across the resistance R and it is equal to IR .

Therefore, $P = I(IR + Ir)$

$$P = I^2 R + I^2 r \quad (2.38)$$

Here $I^2 r$ is the power delivered to the internal resistance and $I^2 R$ is the power delivered to the electrical device (here it is the resistance R). For a good battery, the internal resistance r is very small, then $I^2 r \ll I^2 R$ and almost entire power is delivered to the resistance.

EXAMPLE 2.17

A battery has an emf of 12 V and connected to a resistor of 3Ω . The current in the circuit is 3.93 A. Calculate (a) terminal

voltage and the internal resistance of the battery (b) power delivered by the battery and power delivered to the resistor

Solution

The given values $I = 3.93 \text{ A}$, $\xi = 12 \text{ V}$, $R = 3 \Omega$

(a) The terminal voltage of the battery is equal to voltage drop across the resistor

$$V = IR = 3.93 \times 3 = 11.79 \text{ V}$$

The internal resistance of the battery,

$$r = \left[\frac{\xi - V}{V} \right] R = \left[\frac{12 - 11.79}{11.79} \right] \times 3 = 0.05 \Omega$$

(b) The power delivered by the battery $P = I\xi = 3.93 \times 12 = 47.1 \text{ W}$


The power delivered to the resistor $= I^2 R = 46.3 \text{ W}$

The remaining power $= (47.1 - 46.3) P = 0.772 \text{ W}$ is delivered to the internal resistance and cannot be used to do useful work. (it is equal to $I^2 r$).

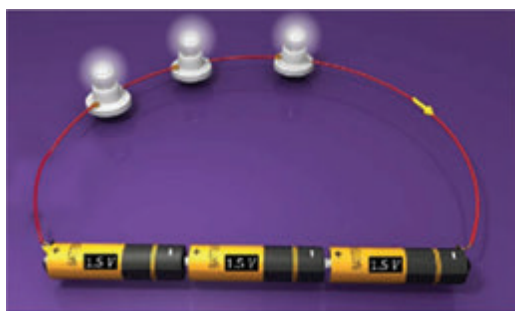
2.4.3 Cells in series

Several cells can be connected to form a battery. In series connection, the negative terminal of one cell is connected to the positive terminal of the second cell, the negative terminal of second cell is connected to the positive terminal of the third cell and so on. The free positive terminal of the first cell and the free negative terminal of the last cell become the terminals of the battery.

Suppose n cells, each of emf ξ volts and internal resistance r ohms are connected in series with an external resistance R as shown in Figure 2.21



Cells in series (Schematic diagram)

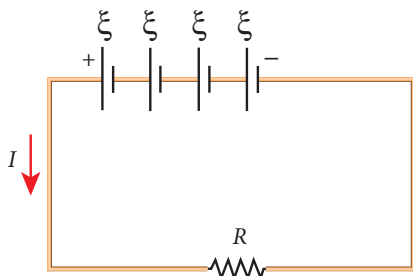

Cells in series (circuit diagram)

Figure 2.21 cells in series

The total emf of the battery = $n\xi$

The total resistance in the circuit = $nr + R$

By Ohm's law, the current in the circuit is

$$I = \frac{\text{total emf}}{\text{total resistance}} = \frac{n\xi}{nr + R} \quad (2.39)$$

Case (a) If $r \ll R$, then,

$$I = \frac{n\xi}{R} \approx nI_1 \quad (2.40)$$

where, I_1 is the current due to a single cell

$$\left(I_1 = \frac{\xi}{R} \right)$$

Thus, if r is negligible when compared to R the current supplied by the battery is n times that supplied by a single cell.


$$\text{Case (b) If } r \gg R, I = \frac{n\xi}{nr} \approx \frac{\xi}{r} \quad (2.41)$$

It is the current due to a single cell. That is, current due to the whole battery is the same as that due to a single cell and hence there is no advantage in connecting several cells.

Thus series connection of cells is advantageous only when the effective internal resistance of the cells is negligibly small compared with R .


ACTIVITY

Construct lemon cells in series and observe the potential of this combination

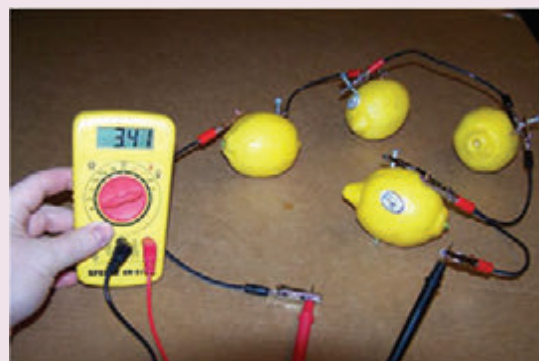

EXAMPLE 2.18

From the given circuit,

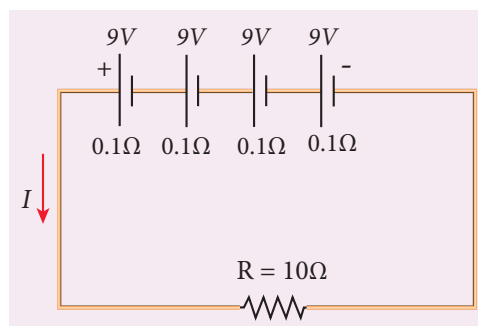

Find

- Equivalent emf of the combination
- Equivalent internal resistance
- Total current
- Potential difference across external resistance
- Potential difference across each cell

Solution

- Equivalent emf of the combination
 $\xi_{eq} = n\xi = 4 \times 9 = 36 \text{ V}$

- ii) Equivalent internal resistance $r_{eq} = nr$
 $= 4 \times 0.1 = 0.4 \Omega$
- iii) Total current $I = \frac{n\xi}{R + nr}$
 $= \frac{4 \times 9}{10 + (4 \times 0.1)}$
 $= \frac{4 \times 9}{10 + 0.4} = \frac{36}{10.4}$
 $I = 3.46 \text{ A}$
- iv) Potential difference across external resistance $V = IR = 3.46 \times 10 = 34.6 \text{ V}$. The remaining 1.4 V is dropped across the internal resistance of cells.
- v) Potential difference across each cell
 $\frac{V}{n} = \frac{34.6}{4} = 8.65 \text{ V}$

2.4.4 Cells in parallel


In parallel connection all the positive terminals of the cells are connected to one point and all the negative terminals to a second point. These two points form the positive and negative terminals of the battery.

Let n cells be connected in parallel between the points A and B and a resistance R is connected between the points A and B as shown in Figure 2.22. Let ξ be the emf and r the internal resistance of each cell.


The equivalent internal resistance of the battery is $\frac{1}{r_{eq}} = \frac{1}{r} + \frac{1}{r} + \dots + \frac{1}{r} (n \text{ terms}) = \frac{n}{r}$. So

$r_{eq} = \frac{r}{n}$ and the total resistance in the circuit $= R + \frac{r}{n}$. The total emf is the potential difference between the points A and B, which is equal to ξ . The current in the circuit is given by

$$I = \frac{\xi}{\frac{r}{n} + R}$$

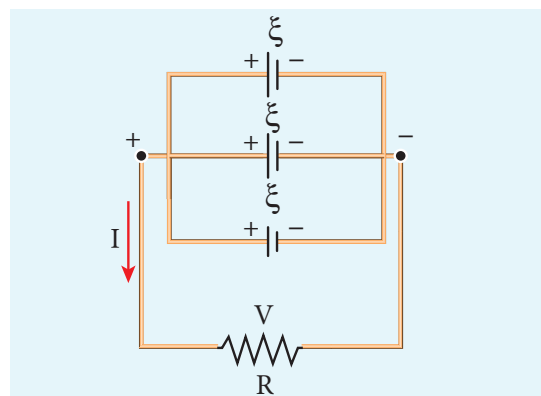

cells in parallel (Circuit diagram)

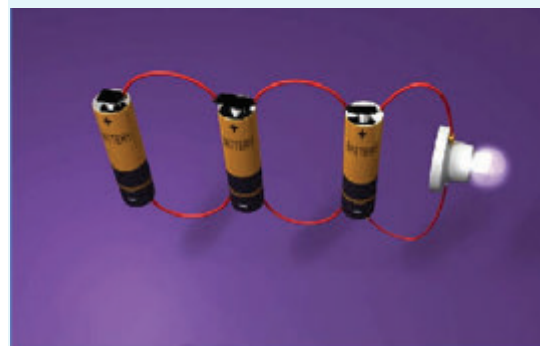

Cells in parallel (Schematic diagram)

Figure 2.22 Cells in parallel

$$I = \frac{n\xi}{r + nR} \quad (2.42)$$

Case (a) If $r \gg R$, $I = \frac{n\xi}{r} = nI_1$ (2.43)

where I_1 is the current due to a single cell and is equal to $\frac{\xi}{r}$ when R is negligible. Thus, the current through the external resistance due to the whole battery is n times the current due to a single cell.

Case (b) If $r \ll R$, $I = \frac{\xi}{R}$ (2.44)




When the car engine is started with headlights turned on, they sometimes become dim. This is due to the internal resistance of the car battery.

The above equation implies that current due to the whole battery is the same as that due to a single cell. Hence it is advantageous to connect cells in parallel when the external resistance is very small compared to the internal resistance of the cells.

EXAMPLE 2.19

From the given circuit

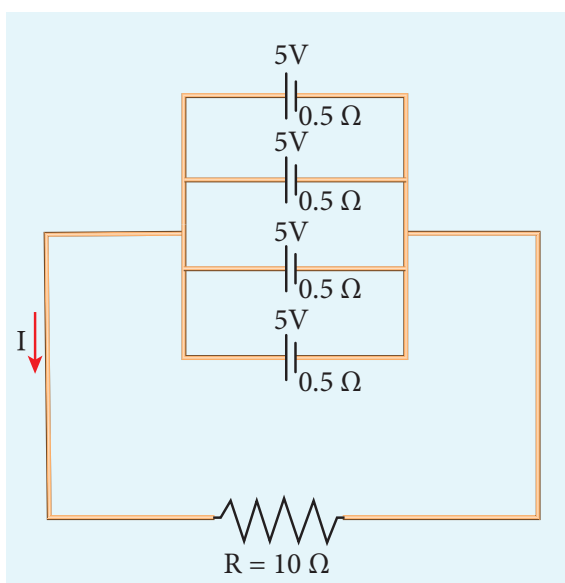

Find

- Equivalent emf
- Equivalent internal resistance
- Total current (I)
- Potential difference across each cell
- Current from each cell

Solution

- Equivalent emf $\xi_{eq} = 5 \text{ V}$
- Equivalent internal resistance,

$$R_{eq} = \frac{r}{n} = \frac{0.5}{4} = 0.125 \Omega$$
- total current, $I = \frac{\xi}{R + r/n}$

$$I = \frac{5}{10 + 0.125} = \frac{5}{10.125}$$

 $I \approx 0.5 \text{ A}$
- Potential difference across each cell
 $V = IR = 0.5 \times 10 = 5 \text{ V}$

v) Current from each cell, $I' = \frac{I}{n}$

$$I' = \frac{0.5}{4} = 0.125 \text{ A}$$

2.5

KIRCHHOFF'S RULES

Ohm's law is useful only for simple circuits. For more complex circuits, Kirchhoff's rules can be used to find current and voltage. There are two generalized rules: i) Kirchhoff's current rule ii) Kirchhoff's voltage rule.

2.5.1 Kirchhoff's first rule (Current rule or Junction rule)

It states that the algebraic sum of the currents at any junction of a circuit is zero. It is a statement of conservation of electric charge. All charges that enter a given junction in a circuit must leave that junction since charge cannot build up or disappear at a junction. Current entering the junction is taken as positive and current leaving the junction is taken as negative.

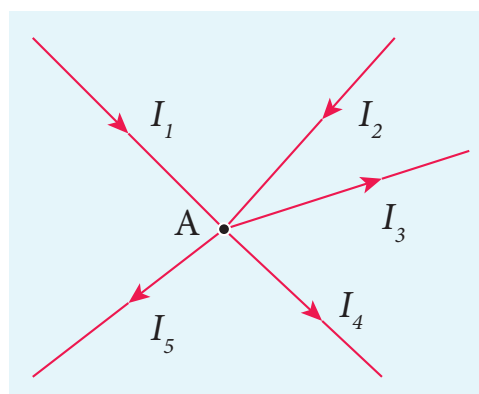


Figure 2.23 Kirchhoff's current rule

Applying this law to the junction A in Figure 2.23


$$I_1 + I_2 - I_3 - I_4 - I_5 = 0$$

(or)

$$I_1 + I_2 = I_3 + I_4 + I_5$$

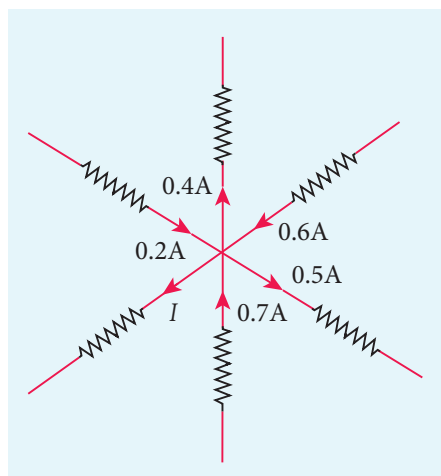EXAMPLE 2.20

From the given circuit find the value of I .



Solution

Applying Kirchoff's rule to the point P in the circuit,

The arrows pointing towards P are positive and away from P are negative.

$$\text{Therefore, } 0.2\text{A} - 0.4\text{A} + 0.6\text{A} - 0.5\text{A} + 0.7\text{A} - I = 0$$

$$1.5\text{A} - 0.9\text{A} - I = 0$$

$$0.6\text{A} - I = 0$$

$$I = 0.6\text{ A}$$

2.5.2 Kirchoff's Second rule (Voltage rule or Loop rule)

It states that in a closed circuit the algebraic sum of the products of the current and resistance of each part of the circuit is equal to the total emf included in the circuit. This rule follows from the law of conservation of energy for an isolated system (The energy supplied by the emf sources is equal to the sum of the energy delivered to all resistors).

The product of current and resistance is taken as positive when the direction of the current is followed. Suppose if the direction of current is opposite to the direction of the loop, then product of current and voltage across the resistor is negative. It is shown in Figure 2.24 (a) and (b). The emf is considered positive when proceeding from the negative to the positive terminal of the cell. It is shown in Figure 2.24 (c) and (d).


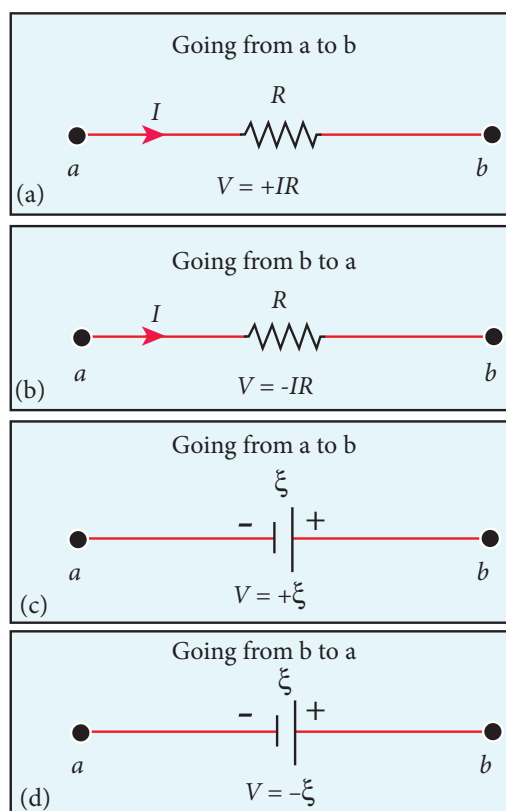


Figure 2.24 Kirchoff voltage rule

Kirchoff voltage rule has to be applied only when all currents in the circuit reach a steady state condition (the current in various branches are constant).

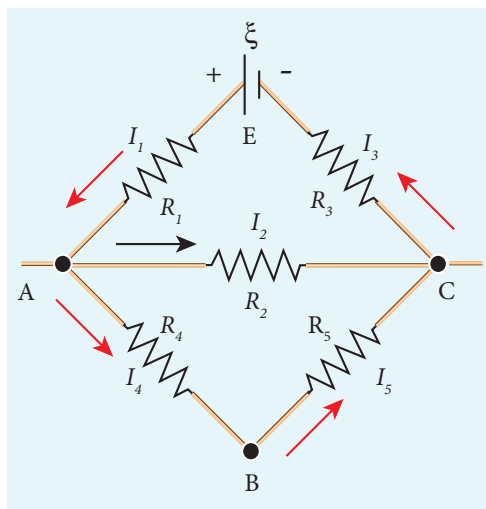EXAMPLE 2.21

The following figure shows a complex network of conductors which can be divided into two closed loops like ACE and ABC. Apply Kirchoff's voltage rule.



Solution

Thus applying Kirchoff's second law to the closed loop EACE

$$I_1 R_1 + I_2 R_2 + I_3 R_3 = \xi$$

and for the closed loop ABCA

$$I_4 R_4 + I_5 R_5 - I_2 R_2 = 0$$

We can denote the current that flows from 9V battery as I_1 and it splits into I_2 and $I_1 - I_2$ in the junction according Kirchoff's current rule (KCR). It is shown below.

Now consider the loop EFCBE and apply KVR, we get

$$1I_2 + 3I_1 + 2I_1 = 9$$

$$5I_1 + I_2 = 9 \quad (1)$$

Applying KVR to the loop EADFE, we get

$$3(I_1 - I_2) - 1I_2 = 6$$

$$3I_1 - 4I_2 = 6 \quad (2)$$


Solving equation (1) and (2), we get

$$I_1 = 1.83 \text{ A and } I_2 = -0.13 \text{ A}$$


It implies that the current in the 1 ohm resistor flows from F to E.

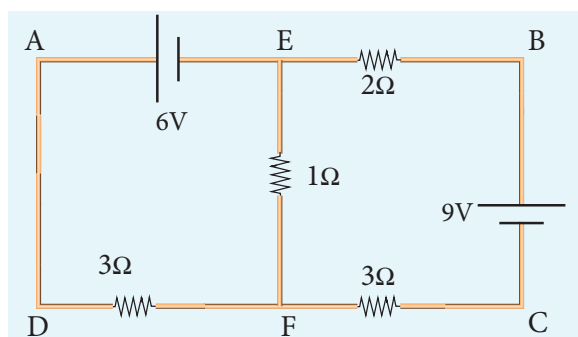EXAMPLE 2.22

Calculate the current that flows in the 1Ω resistor in the following circuit.



Solution

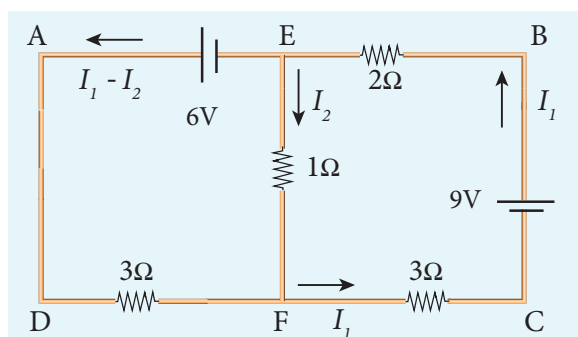

2.5.3 Wheatstone's bridge

An important application of Kirchoff's rules is the Wheatstone's bridge. It is used to compare resistances and also helps in determining the unknown resistance in electrical network. The bridge consists of four resistances P, Q, R and S connected as shown in Figure 2.25. A galvanometer G is connected between the points B and D. The battery is connected between the points A and C. The current through the galvanometer is I_G and its resistance is G.

Applying Kirchoff's current rule to junction B

$$I_1 - I_G - I_3 = 0 \quad (2.45)$$

Applying Kirchoff's current rule to junction D,

$$I_2 + I_G - I_4 = 0 \quad (2.46)$$



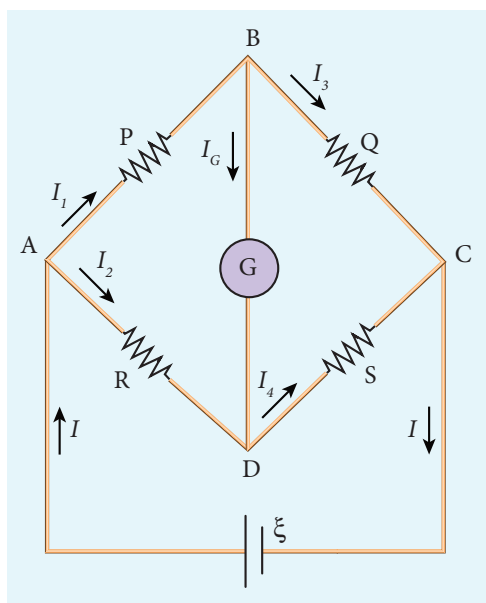


Figure 2.25 Wheatstone's bridge

Applying Kirchhoff's voltage rule to loop ABDA,

$$I_1 P + I_G G - I_2 R = 0 \quad (2.47)$$

Applying Kirchhoff's voltage rule to loop ABCDA,

$$I_1 P + I_3 Q - I_4 S - I_2 R = 0 \quad (2.48)$$

When the points B and D are at the same potential, the bridge is said to be balanced. As there is no potential difference between B and D, no current flows through galvanometer ($I_G = 0$). Substituting $I_G = 0$ in equation (2.45), (2.46) and (2.47), we get

$$I_1 = I_3 \quad (2.49)$$

$$I_2 = I_4 \quad (2.50)$$

$$I_1 P = I_2 R \quad (2.51)$$

Substituting the equation (2.49) and (2.50) in equation (2.48)

$$\begin{aligned} I_1 P + I_1 Q - I_2 S - I_2 R &= 0 \\ I_1 (P + Q) &= I_2 (R + S) \end{aligned} \quad (2.52)$$

Dividing equation (2.52) by equation (2.51), we get

$$\begin{aligned} \frac{P + Q}{P} &= \frac{R + S}{R} \\ 1 + \frac{Q}{P} &= 1 + \frac{S}{R} \\ \frac{Q}{P} &= \frac{S}{R} \\ \frac{P}{Q} &= \frac{R}{S} \end{aligned} \quad (2.53)$$

This is the bridge balance condition. Only under this condition, galvanometer shows null deflection. Suppose we know the values of two adjacent resistances, the other two resistances can be compared. If three of the resistances are known, the value of unknown resistance (fourth one) can be determined.



A galvanometer is an instrument used for detecting and measuring even very small electric currents. It is extensively useful to compare the potential difference between various parts of the circuit.

EXAMPLE 2.23

In a Wheatstone's bridge $P = 100 \, \Omega$, $Q = 1000 \, \Omega$ and $R = 40 \, \Omega$. If the galvanometer shows zero deflection, determine the value of S .

Solution

$$\frac{P}{Q} = \frac{R}{S}$$


$$S = \frac{Q}{P} \times R$$

$$S = \frac{1000}{100} \times 40 \quad S = 400 \, \Omega$$

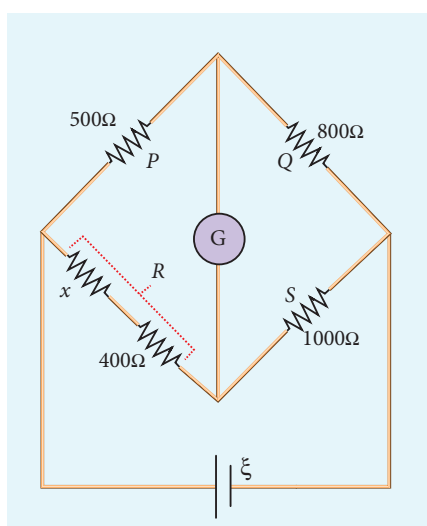EXAMPLE 2.24

What is the value of x when the Wheatstone's network is balanced?

$P = 500 \, \Omega$, $Q = 800 \, \Omega$, $R = x + 400$,
 $S = 1000 \, \Omega$



Solution

$$\frac{P}{Q} = \frac{R}{S}$$

$$\frac{500}{800} = \frac{x + 400}{1000}$$

$$\frac{x + 400}{1000} = \frac{500}{800}$$

$$x + 400 = \frac{500}{800} \times 1000$$

$$x + 400 = \frac{5}{8} \times 1000$$

$$x + 400 = 0.625 \times 1000$$

$$x + 400 = 625$$

$$x = 625 - 400$$

$$x = 225 \, \Omega$$

2.5.4 Meter bridge

The meter bridge is another form of Wheatstone's bridge. It consists of a uniform manganin wire AB of one meter length. This wire is stretched along a meter scale on a wooden board between two copper strips C and D. Between these two copper strips another copper strip E is mounted to enclose two gaps G_1 and G_2 as shown in Figure 2.26. An unknown resistance P is connected in G_1 and a standard resistance Q is connected in G_2 . A jockey (conducting wire) is connected to the terminal E on the central copper strip through a galvanometer (G) and a high resistance (HR). The exact position of jockey on the wire can be read on the scale. A Leclanche cell and a key (K) are connected across the ends of the bridge wire.

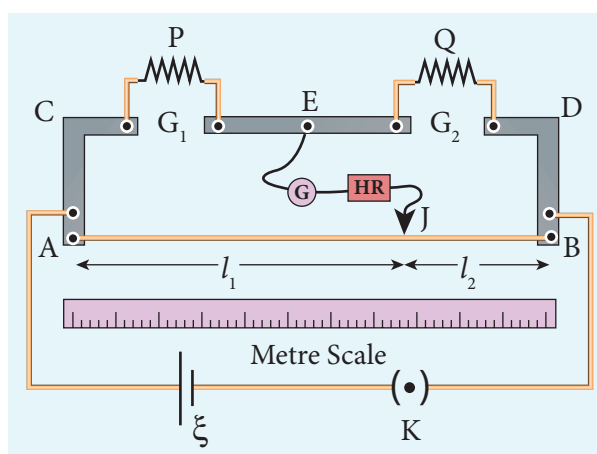


Figure 2.26 Meter bridge

The position of the jockey on the wire is adjusted so that the galvanometer shows zero deflection. Let the point be J. The lengths AJ and JB of the bridge wire now replace the resistance R and S of the Wheatstone's bridge. Then

$$\frac{P}{Q} = \frac{R}{S} = \frac{R'.AJ}{R'.JB} \quad (2.54)$$

where R' is the resistance per unit length of wire

$$\frac{P}{Q} = \frac{AJ}{JB} = \frac{l_1}{l_2} \quad (2.55)$$

$$P = Q \frac{l_1}{l_2} \quad (2.56)$$

The bridge wire is soldered at the ends of the copper strips. Due to imperfect contact, some resistance might be introduced at the contact. These are called end resistances. This error can be eliminated, if another set of readings are taken with P and Q interchanged and the average value of P is found.

To find the specific resistance of the material of the wire in the coil P , the radius r and length l of the wire is measured. The specific resistance or resistivity ρ can be calculated using the relation

$$\text{Resistance} = \rho \frac{l}{A}$$

By rearranging the above equation, we get

$$\rho = \text{Resistance} \times \frac{A}{l} \quad (2.57)$$

If P is the unknown resistance equation (2.57) becomes,

$$\rho = P \frac{\pi r^2}{l}$$

EXAMPLE 2.25

In a meter bridge with a standard resistance of 15Ω in the right gap, the ratio of balancing length is 3:2. Find the value of the other resistance.

Solution

$$Q = 15 \Omega, \quad l_1:l_2 = 3:2$$

$$\frac{l_1}{l_2} = \frac{3}{2}$$

$$\frac{P}{Q} = \frac{l_1}{l_2}$$

$$P = Q \frac{l_1}{l_2}$$

$$P = 15 \frac{3}{2} = 22.5 \Omega$$

EXAMPLE 2.26

In a meter bridge, the value of resistance in the resistance box is 10Ω . The balancing length is $l_1 = 55$ cm. Find the value of unknown resistance.

Solution

$$Q = 10 \Omega$$

$$\frac{P}{Q} = \frac{l_1}{100 - l_1} = \frac{l_1}{l_2}$$

$$P = Q \times \frac{l_1}{100 - l_1}$$

$$P = \frac{10 \times 55}{100 - 55}$$

$$P = \frac{550}{45} = 12.2 \Omega$$

2.5.5 Potentiometer

Potentiometer is used for the accurate measurement of potential differences, current and resistances. It consists of ten meter long uniform wire of manganin or constantan stretched in parallel rows each of 1 meter length, on a wooden board. The two free ends A and B are brought to the same side and fixed to copper strips with binding screws. A meter scale is fixed parallel to the wire. A jockey is provided for making contact.

The principle of the potentiometer is illustrated in Figure 2.27. A steady current is maintained across the wire CD by a battery

Bt. The battery, key and the potentiometer wire are connected in series forms the primary circuit. The positive terminal of a primary cell of emf ξ is connected to the point C and negative terminal is connected to the jockey through a galvanometer G and a high resistance HR. This forms the secondary circuit.

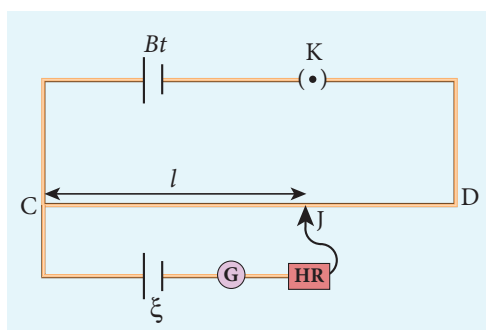


Figure 2.27 Potentiometer

Let contact be made at any point J on the wire by jockey. If the potential difference across CJ is equal to the emf of the cell ξ then no current will flow through the galvanometer and it will show zero deflection. CJ is the balancing length l . The potential difference across CJ is equal to Irl where I is the current flowing through the wire and r is the resistance per unit length of the wire.

$$\text{Hence } \xi = Irl \quad (2.58)$$

Since I and r are constants, $\xi \propto l$. The emf of the cell is directly proportional to the balancing length.

2.5.6 Comparison of emf of two cells with a potentiometer

To compare the emf of two cells, the circuit connections are made as shown in Figure 2.28. Potentiometer wire CD is connected to a battery Bt and a key K in

series. This is the primary circuit. The end C of the wire is connected to the terminal M of a DPDT (Double Pole Double Throw) switch and the other terminal N is connected to a jockey through a galvanometer G and a high resistance HR. The cells whose emf ξ_1 and ξ_2 to be compared are connected to the terminals M_1, N_1 and M_2, N_2 of the DPDT switch. The positive terminals of Bt , ξ_1 and ξ_2 should be connected to the same end C.

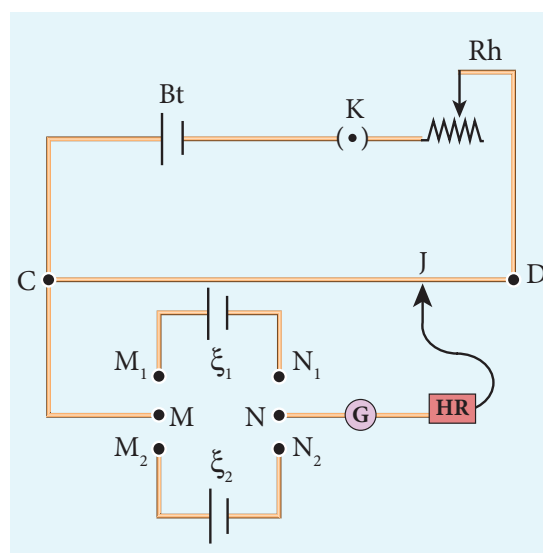


Figure 2.28 Comparison of emf of two cells

The DPDT switch is pressed towards M_1, N_1 so that cell ξ_1 is included in the secondary circuit and the balancing length l_1 is found by adjusting the jockey for zero deflection. Then the second cell ξ_2 is included in the circuit and the balancing length l_2 is determined. Let r be the resistance per unit length of the potentiometer wire and I be the current flowing through the wire.

$$\text{we have } \xi_1 = Irl_1 \quad (2.59)$$

$$\xi_2 = Irl_2 \quad (2.60)$$

By dividing equation (2.59) by (2.60)

$$\frac{\xi_1}{\xi_2} = \frac{l_1}{l_2} \quad (2.61)$$

By including a rheostat (Rh) in the primary circuit, the experiment can be repeated several times by changing the current flowing through it.

2.5.7 Measurement of internal resistance of a cell by potentiometer

To measure the internal resistance of a cell, the circuit connections are made as shown in Figure 2.29. The end C of the potentiometer wire is connected to the positive terminal of the battery Bt and the negative terminal of the battery is connected to the end D through a key K_1 . This forms the primary circuit.

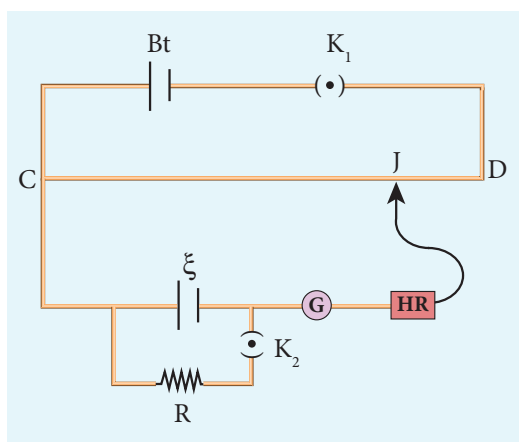


Figure 2.29 measurement of internal resistance

The positive terminal of the cell ξ whose internal resistance is to be determined is also connected to the end C of the wire. The negative terminal of the cell ξ is connected to a jockey through a galvanometer and a high resistance. A resistance box R and key K_2 are connected across the cell ξ . With K_2 open, the balancing point J is obtained and the balancing length CJ = l_1 is measured. Since the cell is in open circuit, its emf is

$$\xi \propto l_1 \quad (2.62)$$

A suitable resistance (say, 10Ω) is included in the resistance box and key K_2 is closed. Let r be the internal resistance of the cell. The current passing through the cell and the resistance R is given by

$$I = \frac{\xi}{R+r}$$

The potential difference across R is

$$V = \frac{\xi R}{R+r}$$

When this potential difference is balanced on the potentiometer wire, let l_2 be the balancing length.

$$\text{Then } \frac{\xi R}{R+r} \propto l_2 \quad (2.63)$$

From equations (2.62) and (2.63)

$$\frac{R+r}{R} = \frac{l_1}{l_2} \quad (2.64)$$

$$1 + \frac{r}{R} = \frac{l_1}{l_2};$$

$$r = R \left[\frac{l_1}{l_2} - 1 \right]$$

$$\therefore r = R \left(\frac{l_1 - l_2}{l_2} \right) \quad (2.65)$$

Substituting the values of the R, l_1 and l_2 , the internal resistance of the cell is determined. The experiment can be repeated for different values of R. It is found that the internal resistance of the cell is not constant but increases with increase of external resistance connected across its terminals.

2.6

HEATING EFFECT OF ELECTRIC CURRENT

When current flows through a resistor, some of the electrical energy delivered to the resistor is converted into heat energy and it is dissipated. This heating effect of

current is known as Joule's heating effect. Just as current produces thermal energy, thermal energy may also be suitably used to produce an electromotive force. This is known as thermoelectric effect.

2.6.1 Joule's law

If a current I flows through a conductor kept across a potential difference V for a time t , the work done or the electric potential energy spent is

$$W = VIt \quad (2.66)$$

In the absence of any other external effect, this energy is spent in heating the conductor. The amount of heat (H) produced is

$$H = VIt \quad (2.67)$$

For a resistance R ,

$$H = I^2 R t \quad (2.68)$$

This relation was experimentally verified by Joule and is known as Joule's law of heating. It states that **the heat developed in an electrical circuit due to the flow of current varies directly as**

- (i) **the square of the current**
- (ii) **the resistance of the circuit and**
- (iii) **the time of flow.**

EXAMPLE 2.27

Find the heat energy produced in a resistance of 10Ω when 5 A current flows through it for 5 minutes.

Solution

$$R = 10 \Omega, I = 5 \text{ A}, t = 5 \text{ minutes} = 5 \times 60 \text{ s}$$

$$H = I^2 R t$$

$$= 5^2 \times 10 \times 5 \times 60$$

$$= 25 \times 10 \times 300$$

$$= 25 \times 3000$$

$$= 75000 \text{ J (or) } 75 \text{ kJ}$$

2.6.2 Application of Joule's heating effect

1. Electric heaters

Electric iron, electric heater, electric toaster shown in Figure 2.30 are some of the home appliances that utilize the heating effect of current. In these appliances, the heating elements are made of nichrome, an alloy of nickel and chromium. Nichrome has a high specific resistance and can be heated to very high temperatures without oxidation.

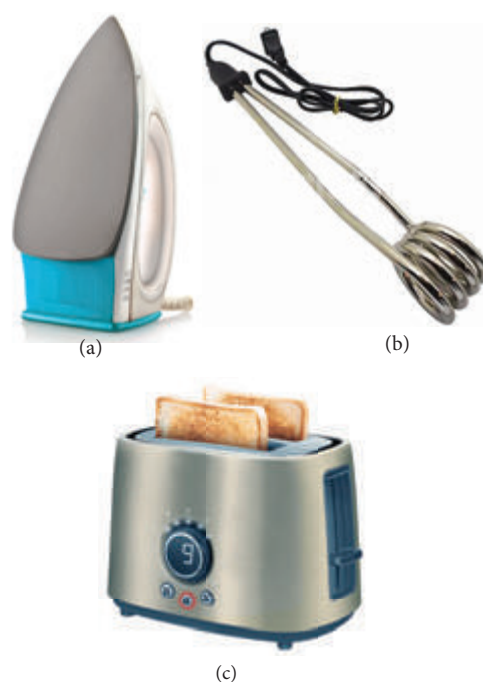


Figure 2.30 (a) Electric Iron box, (b) electric heater (c) electric Toaster

EXAMPLE 2.28

An electric heater of resistance 10Ω connected to 220 V power supply is immersed in the water of 1 kg . How long the electrical heater has to be switched on to increase its temperature from 30°C to 60°C . (The specific heat of water is $s = 4200 \text{ J kg}^{-1}$)



Solution

According to Joule's heating law $H = I^2 R t$

The current passed through the electrical

$$\text{heater} = \frac{220V}{10\Omega} = 22 A$$

The heat produced in one second by the electrical heater $H = I^2 R$

The heat produced in one second $H = (22)^2 \times 10 = 4840 \text{ J} = 4.84 \text{ kJ}$. In fact the power rating of this electrical heater is 4.84 k W.

The amount of energy to increase the temperature of 1kg water from 30°C to 60°C is

$$Q = ms \Delta T \quad (\text{Refer XI physics vol 2, unit 8})$$

Here $m = 1 \text{ kg}$,

$$s = 4200 \text{ J kg}^{-1},$$

$$\Delta T = 30,$$

$$\text{so } Q = 1 \times 4200 \times 30 = 126 \text{ kJ}$$

$$\text{The time required to produce this heat energy } t = \frac{Q}{I^2 R} = \frac{126 \times 10^3}{4840} \approx 26.03 \text{ s}$$

2. Electric fuses

Fuses as shown in Figure 2.31, are connected in series in a circuit to protect the electric devices from the heat developed by the passage of excessive current. It is a short length of a wire made of a low melting point material. It melts and breaks the circuit if current exceeds a certain value. Lead and copper wire melts and burns out when the current increases above 5 A and 35 A respectively.

The only disadvantage with the above fuses is that once fuse wire is burnt due to excessive current, they need to be replaced. Nowadays in houses, circuit breakers (trippers) are also used instead of fuses.

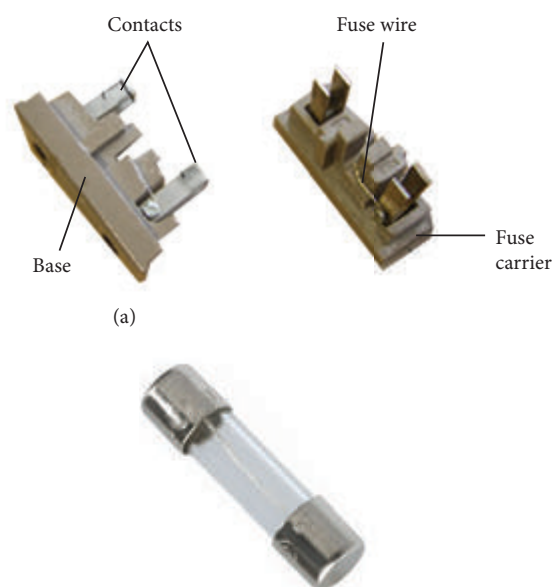


Figure 2.31 Electric Fuse

Whenever there is an excessive current produced due to faulty wire connection, the circuit breaker switch opens. After repairing the faulty connection, we can close the circuit breaker switch. It is shown in the Figure 2.32.



Figure 2.32 circuit breakers

3. Electric furnace

Furnaces as shown in Figure 2.33 are used to manufacture a large number of technologically important materials such as steel, silicon carbide, quartz, gallium arsenide, etc). To produce temperatures up to 1500°C, molybdenum-nichrome wire wound on a silica tube is used. Carbon arc furnaces produce temperatures up to 3000 °C.



Figure 2.33 Electric furnace

4. Electrical lamp

It consists of a tungsten filament (melting point $3380\text{ }^{\circ}\text{C}$) kept inside a glass bulb and heated to incandescence by current. In incandescent electric lamps only about 5% of electrical energy is converted into light and the rest is wasted as heat. Electric discharge lamps, electric welding and electric arc also utilize the heating effect of current as shown in Figure 2.34.

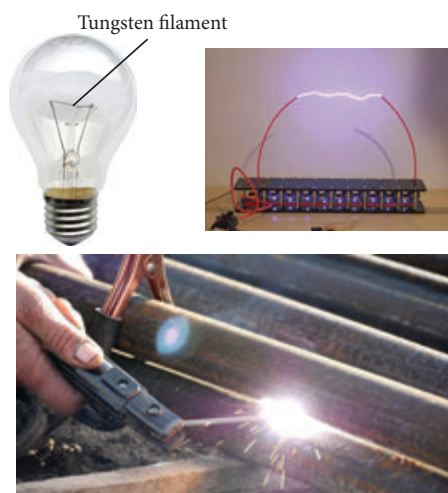


Figure 2.34 Electric bulb, electric arc and electric welding

2.7

THERMOELECTRIC EFFECT

Conversion of temperature differences into electrical voltage and vice versa is known as thermoelectric effect. A thermoelectric device generates voltage when there is a temperature difference on each side. If a voltage is applied, it generates a temperature difference.

2.7.1 Seebeck effect

Seebeck discovered that in a closed circuit consisting of two dissimilar metals, when the junctions are maintained at different temperatures an emf (potential difference) is developed. The current that flows due to the emf developed is called thermoelectric current. The two dissimilar metals connected to form two junctions is known as thermocouple (Figure 2.35).

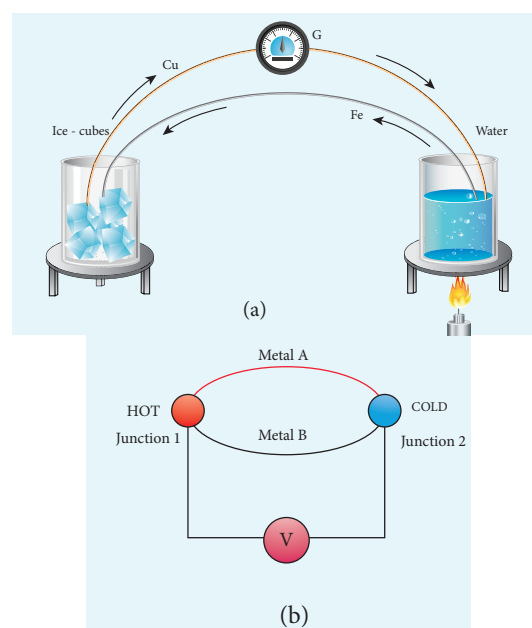


Figure 2.35 Seebeck effect (Thermocouple)

If the hot and cold junctions are interchanged, the direction of current also reverses. Hence the effect is reversible.

The magnitude of the emf developed in a thermocouple depends on (i) the nature of the metals forming the couple and (ii) the temperature difference between the junctions.

Applications of Seebeck effect

1. Seebeck effect is used in thermoelectric generators (Seebeck generators). These thermoelectric generators are used in power plants to convert waste heat into electricity.

- This effect is utilized in automobiles as automotive thermoelectric generators for increasing fuel efficiency.
- Seebeck effect is used in thermocouples and thermopiles to measure the temperature difference between the two objects.

2.7.2 Peltier effect

In 1834, Peltier discovered that **when an electric current is passed through a circuit of a thermocouple, heat is evolved at one junction and absorbed at the other junction. This is known as Peltier effect.**

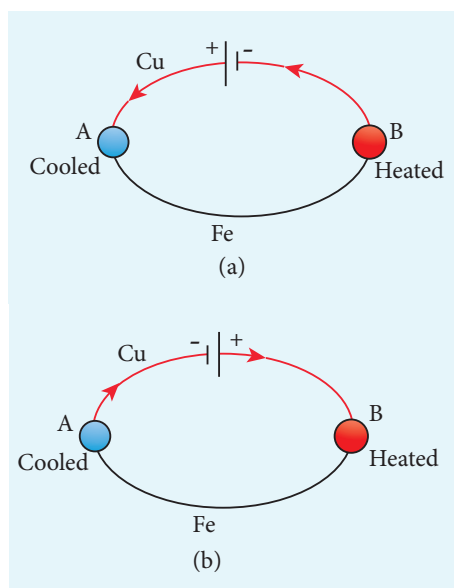


Figure 2.36 Peltier effect: Cu – Fe thermocouple

In the Cu-Fe thermocouple the junctions A and B are maintained at the same temperature. Let a current from a battery flow through the thermocouple (Figure 2.36 (a)). At the junction A, where the current flows from Cu to Fe, heat is absorbed and the junction A becomes cold. At the junction B, where the current flows from Fe to Cu heat is liberated and it becomes hot. When the direction of current is reversed, junction A

gets heated and junction B gets cooled as shown in the Figure 2.36(b). Hence Peltier effect is reversible.

2.7.3 Thomson effect

Thomson showed that **if two points in a conductor are at different temperatures, the density of electrons at these points will differ and as a result the potential difference is created between these points. Thomson effect is also reversible.**

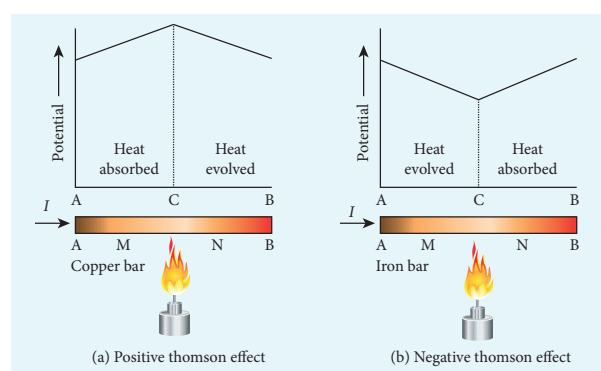


Figure 2.37 (a) Positive Thomson effect
(b) Negative Thomson effect


If current is passed through a copper bar AB which is heated at the middle point C, the point C will be at higher potential. This indicates that the heat is absorbed along AC and evolved along CB of the conductor as shown in Figure 2.37(a). Thus heat is transferred due to the current flow in the direction of the current. It is called positive Thomson effect. Similar effect is observed in metals like silver, zinc, and cadmium.

When the copper bar is replaced by an iron bar, heat is evolved along CA and absorbed along CB. Thus heat is transferred due to the current flow in the direction opposite to the direction of current. It is called negative Thomson effect as shown in the Figure 2.37(b). Similar effect is observed in metals like platinum, nickel, cobalt, and mercury.

SUMMARY

- The current, I flowing in a conductor $I = \frac{dQ}{dt}$, where dQ is the charge that flows through a cross-section in a time interval dt . SI unit of current is ampere (A).
 $1\text{A} = 1\text{C s}^{-1}$.
- The current density J in a conductor is the current flowing per unit area. $\left(J = \frac{I}{A} \right)$
- Current is a scalar but current density is a vector.
- The general form of Ohm's law $\vec{J} = \sigma \vec{E}$
- Practical form of Ohm's law states that $V \propto I$, or $V = IR$ where I is the current.
- The resistance R of a conductor is $R = \frac{V}{I}$. SI unit of resistance is ohm (Ω) and
 $1\ \Omega = \frac{1\text{V}}{1\text{A}}$
- The resistance of a material $R = \rho \frac{l}{A}$ where l is length of the material and A is the area of cross section.
- The resistivity of a material determines how much resistance it offers to the flow of current.
- The equivalent resistance (R_s) of several resistances (R_1, R_2, R_3, \dots) connected in series combination is $R_s = (R_1 + R_2 + R_3, \dots)$
- The equivalent resistance (R_p) of several resistances (R_1, R_2, R_3, \dots) connected in parallel combination is $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$
- Kirchoff's first rule (Current rule or junction rule): The algebraic sum of the currents at any junction is zero.
- Kirchoff's second rule (Voltage rule or loop rule): In a closed circuit the algebraic sum of the products of the current and resistance of each part of the circuit is equal to the total emf included in the circuit.
- Electric power is the rate at which energy is transformed.
- If a current I flows across a potential difference V , the power delivered to the circuit is $P = IV$.
- In a resistor R , the electrical power converted to heat is $P = I^2R = \frac{V^2}{R}$
- The energy equivalent of one kilowatt-hour (kWh) is $1\text{kWh} = 3.6 \times 10^6\text{ J}$.
- Metre bridge is one form of Wheatstone's bridge.
- Potentiometer is used to compare potential differences.
- Joule's law of heating is $H = VIt$ (or) $H = I^2Rt$.
- Thermoelectric effect: Conversion of temperature differences into electrical voltage and vice versa.

CONCEPT MAP

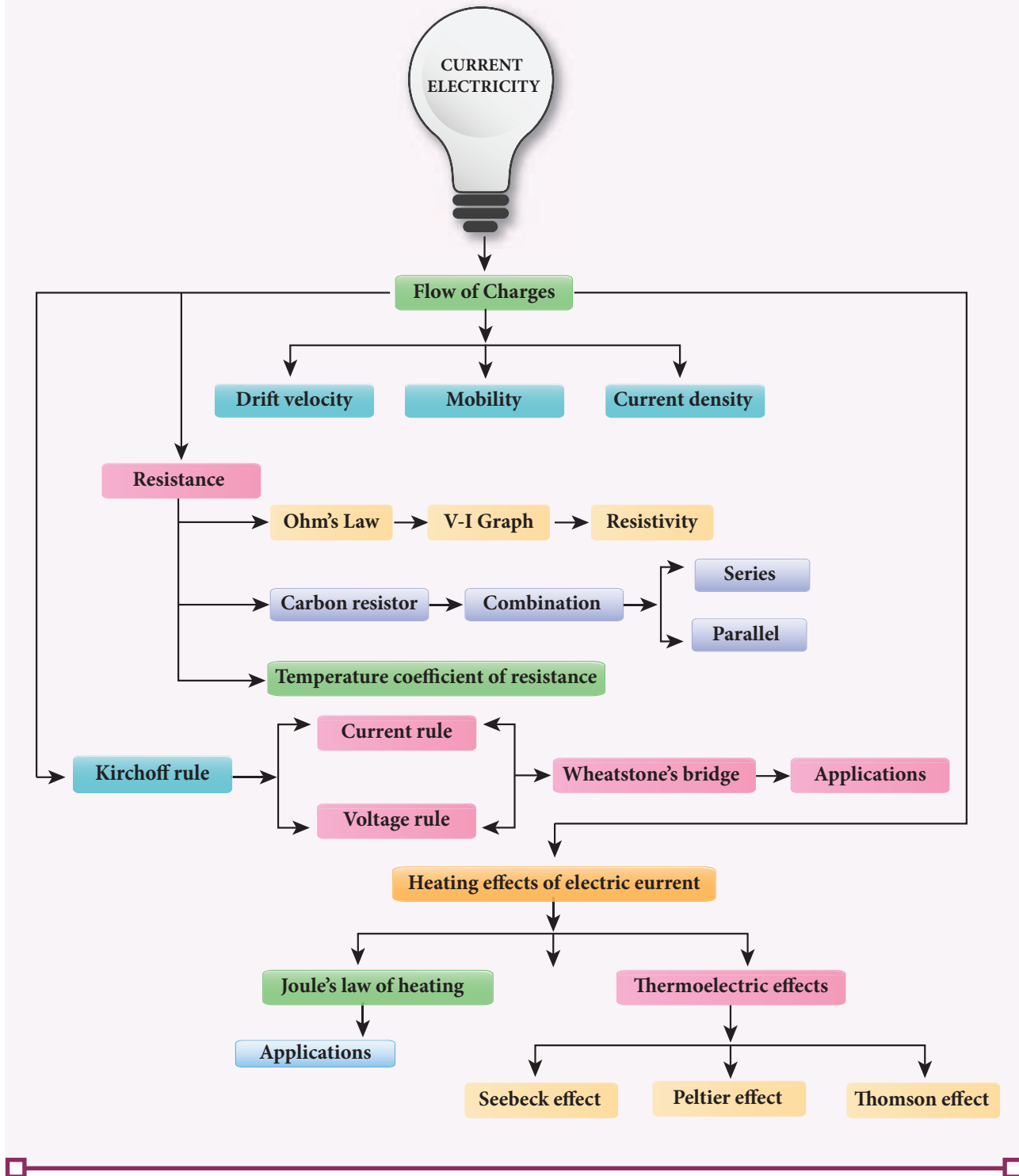




EVALUATION




I Multiple Choice Questions

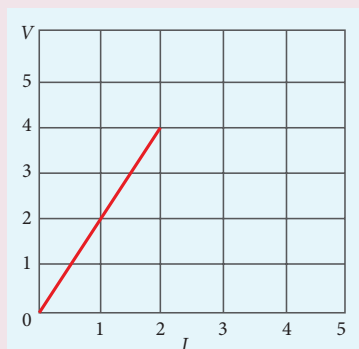1. The following graph shows current versus voltage values of some unknown conductor. What is the resistance of this conductor?



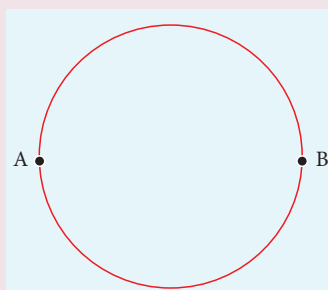- (a) 2 ohm
(b) 4 ohm
(c) 8 ohm
(d) 1 ohm
2. A wire of resistance 2 ohms per meter is bent to form a circle of radius 1m. The equivalent resistance between its two diametrically opposite points, A and B as shown in the figure is



- (a) $\pi \Omega$
(b) $\frac{\pi}{2} \Omega$
(c) $2\pi \Omega$
(d) $\frac{\pi}{4} \Omega$
3. A toaster operating at 240 V has a resistance of 120 Ω . The power is
- a) 400 W
b) 2 W
c) 480 W
d) 240 W

4. A carbon resistor of $(47 \pm 4.7) \text{ k}\Omega$ to be marked with rings of different colours for its identification. The colour code sequence will be
- a) Yellow – Green – Violet – Gold
b) Yellow – Violet – Orange – Silver
c) Violet – Yellow – Orange – Silver
d) Green – Orange – Violet – Gold
5. What is the value of resistance of the following resistor?



- (a) 100 k Ω
(b) 10 k Ω
(c) 1k Ω
(d) 1000 k Ω
6. Two wires of A and B with circular cross section made up of the same material with equal lengths. Suppose $R_A = 3 R_B$, then what is the ratio of radius of wire A to that of B?
- (a) 3
(b) $\sqrt{3}$
(c) $\frac{1}{\sqrt{3}}$
(d) $\frac{1}{3}$
7. A wire connected to a power supply of 230 V has power dissipation P_1 . Suppose the wire is cut into two equal pieces and connected parallel to the same power supply. In this case power dissipation is P_2 . The ratio $\frac{P_2}{P_1}$ is
- (a) 1
(b) 2
(c) 3
(d) 4




8. In India electricity is supplied for domestic use at 220 V. It is supplied at 110 V in USA. If the resistance of a 60W bulb for use in India is R , the resistance of a 60W bulb for use in USA will be

- (a) R (b) $2R$
 (c) $\frac{R}{4}$ (d) $\frac{R}{2}$

9. In a large building, there are 15 bulbs of 40W, 5 bulbs of 100W, 5 fans of 80W and 1 heater of 1kW are connected. The voltage of electric mains is 220V. The minimum capacity of the main fuse of the building will be (IIT-JEE 2014)


- (a) 14 A (b) 8 A
 (c) 10 A (d) 12 A

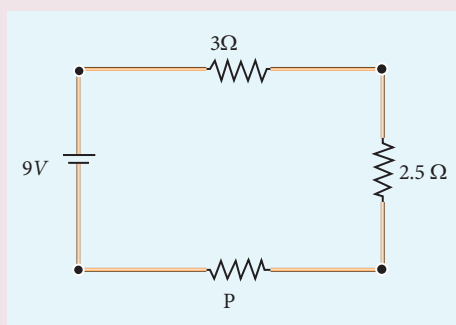10. There is a current of 1.0 A in the circuit shown below. What is the resistance of P?



- (a) 1.5 Ω (b) 2.5 Ω
 (c) 3.5 Ω (d) 4.5 Ω

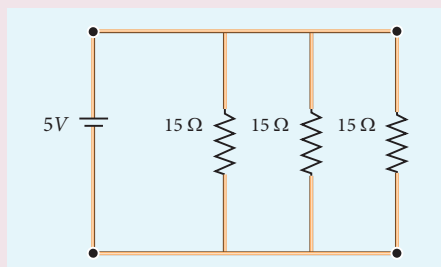11. What is the current out of the battery?



- a) 1A (b) 2A
 c) 3A (d) 4A

12. The temperature coefficient of resistance of a wire is 0.00125 per °C. At 300 K, its resistance is 1 Ω. The resistance of the wire will be 2 Ω at

- a) 1154 K (b) 1100 K
 c) 1400 K (d) 1127 K

13. The internal resistance of a 2.1 V cell which gives a current of 0.2 A through a resistance of 10 Ω is

- a) 0.2 Ω (b) 0.5 Ω
 c) 0.8 Ω (d) 1.0 Ω

14. A piece of copper and another of germanium are cooled from room temperature to 80 K. The resistance of

- a) each of them increases
 b) each of them decreases
 c) copper increases and germanium decreases
 d) copper decreases and germanium increases

15. In Joule's heating law, when I and t are constant, if the H is taken along the y axis and I^2 along the x axis, the graph is

- a) straight line (b) parabola
 c) circle (d) ellipse

Answers

- 1) a 2) b 3) c 4) b 5) a
 6) c 7) d 8) c 9) d 10) c
 11) a 12) d 13) b 14) d 15) a

II Short Answer Questions

- Why current is a scalar?
- Distinguish between drift velocity and mobility.
- State microscopic form of Ohm's law.

4. State macroscopic form of Ohm's law.
5. What are ohmic and non ohmic devices?
6. Define electrical resistivity.
7. Define temperature coefficient of resistance.
8. What is superconductivity?
9. What is electric power and electric energy?
10. Define current density.
11. Derive the expression for power $P=VI$ in electrical circuit.
12. Write down the various forms of expression for power in electrical circuit.
13. State Kirchhoff's current rule.
14. State Kirchhoff's voltage rule.
15. State the principle of potentiometer.
16. What do you mean by internal resistance of a cell?
17. State Joule's law of heating.
18. What is Seebeck effect?
19. What is Thomson effect?
20. What is Peltier effect?
21. State the applications of Seebeck effect.


III Long Answer Questions

1. Describe the microscopic model of current and obtain general form of Ohm's law
2. Obtain the macroscopic form of Ohm's law from its microscopic form and discuss its limitation.
3. Explain the equivalent resistance of a series and parallel resistor network
4. Explain the determination of the internal resistance of a cell using voltmeter.

5. State and explain Kirchhoff's rules.
6. Obtain the condition for bridge balance in Wheatstone's bridge.
7. Explain the determination of unknown resistance using meter bridge.
8. How the emf of two cells are compared using potentiometer?

IV Numerical problems

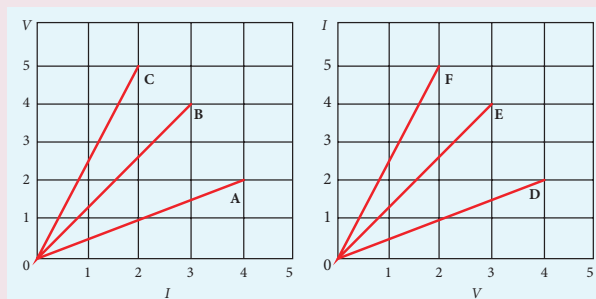1. The following graphs represent the current versus voltage and voltage versus current for the six conductors A,B,C,D,E and F. Which conductor has least resistance and which has maximum resistance?



- Ans: Least: $R_F = 0.4 \Omega$, maximum $R_C = 2.5 \Omega$
2. Lightning is very good example of natural current. In typical lightning, there is 10^9 J energy transfer across the potential difference of 5×10^7 V during a time interval of 0.2 s.



Using this information, estimate the following quantities (a) total amount of charge transferred between cloud and ground (b) the current in the lightning bolt (c) the power delivered in 0.2 s.

Ans: charge = 20 C, $I = 100$ A, $P = 5$ GW

3. A copper wire of 10^{-6} m² area of cross section, carries a current of 2 A. If the number of electrons per cubic meter is 8×10^{28} , calculate the current density and average drift velocity.


Ans: $J = 2 \times 10^6$ Am⁻²; $v_d = 15.6 \times 10^{-5}$ ms⁻¹

4. The resistance of a nichrome wire at 0 °C is 10 Ω. If its temperature coefficient of resistance is 0.004/°C, find its resistance at boiling point of water. Comment on the result.

Ans: $R_T = 14$ Ω.

As the temperature increases the resistance of the wire also increases.

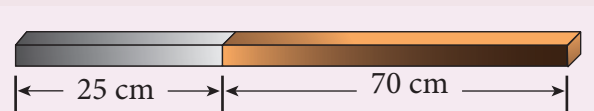
5. The rod given in the figure is made up of two different materials.



Both have square cross sections of 3 mm side. The resistivity of the first material is 4×10^{-3} Ω.m and it is 25 cm long while second material has resistivity of 5×10^{-3} Ω.m and is of 70 cm long. What is the resistivity of rod between its ends?

Ans: 500 Ω

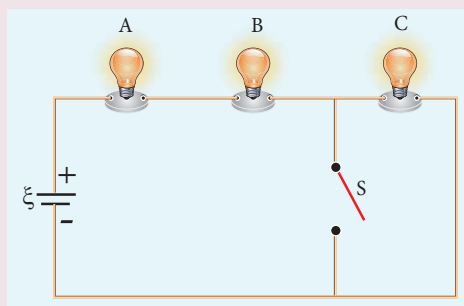6. Three identical lamps each having a resistance R are connected to the battery of emf as shown in the figure.



Suddenly the switch S is closed. (a) Calculate the current in the circuit when S is open and closed (b) What happens to the intensities of the bulbs A, B and C . (c) Calculate the voltage across the three bulbs when S is open and closed (d) Calculate the power delivered to the circuit when S is opened and closed (e) Does the power delivered to the circuit decreases, increases or remain same?

Ans:

Electrical quantities	Switch S is open	Switch S is closed
Current	$\frac{\xi}{3R}$	$\frac{\xi}{2R}$
Voltage	$V_A = \frac{\xi}{3R}$, $V_B = \frac{\xi}{3R}$, $V_C = \frac{\xi}{3R}$	$V_A = \frac{\xi}{2R}$, $V_B = \frac{\xi}{2R}$, $V_C = 0$
Power	$P_A = \frac{\xi^2}{9R}$, $P_B = \frac{\xi^2}{9R}$, $P_C = \frac{\xi^2}{9R}$	$P_A = \frac{\xi^2}{4R}$, $P_B = \frac{\xi^2}{4R}$, $P_C = 0$ Total power increases
Intensity	All the bulbs glow with equal intensity	The intensities of the bulbs A and B equally increase. Bulb C will not glow since no current pass through it.

7. The current through an element is shown in the figure. Determine the total charge that pass through the element at a) $t = 0$ s, b) $t = 2$ s, c) $t = 5$ s



Ans: At $t = 0$ s, $dq = 0$ C, At $t = 2$ s,
 $dq = 10$ C; At $t = 5$ s, $dq = 0$ C


8. An electronics hobbyist is building a radio which requires 150Ω in her circuit, but she has only 220Ω , 79Ω and 92Ω resistors available. How can she connect the available resistors to get desired value of resistance?

Ans: Parallel combination of 220Ω and 79Ω in series with 92Ω

9. A cell supplies a current of 0.9 A through a 2Ω resistor and a current of 0.3 A through a 7Ω resistor. Calculate the internal resistance of the cell.

Ans: 0.5Ω

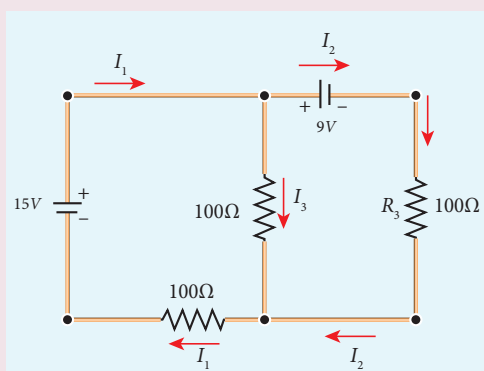10. Calculate the currents in the following circuit.




Ans : $I_1 = 0.070$ A, $I_2 = -0.010$ A and
 $I_3 = 0.080$ A

11. A potentiometer wire has a length of 4 m and resistance of 20Ω . It is connected in series with resistance of 2980Ω and a cell of emf 4 V. Calculate the potential along the wire.

Ans: Potential = $0.65 \times 10^{-2} \text{ V m}^{-1}$.

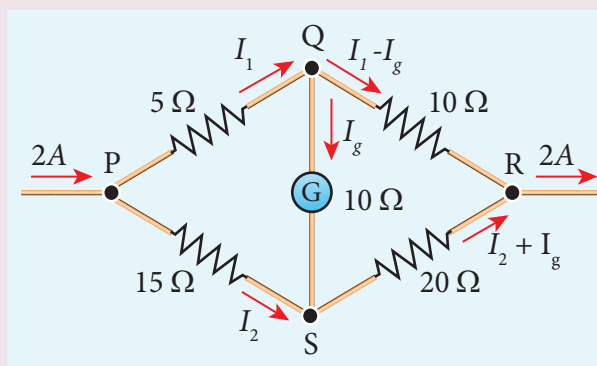12. Determine the current flowing through the galvanometer (G) as shown in the figure.



Ans: $I_g = \frac{1}{11} \text{ A}$

13. Two cells each of 5 V are connected in series across a 8Ω resistor and three parallel resistors of 4Ω , 6Ω and 12Ω . Draw a circuit diagram for the above arrangement. Calculate i) the current drawn from the cell (ii) current through each resistor

Ans: The current at 4Ω , $I = \frac{2}{4} = 0.5 \text{ A}$,

the current at 6Ω , $I = \frac{2}{6} = 0.33 \text{ A}$,


the current at 12Ω , $I = \frac{2}{12} = 0.17 \text{ A}$

14. Four light bulbs P, Q, R, S are connected in a circuit of unknown arrangement. When each bulb is removed one at a time and replaced, the following behavior is observed.

	P	Q	R	S
P removed	*	on	on	on
Q removed	on	*	on	off
R removed	off	off	*	off
S removed	on	off	on	*

Draw the circuit diagram for these bulbs.

Ans:

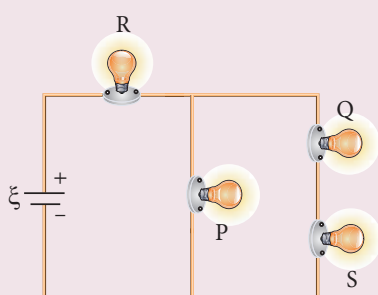

15. In a potentiometer arrangement, a cell of emf 1.25 V gives a balance point at 35 cm length of the wire. If the cell is replaced by another cell and the balance point shifts to 63 cm, what is the emf of the second cell?

Ans: emf of the second cell is 2.25 V

BOOKS FOR REFERENCE:

1. Douglas C. Giancoli, , “*Physics for Scientist & Engineers with Modern Physics*”, Pearson Prentice Hall, Fourth edition
2. James Walker, *Physics*, Pearson- Addison Wesley publishers, Fourth edition
3. Tipler, Mosca, “*Physics for scientist and Engineers with Modern Physics*”, Freeman and Company, sixth edition
4. Purcell, Morin, *Electricity and magnetism*, Cambridge university press, third edition
5. Serway and Jewett, “*Physics for Scientist and Engineers with Modern Physics*”, Brook/Cole publishers, eighth edition
6. Tarasov and Tarasova, “*Questions and problems in School Physics*”, Mir Publishers
7. H.C. Verma, “*Concepts of Physics Vol 2*”, Bharthi Bhawan publishers
8. Eric Roger, *Physics for the Inquiring Mind*, Princeton University press



ICT CORNER

Electric current

In this activity you will be able to

- (a) measure the potential difference of cells
- (b) measure the internal resistance of a given primary cell

Topic: Potentiometer


STEPS:

- Open the browser and type “olabs.edu.in” in the address bar. Click physics tab and then click “Potentiometer-Internal Resistance of a Cell” in class 12 section. Go to “simulator” tab to do the experiment.
- Construct the electric circuit as per the connection diagram by clicking “show circuit diagram” tab. You can connect wires between electric component by dragging the mouse between the component.
- To check whether the connections are correct or not, drag the jockey and place it at the two end points of the wire. If the galvanometer shows opposite deflections, the connections are correct. (keep both keys on)


Step1




Step2

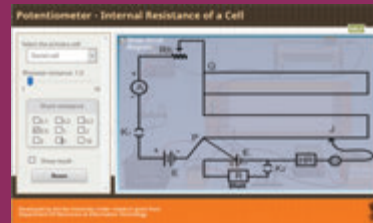

Step3

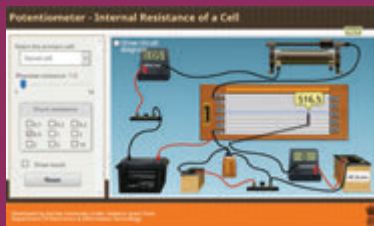

Step4

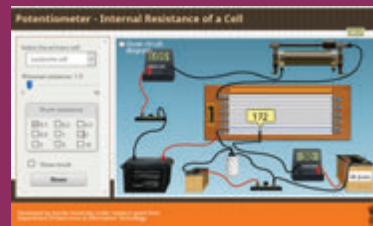

Find the balancing length. Calculate the internal resistance for the observed balancing lengths. Repeat the experiment for five times and take the average.

Note:

1. One time sign up is needed to do simulation. Then login using that username and password.
2. Read theory, procedure and animation to get the theory by clicking the corresponding tab.

URL:

<http://amrita.olabs.edu.in/?sub=1&brch=6&sim=147&cnt=4>

* Pictures are indicative only.

* If browser requires, allow **Flash Player** or **Java Script** to load the page.



B263_12_PHYSICS_EM