

**Q1:** A series AC circuit containing an inductor (20 mH), a capacitor (120 F) and a resistor (60  $\Omega$ ) is driven by an AC source of 24 V/50 Hz. The energy dissipated in the circuit in 60 s is

- (a)  $3.39 \times 10^3$  J
- (b)  $5.65 \times 10^2$  J
- (c)  $2.26 \times 10^3$  J
- (d)  $5.17 \times 10^2$  J

**Solution**

Impedance,

$$Z = (R^2 + (X_C - X_L)^2)^{1/2}$$

$$X_L = \omega L = (2\pi\nu L)$$

$$X_L = 6.28 \times 50 \times 20 \times 10^{-3} = 6.28 \Omega$$

$$X_C = 1/(\omega C) = 1/(2\pi\nu C) = 1/(6.28 \times 120 \times 10^{-6} \times 50) = 26.54 \Omega$$

$$Z = ((60)^2 + (20.26)^2)^{1/2}$$

$$Z^2 = 4010 \Omega^2$$

Average power dissipated,  $P_{av} = \epsilon_{rms} I_{rms} \cos \Phi$

$$P_{av} = \epsilon_{rms} \times (\epsilon_{rms}/Z) \times (R/Z)$$

$$P_{av} = (\epsilon_{rms}^2/Z^2) \times R = [(24)^2/4010] \times 60 \text{ W} = 8.62 \text{ W}$$

Energy dissipated in 60 S =  $8.62 \times 60 = 5.17 \times 10^2$  J

**Answer: (b)  $5.65 \times 10^2$  J**

**Q2:** In an AC generator, a coil with N turns, all of the same area A and total resistance R, rotates with frequency in a magnetic field B. The maximum value of emf generated in the coil is

- (a) NAB
- (b) NABR
- (c) NAB
- (d) NABR

**Answer: (a) In an a.c. generator, maximum emf = NAB**

**Q3:** The phase difference between the alternating current and emf is  $\pi/2$ . Which of the following cannot be the constituent of the circuit?

- (a) LC
- (b) L alone
- (c) C alone

(d) R, L

**Solution**

R and L cause phase difference to lie between 0 and  $\pi/2$  but never 0 and  $\pi/2$  at extremities

**Answer: (d) R, L**

**Q4: Alternating current cannot be measured by D.C ammeter because**

- (a) A.C cannot pass through D.C ammeter
- (b) A.C changes direction
- (c) The average value of current for the complete cycle is zero
- (d) D.C. ammeter will get damaged

**Solution**

The average value of A.C for the complete cycle is zero. Hence A.C cannot be measured by D.C ammeter

**Answer: (c) The average value of current for the complete cycle is zero**

**Q5: A power transmission line feeds input power at 2300 V to a step-down transformer with its primary windings having 4000 turns. The output power is delivered at 230 V by the transformer. If the current in the primary of the transformer is 5 A and its efficiency is 90%, the output current would be**

- (a) 25 A
- (b) 50 A
- (c) 45 A
- (d) 35 A

**Solution**

Given  $\epsilon_p = 2300$  V,  $N_p = 4000$

$\epsilon_s = 230$  V,

$I_p = 5$  A,

$\eta = 90\% = 0.9$

$\eta = P_o/P_i = (\epsilon_s I_s)/(\epsilon_p I_p)$

$I_s = \eta \epsilon_p I_p / \epsilon_s = (0.9 \times 2300 \times 5) / 230 = 45$  A

**Answer: (c) 45 A**

**Q6: An alternating voltage  $v(t) = 220 \sin 100\pi t$  volts is applied to a purely resistive load of 50. The time taken for the current to rise from half of the peak value to the peak value is**

- (a) 3.3 ms
- (b) 5 ms

(c) 2.2 ms

(d) 7.2 ms

### Solution

$$\Delta\Phi = \pi/3 = (100\pi)\Delta t$$

$$\Delta t = (10^3/300) = 3.3 \text{ ms}$$

**Answer: (a) 3.3 ms**

**Q7: A circuit connected to an ac source of emf  $e = e_0 \sin(100 t)$  with  $t$  in seconds, gives a phase difference of  $\pi/4$  between the emf  $e$  and current  $I$ . Which of the following circuits will exhibit this?**

(a) RC circuit with  $R = 1 \text{ k}\Omega$  and  $C = 10\mu\text{F}$

(b) RL circuit with  $R = 1 \text{ k}\Omega$  and  $L = 10\text{mH}$

(c) RC circuit with  $R = 1 \text{ k}\Omega$  and  $C = 1\mu\text{F}$

(d) RL circuit with  $R = 1 \text{ k}\Omega$  and  $L = 1\text{mH}$

### Solution

$$X_c = R$$

$$1/\omega C = R$$

$$1/100 = RC$$

$$R = 10^3 \Omega$$

$$C = 10^{-5} \text{ F}$$

**Answer (a) RC circuit with  $R = 1 \text{ k}\Omega$  and  $C = 10\mu\text{F}$**

**Q8: In an a.c. circuit, the instantaneous e.m.f. and current is given by**

$$e = 100\sin 30t, i = 20\sin(30t - \pi/4)$$

**In one cycle of A.C, the average power consumed by the circuit and the wattless current are, respectively**

(a) 50, 10

(b)  $1000/\sqrt{2}$ , 10

(c)  $50/\sqrt{2}$ , 0

(d) 50, 0

### Solution

$$P_{\text{avg}} = V_{\text{rms}} I_{\text{rms}} \cos\theta$$

$$P_{\text{avg}} = (V_0/\sqrt{2}) (I_0/\sqrt{2}) \cos\theta$$

$$= (100/\sqrt{2}) (20/\sqrt{2}) \cos 45^\circ$$

$$P_{\text{avg}} = 1000/\sqrt{2} \text{ watt}$$

$$\text{Wattless current} = I_{\text{rms}} \sin \theta$$

$$\text{Wattless current} = (I_0/\sqrt{2}) \sin \theta$$

$$= (20/\sqrt{2}) \sin 45^\circ$$

$$= 10 \text{ amp}$$

**Answer: (b)  $1000/\sqrt{2}$  ,10**

**Q9: A coil having  $n$  turns and resistance  $R \Omega$  is connected with a galvanometer of resistance  $4R\Omega$ . This combination is moved in time  $t$  seconds from a magnetic field  $W_1$  weber to  $W_2$  weber. The induced current in the circuit is**

(a)  $-(W_2 - W_1)/5Rnt$

(b)  $-n(W_2 - W_1)/5Rt$

(c)  $-(W_2 - W_1)/Rnt$

(d)  $-(W_2 - W_1)/5Rnt$

### Solution

The emf induced in the coil is  $e = -n(d\Phi/dt)$

$$\text{Induced current, } I = e/R' = -(n/R')(d\Phi/dt) \text{ ———(1)}$$

Given,  $R' = R + 4R = 5R$

$$d\Phi = W_2 - W_1$$

$$dt = t$$

(here,  $W_1$  and  $W_2$  are flux associated with one turn)

Substituting the given values in equa(1) we get

$$I = (-n/5R)(W_2 - W_1/t)$$

**Answer: (b)  $-n(W_2 - W_1)/5Rt$**

**Q10: A series AC circuit containing an inductor (20 mH), a capacitor (120  $\mu$ F) and a resistor (60  $\Omega$ ) is driven by an AC source of 24 V/50 Hz. The energy dissipated in the circuit in 60 s is**

(a)  $5.65 \times 10^2 \text{ J}$

(b)  $2.26 \times 10^3 \text{ J}$

(c)  $5.17 \times 10^2 \text{ J}$

(d)  $3.39 \times 10^3 \text{ J}$

### Solution

Given


$$R = 60\Omega, f = 50 \text{ Hz}, \omega = 2\pi f = 100\pi \text{ and } v = 24\text{v}$$

$$C = 120 \mu\text{F} = 120 \times 10^{-6} \text{ F}$$

$$X_c = 1/\omega C = 1/(100\pi \times 120 \times 10^{-6}) = 26.52 \Omega$$

$$X_L = \omega L = 100\pi \times 120 \times 10^{-3} = 2\pi\Omega$$

$$X_c - X_L = 20.24 \approx 20$$

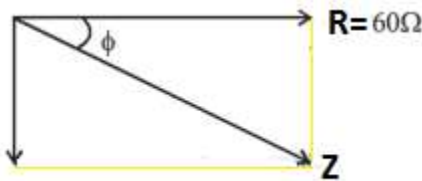

$$Z = [(R^2 + (X_c - X_L)^2)]^{1/2}$$

$$Z = 20\sqrt{10} \Omega$$

$$\cos \Phi = R/Z = 60/20\sqrt{10} = 3/\sqrt{10}$$

$$P_{\text{avg}} = VI \cos \Phi = v/z = (v^2/z) \cos \Phi = 8.64 \text{ watt}$$

Energy dissipated(Q) in time  $t = 60 \text{ s}$  is

$$Q = P \cdot t = 8.64 \times 60 = 5.17 \times 10^2 \text{ J}$$

**Answer: (c)  $5.17 \times 10^2 \text{ J}$**

**Q11: An alternating voltage  $V(t) = 220 \sin 100\pi t$  volts is applied to a purely resistive load of  $50 \Omega$ . The time taken for the current to rise from half of the peak value is**

- (a) 5 ms
- (b) 2.2 ms
- (c) 7.2 ms
- (d) 3.3 ms

### Solution

$$\text{As } v(t) = 220 \sin 100\pi t$$

$$\text{So, } I(t) = (220/50) \sin 100\pi t$$

$$\text{I.e., } I = I_m \sin 100\pi t$$

$$\text{For } I = I_m$$

$$t_1 = (\pi/2) \times (1/100\pi) = (1/200) \text{ sec,}$$

And for  $I = I_m/2$

$$\Rightarrow (I_m/2) = I_m \sin(100\pi t_2)$$

$$\Rightarrow (\pi/6) = 100\pi t_2$$

$$\Rightarrow t_2 = (1/600) \text{ s}$$

$$\therefore t_{\text{req}} = (1/200) - (1/600) = (2/600) = (1/300) \text{ s} = 3.3 \text{ ms}$$

**Answer: (d) 3.3 ms**

**Q12:** An arc lamp requires a direct current of 10A at 80V to function. If it is connected to a 220V (RMS), 50 Hz AC supply, the series inductor needed for it to work is close to

- (a) 0.065 H
- (b) 80 H
- (c) 0.08 H
- (d) 0.044 H

**Solution**

$$I = 10 \text{ A}$$

$$V = 80 \text{ V}$$

$$R = 8 \ \Omega$$

$$10 = 220 / (8^2 + X_L^2)^{1/2}$$

$$64 + X_L^2 = 484$$

$$X_L = \sqrt{420}$$

$$2\pi \times 50L = \sqrt{420}$$

$$L = \sqrt{420} / 100\pi$$

$$L = 0.065 \text{ H}$$

**Answer: (a) 0.065 H**

**Q13:** In a series, LCR circuit  $R = 200\ \Omega$  and the voltage and the frequency of the main supply is 220 V and 50 Hz respectively. On taking out the capacitance from the circuit the current lags behind the voltage by  $30^\circ$ . On taking out the inductor from the circuit the current leads the voltage by  $30^\circ$ . The power dissipated in the LCR circuit is

- (a) 242 W
- (b) 305 W
- (c) 210 W

(d) Zero

**Solution**

$$\tan \Phi = (X_L - X_C)/R$$

$$\tan 30^\circ = X_C/R = X_C = R/\sqrt{3}$$

$$\tan 30^\circ = X_L/R = X_L = R/\sqrt{3}$$

$$X_L = X_C \Rightarrow \text{Condition for resonance}$$

$$\text{So } \Phi = 0^\circ$$

$$P = VI \cos 0^\circ$$

$$P = V^2/R = (220)^2/200 = 242 \text{ W}$$

**Answer: (a) 242 W**

