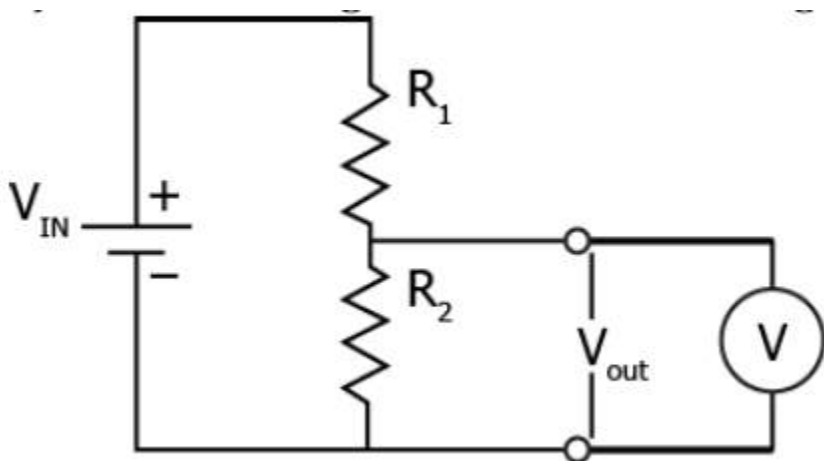


# CBSE Class 10 Science MCQ Chapter 12 Electricity

Q1) The image shows a circuit diagram.



What is being measured using the voltmeter?

- (a) current in the circuit
- (b) voltage in the circuit
- (c) voltage across the resistor
- (d) resistance offered by the resistor

Correct Answer: Option (c)

Q2) The least resistance obtained by using  $2\ \Omega$ ,  $4\ \Omega$ ,  $1\ \Omega$  and  $100\ \Omega$  is

- (a)  $< 100\ \Omega$
- (b)  $< 4\ \Omega$
- (c)  $< 1\ \Omega$
- (d)  $> 2\ \Omega$

Correct Answer: Option (c)

Q3) Work of 14 J is done to move 2 C charge between two points on a conducting wire. What is the potential difference between the two points?

- (a) 28 V
- (b) 14 V
- (c) 7 V
- (d) 3.5 V

Correct Answer: Option (c)

Q4) A fuse wire repeatedly gets burnt when used with a good heater. It is advised to use a fuse wire of

- (a) more length
- (b) less radius
- (c) less length
- (d) more radius

Correct Answer: Option (d)

Q5) A circuit has a charge of 2C moving through it in 3 s. Which electrical component in the circuit, if present, will show the current?

- (a) Voltmeter will show a current of 6 A.
- (b) Ammeter will show a current of 0.7 A.
- (c) Rheostat will show a current of 0.7 A.
- (d) Resistor will show a current of 0.35 A.

Correct Answer: Option (b)

Q6) Electrical resistivity of a given metallic wire depends upon

- (a) its length
- (b) its thickness
- (c) its shape
- (d) nature of the material

Correct Answer: Option (d)

Q7) Two devices are connected between two points, say A and B in parallel. The physical quantity that will remain the same between the two points is

- (a) current
- (b) voltage
- (c) resistance
- (d) None of these

Correct Answer: Option (b)

Q8) Unit of electric power may also be expressed as

- (a) volt ampere
- (b) kilowatt hour
- (c) watt second
- (d) joule second


Correct Answer: Option (b)

Q9) What is the relationship between resistance and current?

- (a) They are directly related to each other.
- (b) They are inversely related to each other.
- (c) The resistance has a greater magnitude than current.
- (d) The current has a greater magnitude than resistance.

Correct Answer: Option (b)

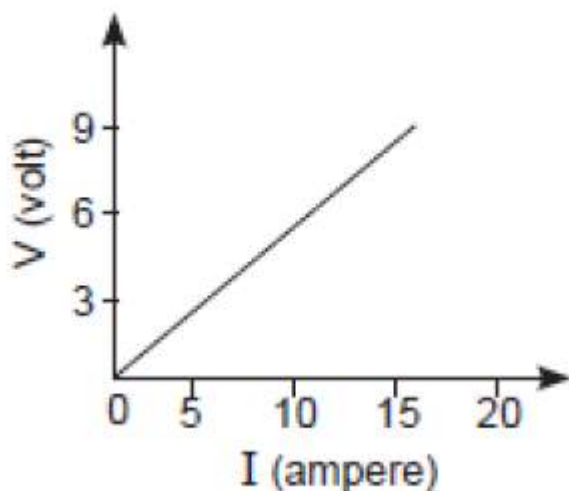Q10) The resistance whose V – I graph is given below is



- (a)  $5/3 \Omega$
- (b)  $3/5 \Omega$
- (c)  $5/2 \Omega$
- (d)  $2/5 \Omega$

Correct Answer: Option (b)

Q11) A current of 1 A is drawn by a filament of an electric bulb. Number of electrons passing through a cross section of the filament in 16 seconds would be roughly

- (a)  $10^{20}$
- (b)  $10^{16}$
- (c)  $10^{18}$
- (d)  $10^{23}$

Correct Answer: Option (a)

Q12) How much more heat is produced, if the current is doubled?

- (a) twice the original amount
- (b) thrice the original amount
- (c) four times the original amount
- (d) five times the original amount

Correct Answer: Option (c)

Q13) Which of the following represents voltage?

- (a) Work done / Current $\times$ Time
- (b) Work done  $\times$  Charge
- (c) Work done $\times$ Time / Current
- (d) Work done  $\times$  Charge  $\times$  Time

Correct Answer: Option (a)

Q14) A cooler of 1500 W, 200 volt and a fan of 500 W, 200 volt are to be used from a household supply. The rating of fuse to be used is

- (a) 2.5 A
- (b) 5.0 A
- (c) 7.5 A
- (d) 10 A

Correct Answer: Option (d)

Q15) Which combination of a  $2\ \Omega$  resistor and  $4\ \Omega$  resistor offers the least resistance to current in the circuit?

- (a) Series combination, which results in a net resistance of  $2\ \Omega$ .
- (b) Parallel combination, which results in a net resistance of  $2\ \Omega$ .
- (c) Series combination, which results in a net resistance of  $1.5\ \Omega$ .
- (d) Parallel combination, which results in a net resistance of  $0.5\ \Omega$ .

Correct Answer: Option (d)

Q16) In an electrical circuit two resistors of  $2\ \Omega$  and  $4\ \Omega$  respectively are connected in series to a  $6\ \text{V}$  battery. The heat dissipated by the  $4\ \Omega$  resistor in  $5\ \text{s}$  will be

- (a)  $5\ \text{J}$
- (b)  $10\ \text{J}$
- (c)  $20\ \text{J}$
- (d)  $30\ \text{J}$

Correct Answer: Option (c)

Q17) In order to reduce electricity consumption at home, what kind of appliance should one purchase?

- (a) one which draws low power
- (b) one which produces less heat
- (c) one which operates at a higher voltage
- (d) one which draws a high amount of current

Correct Answer: Option (a)

Q18) If  $n$  resistors each of resistance  $R$  are connected in parallel combination then their equivalent resistance is

- (a)  $R/n^2$
- (b)  $n^2/R$
- (c)  $n/R$
- (d)  $R/n$

Correct Answer: Option (d)

Q19) Which one among a bar of an alloy of mass 2 kg and a 3 kg iron bar of same dimension has greater resistivity?

- (a) Iron bar because it has higher mass.
- (b) Alloy bar because it has lower mass.
- (c) Iron bar because it has the same types of atoms.
- (d) Alloy bar because it has different types of atoms.

Correct Answer: Option (d)

Q20) Two resistors connected in series gives an equivalent resistance of  $10\ \Omega$ . When connected in parallel, give  $2.4\ \Omega$ . Then the individual resistance are

- (a) each of  $5\ \Omega$
- (b)  $6\ \Omega$  and  $4\ \Omega$
- (c)  $7\ \Omega$  and  $4\ \Omega$
- (d)  $8\ \Omega$  and  $2\ \Omega$

Correct Answer: Option (b)

Q21) A battery of 10 volt carries 20,000 C of charge through a resistance of  $20\ \Omega$ . The work done in 10 seconds is

- (a)  $2 \times 10^3$  joule
- (b)  $2 \times 10^5$  joule
- (c)  $2 \times 10^4$  joule
- (d)  $2 \times 10^2$  joule


Correct Answer: Option (b)

Q22) Two bulbs are rated 40W, 220W and 60W, 220W. The ratio of their resistances will be:

- (a) 4:3
- (b) 3:4
- (c) 2:3
- (d) 3:2

Correct Answer: Option (d)

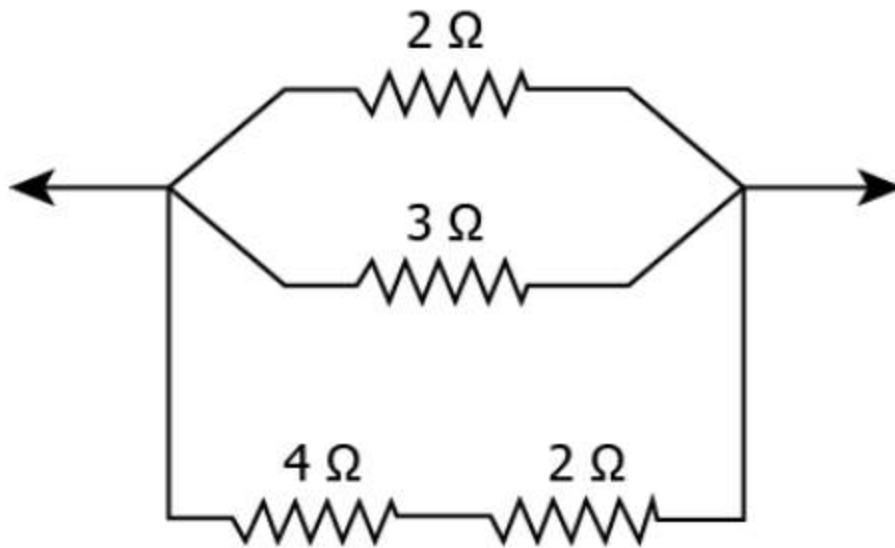Q23) The image shows a combination of 4 resistors.



What is the net resistance between the two points in the circuit?

- (a)  $0.5\ \Omega$
- (b)  $1.0\ \Omega$
- (c)  $1.5\ \Omega$
- (d)  $2.0\ \Omega$

Correct Answer: Option (b)

Q24) If  $R_1$  and  $R_2$  be the resistance of the filament of  $40\ \text{W}$  and  $60\ \text{W}$  respectively operating  $220\ \text{V}$ , then

- (a)  $R_1 < R_2$
- (b)  $R_2 < R_1$
- (c)  $R_1 = R_2$
- (d)  $R_1 \geq R_2$

Correct Answer: Option (b)

Q25) An electric toaster has a power rating of  $200\ \text{W}$ . It operates for  $1$  hour in the morning and  $1$  hour in the evening. How much does it cost to operate the toaster for  $10$  days at  $\text{Rs } 5$  per  $\text{kW h}$ ?

- (a)  $\text{Rs } 20$
- (b)  $\text{Rs } 400$
- (c)  $\text{Rs } 5000$
- (d)  $\text{Rs } 10000$

Correct Answer: Option (a)


Q26) A coil in the heater consumes power  $P$  on passing current. If it is cut into halves and joined in parallel, it will consume power

- (a)  $P$

- (b) P/2
- (c) 2 P
- (d) 4 P

Correct Answer: Option (d)

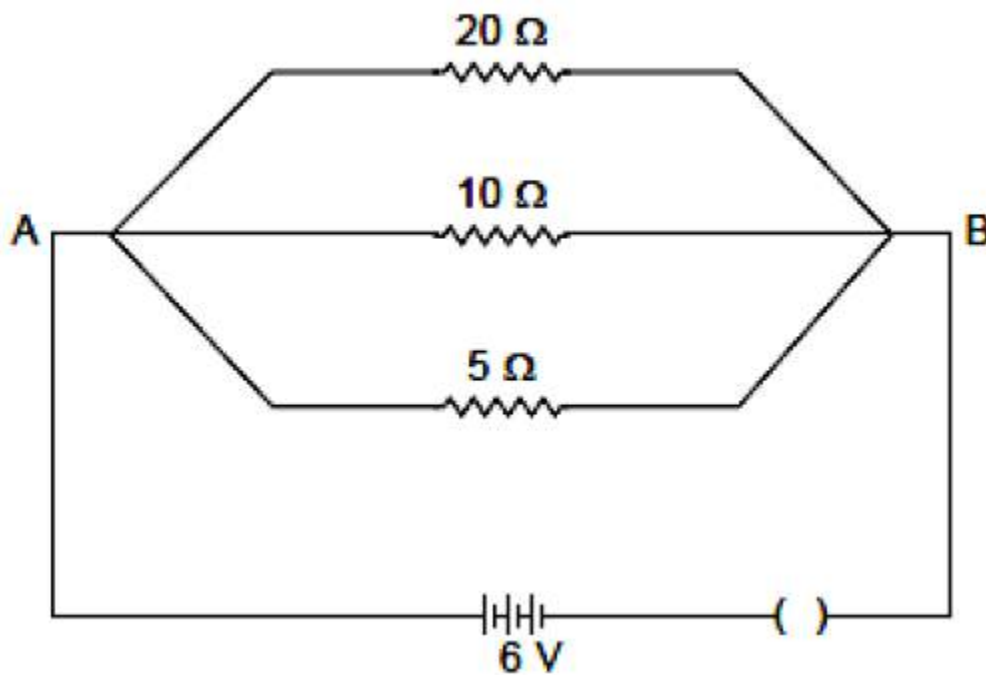
Q27) Calculate the current flow through the  $10\ \Omega$  resistor in the following circuit.



- (a) 1.2 A
- (b) 0.6 A
- (c) 0.2 A
- (d) 2.0 A

Correct Answer: Option (b)

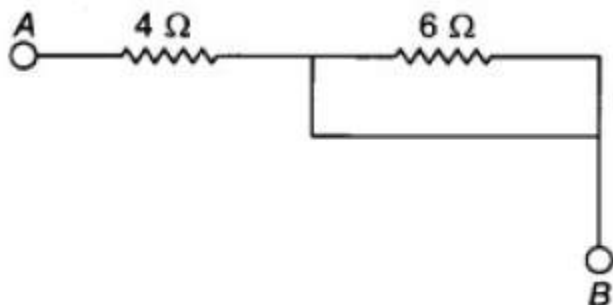Q28) The effective resistance between A and B is



- (a)  $4\ \Omega$



- (b)  $6\Omega$
- (c) May be  $10\Omega$
- (d) Must be  $10\Omega$

Correct Answer: Option (a)

Q29) In this question, the Assertion and Reason have been put forward. Read the statements carefully and choose the correct alternative from the following:

**Assertion:** In an open circuit, the current passes from one terminal of the electric cell to another.

**Reason:** Generally, the metal disc of a cell acts as a positive terminal.

- (a) Both the Assertion and the Reason are correct and the Reason is the correct explanation of the Assertion.
- (b) The Assertion and the Reason are correct but the Reason is not the correct explanation of the Assertion.
- (c) Assertion is true but the Reason is false.
- (d) The statement of the Assertion is false but the Reason is true.

Correct Answer: Option (d)

