

# SESSION - 2



# Graduate Aptitude Test in Engineering

## Notations :

- Options shown in green color and with ✓ icon are correct.
- Options shown in red color and with ✗ icon are incorrect.

**Question Paper Name:** EE: ELECTRICAL ENGINEERING 7th Feb Shift2  
**Number of Questions:** 65  
**Total Marks:** 100.0

Wrong answer for MCQ will result in negative marks, (-1/3) for 1 mark Questions and (-2/3) for 2 marks Questions.

## General Aptitude

Number of Questions: 10  
Section Marks: 15.0

Q.1 to Q.5 carry 1 mark each & Q.6 to Q.10 carry 2 marks each.

### Question Number : 1 Question Type : MCQ

We \_\_\_\_\_ our friend's birthday and we \_\_\_\_\_ how to make it up to him.

- (A) completely forgot --- don't just know
- (B) forgot completely --- don't just know
- (C) completely forgot --- just don't know
- (D) forgot completely --- just don't know

#### Options :

- ✗ A
- ✗ B
- ✓ C
- ✗ D

### Question Number : 2 Question Type : MCQ

Choose the statement where underlined word is used correctly.

- (A) The industrialist had a personnel jet.
- (B) I write my experience in my personnel diary.
- (C) All personnel are being given the day off.
- (D) Being religious is a personnel aspect.

#### Options :

- ✗ A
- ✗ B
- ✓ C
- ✗ D

**Question Number : 3 Question Type : MCQ**

A generic term that includes various items of clothing such as a skirt, a pair of trousers and a shirt is

- (A) fabric (B) textile (C) fibre (D) apparel

Options :

1. ✗ A  
2. ✗ B  
3. ✗ C  
4. ✓ D

**Question Number : 4 Question Type : MCQ**

Based on the given statements, select the most appropriate option to solve the given question.

What will be the total weight of 10 poles each of same weight?

Statements:

- (I) One fourth of the weight of a pole is 5 Kg.  
(II) The total weight of these poles is 160 kg more than the total weight of two poles.

- (A) Statement I alone is not sufficient.  
(B) Statement II alone is not sufficient.  
(C) Either I or II alone is sufficient.  
(D) Both statements I and II together are not sufficient.

Options :

1. ✗ A  
2. ✗ B  
3. ✓ C  
4. ✗ D

**Question Number : 5 Question Type : MCQ**

Consider a function  $f(x) = 1 - |x|$  on  $-1 \leq x \leq 1$ . The value of  $x$  at which the function attains a maximum, and the maximum value of the function are:

- (A) 0, -1 (B) -1, 0 (C) 0, 1 (D) -1, 2

Options :

1. ✗ A  
2. ✗ B  
3. ✓ C  
4. ✗ D

**Question Number : 6 Question Type : MCQ**

Out of the following four sentences, select the most suitable sentence with respect to grammar and usage:


- (A) Since the report lacked needed information, it was of no use to them.  
(B) The report was useless to them because there were no needed information in it.  
(C) Since the report did not contain the needed information, it was not real useful to them.  
(D) Since the report lacked needed information, it would not had been useful to them.

Options :

1. ✓ A
2. ✗ B
3. ✗ C
4. ✗ D

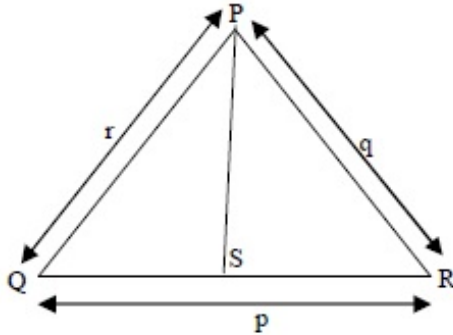Question Number : 7 Question Type : MCQ

In a triangle PQR, PS is the angle bisector of  $\angle QPR$  and  $\angle QPS = 60^\circ$ . What is the length of PS?



- (A)  $\frac{(q+r)}{qr}$
- (B)  $\frac{qr}{(q+r)}$
- (C)  $\sqrt{(q^2 + r^2)}$
- (D)  $\frac{(q+r)^2}{qr}$

Options :

1. ✗ A
2. ✓ B
3. ✗ C
4. ✗ D

Question Number : 8 Question Type : NAT

If  $p, q, r, s$  are distinct integers such that:

$$f(p, q, r, s) = \max(p, q, r, s)$$

$$g(p, q, r, s) = \min(p, q, r, s)$$

$$h(p, q, r, s) = \text{remainder of } (p \times q) / (r \times s) \text{ if } (p \times q) > (r \times s) \text{ or remainder of } (r \times s) / (p \times q) \text{ if } (r \times s) > (p \times q)$$

$$\text{Also a function } fgh(p, q, r, s) = f(p, q, r, s) \times g(p, q, r, s) \times h(p, q, r, s)$$

Also the same operations are valid with two variable functions of the form  $f(p, q)$ .

What is the value of  $fg(h(2,5,7,3), 4,6,8)$ ?

Correct Answers :

8

Question Number : 9 Question Type : MCQ

If the list of letters, P, R, S, T, U is an arithmetic sequence, which of the following are also in arithmetic sequence?

- I.  $2P, 2R, 2S, 2T, 2U$
- II.  $P-3, R-3, S-3, T-3, U-3$
- III.  $P^2, R^2, S^2, T^2, U^2$

- (A) I only
- (B) I and II
- (C) II and III
- (D) I and III

Options :

- 1. ✖ A
- 2. ✔ B
- 3. ✖ C
- 4. ✖ D

Question Number : 10 Question Type : MCQ

Four branches of a company are located at M, N, O, and P. M is north of N at a distance of 4 km; P is south of O at a distance of 2 km; N is southeast of O by 1 km. What is the distance between M and P in km?

- (A) 5.34
- (B) 6.74
- (C) 28.5
- (D) 45.49

Options :

- 1. ✔ A
- 2. ✖ B
- 3. ✖ C
- 4. ✖ D

Electrical Engineering

Number of Questions:	55
Section Marks:	85.0

Q.11 to Q.35 carry 1 mark each & Q.36 to Q.65 carry 2 marks each.

Question Number : 11 Question Type : MCQ

Given  $f(z) = g(z) + h(z)$ , where  $f, g, h$  are complex valued functions of a complex variable  $z$ . Which one of the following statements is TRUE?

- (A) If  $f(z)$  is differentiable at  $z_0$ , then  $g(z)$  and  $h(z)$  are also differentiable at  $z_0$ .
- (B) If  $g(z)$  and  $h(z)$  are differentiable at  $z_0$ , then  $f(z)$  is also differentiable at  $z_0$ .
- (C) If  $f(z)$  is continuous at  $z_0$ , then it is differentiable at  $z_0$ .
- (D) If  $f(z)$  is differentiable at  $z_0$ , then so are its real and imaginary parts.

Options :

- 1. ✖ A
- 2. ✔ B
- 3. ✖ C
- 4. ✖ D



Question Number : 12 Question Type : MCQ

We have a set of 3 linear equations in 3 unknowns. ' $X \equiv Y$ ' means  $X$  and  $Y$  are equivalent statements and ' $X \not\equiv Y$ ' means  $X$  and  $Y$  are not equivalent statements.

P: There is a unique solution.

Q: The equations are linearly independent.

R: All eigenvalues of the coefficient matrix are nonzero.

S: The determinant of the coefficient matrix is nonzero.

Which one of the following is TRUE?

(A)  $P \equiv Q \equiv R \equiv S$

(B)  $P \equiv R \not\equiv Q \equiv S$

(C)  $P \equiv Q \not\equiv R \equiv S$

(D)  $P \not\equiv Q \not\equiv R \not\equiv S$

Options :

1. ☒ A

2. ☐ B

3. ☐ C

4. ☐ D

Question Number : 13 Question Type : MCQ

Match the following.

P. Stokes's Theorem

Q. Gauss's Theorem

R. Divergence Theorem

S. Cauchy's Integral Theorem

1.  $\oint \mathbf{D} \cdot d\mathbf{s} = Q$

2.  $\oint f(z) dz = 0$

3.  $\iiint (\nabla \cdot \mathbf{A}) dv = \oint \mathbf{A} \cdot d\mathbf{s}$

4.  $\iint (\nabla \times \mathbf{A}) \cdot d\mathbf{s} = \oint \mathbf{A} \cdot d\mathbf{l}$

(A)

P-2

Q-1

R-4

S-3

(B)

P-4

Q-1

R-3

S-2

(C)

P-4

Q-3

R-1

S-2

(D)

P-3

Q-4

R-2

S-1

Options :

1. ☐ A

2. ☒ B

3. ☐ C

4. ☐ D

Question Number : 14 Question Type : MCQ

The Laplace transform of  $f(t) = 2\sqrt{t/\pi}$  is  $s^{-3/2}$ . The Laplace transform of  $g(t) = \sqrt{1/\pi t}$  is

(A)  $3s^{-5/2}/2$

(B)  $s^{-1/2}$

(C)  $s^{1/2}$

(D)  $s^{3/2}$

Options :

1. ☐ A

2. ☒ B

3. ☐ C

4. ✖ D

Question Number : 15 Question Type : MCQ

Match the following.

**Instrument Type**

- P. Permanent magnet moving coil  
Q. Moving iron connected through current transformer  
R. Rectifier  
S. Electrodynamometer

**Used for**

1. DC Only  
2. AC Only  
3. AC and DC

(A)	(B)	(C)	(D)
P-1	P-1	P-1	P-3
Q-2	Q-3	Q-2	Q-1
R-1	R-1	R-3	R-2
S-3	S-2	S-3	S-1

Options :

1. ✖ A  
2. ✖ B  
3. ✔ C  
4. ✖ D

Question Number : 16 Question Type : MCQ

A 3-phase balanced load which has a power factor of 0.707 is connected to a balanced supply. The power consumed by the load is 5 kW. The power is measured by the two-wattmeter method. The readings of the two wattmeters are


- (A) 3.94 kW and 1.06 kW  
(B) 2.50 kW and 2.50 kW  
(C) 5.00 kW and 0.00 kW  
(D) 2.96 kW and 2.04 kW

Options :

1. ✔ A  
2. ✖ B  
3. ✖ C  
4. ✖ D

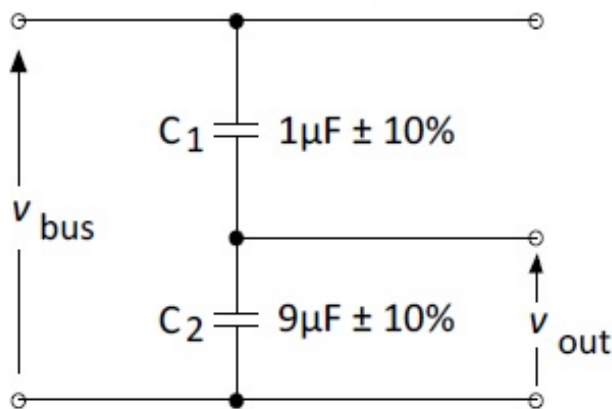Question Number : 17 Question Type : NAT

A capacitive voltage divider is used to measure the bus voltage  $V_{bus}$  in a high-voltage 50 Hz AC system as shown in the figure. The measurement capacitors  $C_1$  and  $C_2$  have tolerances of  $\pm 10\%$  on their nominal capacitance values. If the bus voltage  $V_{bus}$  is 100 kV rms, the maximum rms output voltage  $V_{out}$  (in kV), considering the capacitor tolerances, is \_\_\_\_\_.




Correct Answer :

11.75 to 12.25

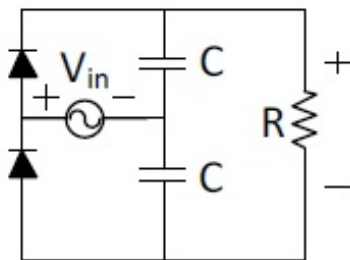Question Number : 18 Question Type : MCQ

In the following circuit, the input voltage  $V_{in}$  is  $100 \sin(100\pi t)$ . For  $100\pi RC = 50$ , the average voltage across  $R$  (in Volts) under steady-state is nearest to



- (A) 100                      (B) 31.8                      (C) 200                      (D) 63.6

Options :

1. ✗ A
2. ✗ B
3. ✓ C
4. ✗ D

Question Number : 19 Question Type : MCQ

Two semi-infinite dielectric regions are separated by a plane boundary at  $y = 0$ . The dielectric constants of region 1 ( $y < 0$ ) and region 2 ( $y > 0$ ) are 2 and 5, respectively. Region 1 has uniform electric field  $\vec{E} = 3\hat{a}_x + 4\hat{a}_y + 2\hat{a}_z$ , where  $\hat{a}_x$ ,  $\hat{a}_y$ , and  $\hat{a}_z$  are unit vectors along the  $x$ ,  $y$  and  $z$  axes, respectively. The electric field in region 2 is

- (A)  $3\hat{a}_x + 1.6\hat{a}_y + 2\hat{a}_z$                       (B)  $1.2\hat{a}_x + 4\hat{a}_y + 2\hat{a}_z$   
 (C)  $1.2\hat{a}_x + 4\hat{a}_y + 0.8\hat{a}_z$                       (D)  $3\hat{a}_x + 10\hat{a}_y + 0.8\hat{a}_z$

Options :


1. ✓ A



2. ✖ B
3. ✖ C
4. ✖ D

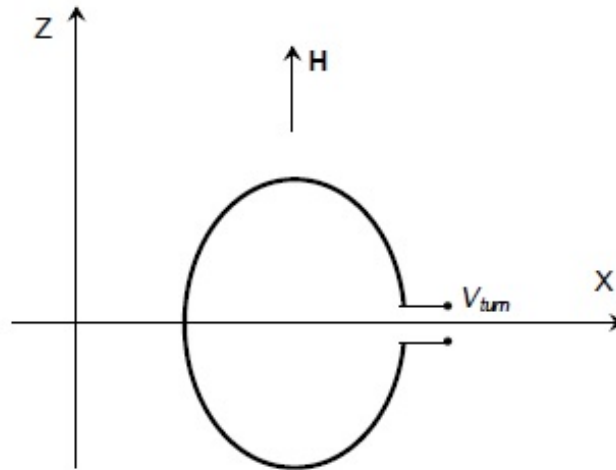Question Number : 20 Question Type : NAT

A circular turn of radius 1 m revolves at 60 rpm about its diameter aligned with the x-axis as shown in the figure. The value of  $\mu_0$  is  $4\pi \times 10^{-7}$  in SI unit. If a uniform magnetic field intensity  $\vec{H} = 10^7 \hat{z}$  A/m is applied, then the peak value of the induced voltage,  $V_{\text{turn}}$  (in Volts), is \_\_\_\_\_.




Correct Answer :

246 to 250

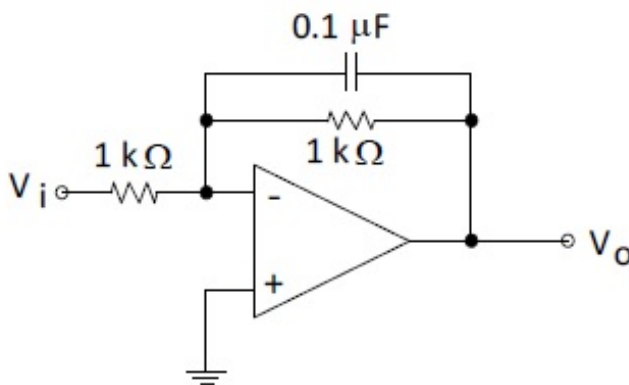Question Number : 21 Question Type : NAT

The operational amplifier shown in the figure is ideal. The input voltage (in Volt) is  $V_i = 2 \sin(2\pi \times 2000t)$ . The amplitude of the output voltage  $V_o$  (in Volt) is \_\_\_\_\_.




Correct Answer:

1.1 to 1.4

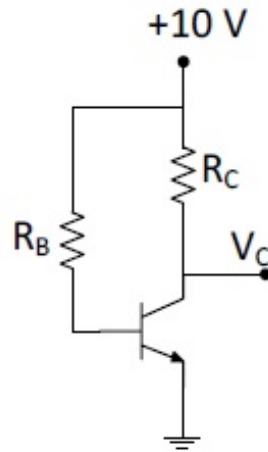Question Number : 22 Question Type : NAT

In the following circuit, the transistor is in active mode and  $V_C = 2\text{ V}$ . To get  $V_C = 4\text{ V}$ , we replace  $R_C$  with  $R'_C$ . Then the ratio  $R'_C/R_C$  is \_\_\_\_\_.



Correct Answer:

0.74 to 0.76

Question Number : 23 Question Type : MCQ

Consider the following Sum of Products expression,  $F$ .

$$F = ABC + \bar{A}\bar{B}C + A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}\bar{C}$$

The equivalent Product of Sums expression is


- (A)  $F = (A + \bar{B} + C)(\bar{A} + B + C)(\bar{A} + \bar{B} + C)$
- (B)  $F = (A + \bar{B} + \bar{C})(A + B + C)(\bar{A} + \bar{B} + \bar{C})$
- (C)  $F = (\bar{A} + B + \bar{C})(A + \bar{B} + \bar{C})(A + B + C)$
- (D)  $F = (\bar{A} + \bar{B} + C)(A + B + \bar{C})(A + B + C)$

Options :

- 1. ✓ A
- 2. ✗ B
- 3. ✗ C
- 4. ✗ D

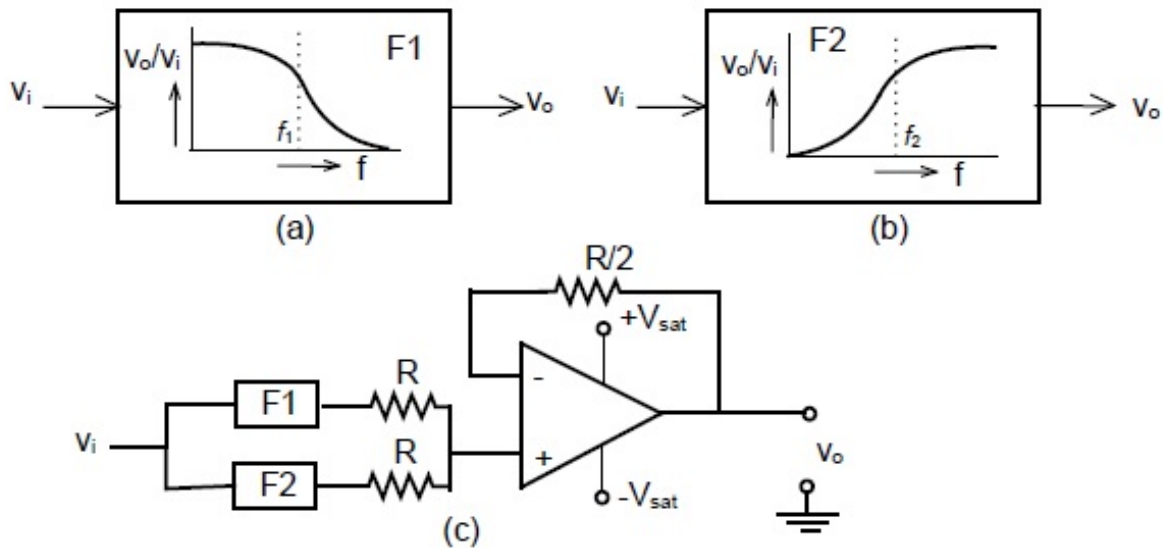Question Number : 24 Question Type : MCQ

The filters F1 and F2 having characteristics as shown in Figures (a) and (b) are connected as shown in Figure (c).



The cut-off frequencies of F1 and F2 are  $f_1$  and  $f_2$  respectively. If  $f_1 < f_2$ , the resultant circuit exhibits the characteristic of a

- (A) Band-pass filter  
(B) Band-stop filter  
(C) All pass filter  
(D) High-Q filter

Options :

1. ✗ A  
2. ✓ B  
3. ✗ C  
4. ✗ D

Question Number : 25 Question Type : MCQ

When a bipolar junction transistor is operating in the saturation mode, which one of the following statements is TRUE about the state of its collector-base (CB) and the base-emitter (BE) junctions?


- (A) The CB junction is forward biased and the BE junction is reverse biased.  
(B) The CB junction is reverse biased and the BE junction is forward biased.  
(C) Both the CB and BE junctions are forward biased.  
(D) Both the CB and BE junctions are reverse biased.

Options :


1. ✗ A  
2. ✗ B  
3. ✓ C  
4. ✗ D

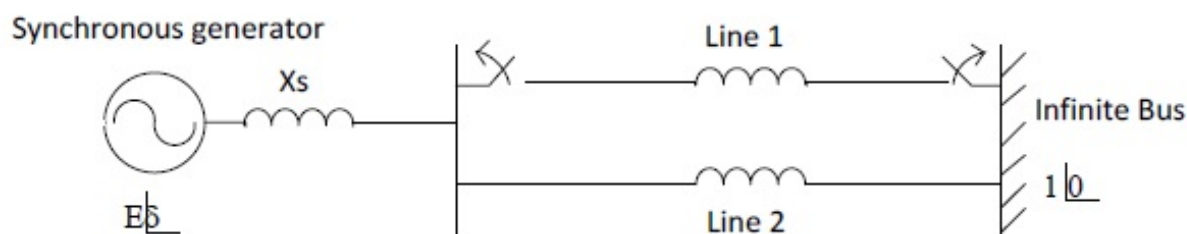Question Number : 26 Question Type : MCQ


The synchronous generator shown in the figure is supplying active power to an infinite bus via two short, lossless transmission lines, and is initially in steady state. The mechanical power input to the generator and the voltage magnitude  $E$  are constant. If one line is tripped at time  $t_1$  by opening the circuit breakers at the two ends (although there is no fault), then it is seen that the generator undergoes a stable transient. Which one of the following waveforms of the rotor angle  $\delta$  shows the transient correctly?




(A)

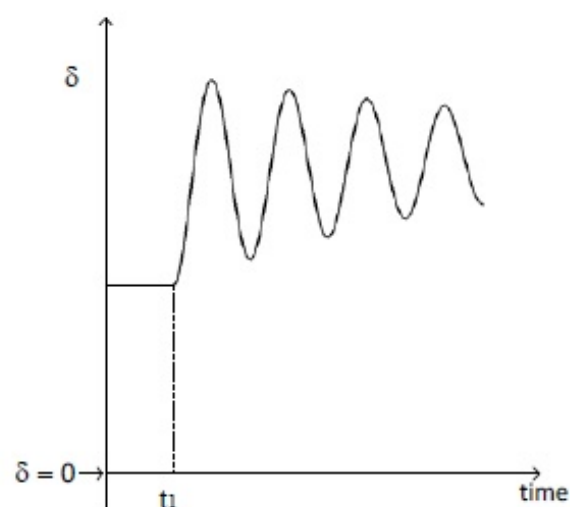


(B)

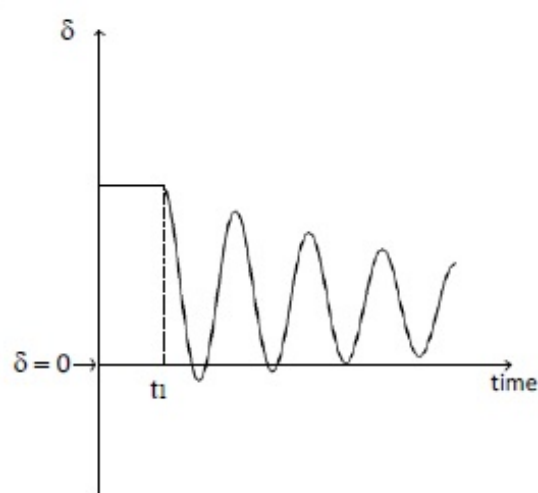

(C)

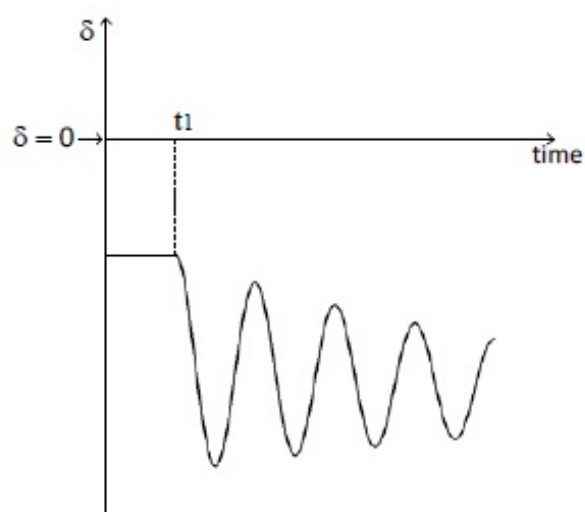

(D)

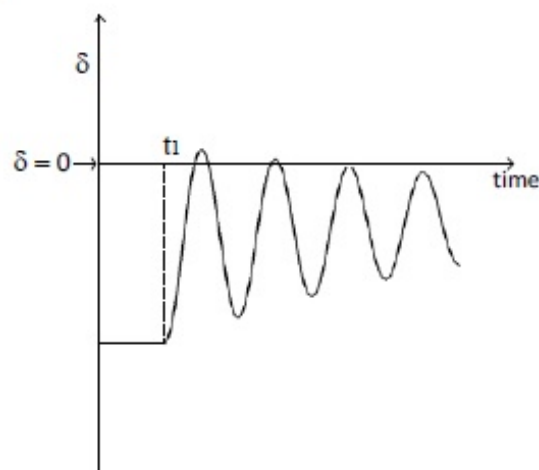

Options :

1. ✓ A
2. ✗ B
3. ✗ C
4. ✗ D

Question Number : 27 Question Type : MCQ

A 3-bus power system network consists of 3 transmission lines. The bus admittance matrix of the uncompensated system is

$$\begin{bmatrix} -j6 & j3 & j4 \\ j3 & -j7 & j5 \\ j4 & j5 & -j8 \end{bmatrix} \text{ pu.}$$

If the shunt capacitance of all transmission lines is 50% compensated, the imaginary part of the 3<sup>rd</sup> row 3<sup>rd</sup> column element (in pu) of the bus admittance matrix after compensation is


- (A)  $-j7.0$  (B)  $-j8.5$  (C)  $-j7.5$  (D)  $-j9.0$

Options :

1. ✗ A  
2. ✓ B  
3. ✗ C  
4. ✗ D

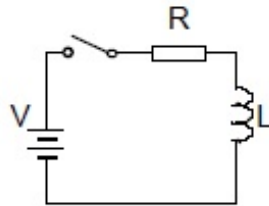Question Number : 28 Question Type : MCQ

A series RL circuit is excited at  $t = 0$  by closing a switch as shown in the figure. Assuming zero initial conditions, the value of  $\frac{d^2i}{dt^2}$  at  $t = 0^+$  is




- (A)  $\frac{V}{L}$  (B)  $\frac{-V}{R}$  (C) 0 (D)  $\frac{-RV}{L^2}$

Options :

1. ✗ A  
2. ✗ B  
3. ✗ C  
4. ✓ D

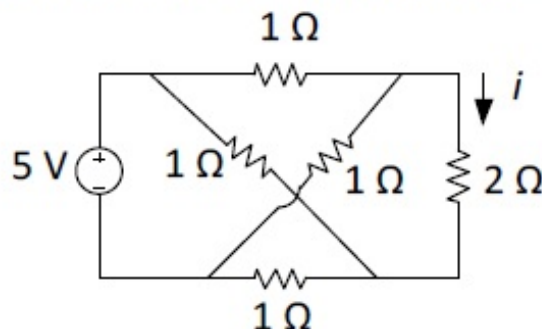Question Number : 29 Question Type : NAT

The current  $i$  (in Ampere) in the  $2\ \Omega$  resistor of the given network is \_\_\_\_\_.






Correct Answer :

0

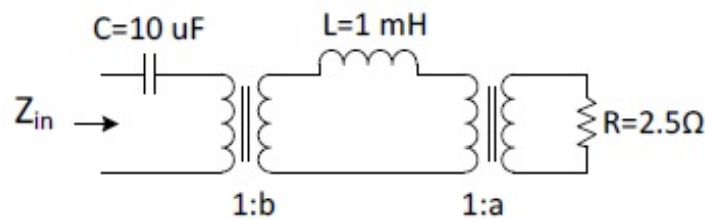Question Number : 30 Question Type : MCQ

Find the transformer ratios  $a$  and  $b$  such that the impedance ( $Z_{in}$ ) is resistive and equals  $2.5 \Omega$  when the network is excited with a sine wave voltage of angular frequency of  $5000 \text{ rad/s}$ .



(A)  $a = 0.5, b = 2.0$

(B)  $a = 2.0, b = 0.5$

(C)  $a = 1.0, b = 1.0$

(D)  $a = 4.0, b = 0.5$

Options :

1. ✗ A

2. ✓ B

3. ✗ C

4. ✗ D

Question Number : 31 Question Type : NAT


A shunt-connected DC motor operates at its rated terminal voltage. Its no-load speed is  $200 \text{ radian/second}$ . At its rated torque of  $500 \text{ Nm}$ , its speed is  $180 \text{ radian/second}$ . The motor is used to directly drive a load whose load torque  $T_L$  depends on its rotational speed  $\omega_r$  (in  $\text{radian/second}$ ), such that  $T_L = 2.78 \times \omega_r$ . Neglecting rotational losses, the steady-state speed (in  $\text{radian/second}$ ) of the motor, when it drives this load, is \_\_\_\_\_.

Correct Answer :

177 to 183

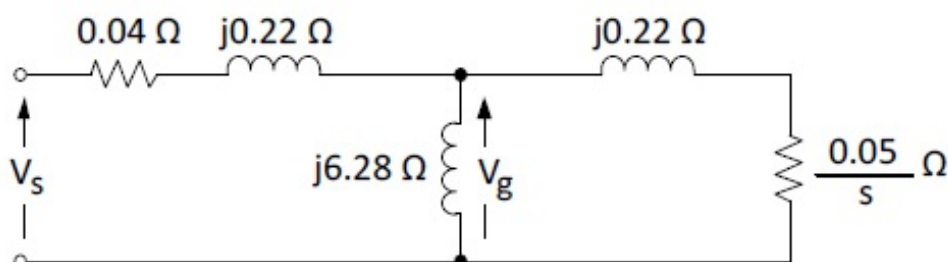Question Number : 32 Question Type : NAT

The figure shows the per-phase equivalent circuit of a two-pole three-phase induction motor operating at  $50 \text{ Hz}$ . The “air-gap” voltage,  $V_g$  across the magnetizing inductance, is  $210 \text{ V rms}$ , and the slip,  $s$ , is  $0.05$ . The torque (in  $\text{Nm}$ ) produced by the motor is \_\_\_\_\_.



**Correct Answer :**

400 to 403

**Question Number : 33 Question Type : MCQ**

A 4-pole, separately excited, wave wound DC machine with negligible armature resistance is rated for 230 V and 5 kW at a speed of 1200 rpm. If the same armature coils are reconnected to form a lap winding, what is the rated voltage (in volts) and power (in kW) respectively at 1200 rpm of the reconnected machine if the field circuit is left unchanged ?

- (A) 230 and 5                      (B) 115 and 5                      (C) 115 and 2.5                      (D) 230 and 2.5

**Options :**

1. ✖ A

2. ✔ B

3. ✖ C

4. ✖ D

**Question Number : 34 Question Type : NAT**



An open loop control system results in a response of  $e^{-2t}(\sin 5t + \cos 5t)$  for a unit impulse input. The DC gain of the control system is \_\_\_\_\_.

**Correct Answer :**

0.23 to 0.25

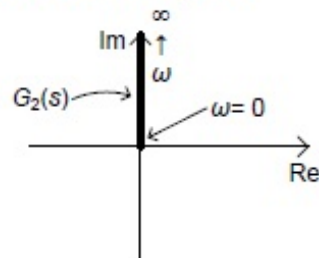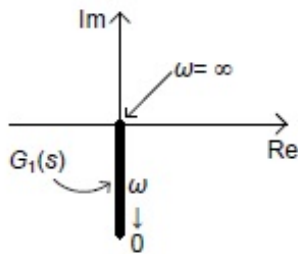
**Question Number : 35 Question Type : MCQ**

Nyquist plots of two functions  $G_1(s)$  and  $G_2(s)$  are shown in figure.




Nyquist plot of the product of  $G_1(s)$  and  $G_2(s)$  is


(A)

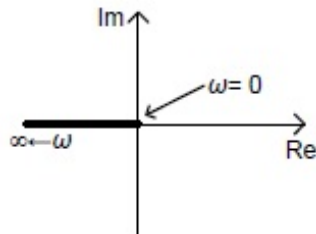


(B)

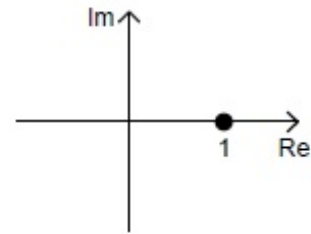

(C)

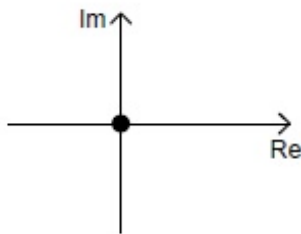

(D)

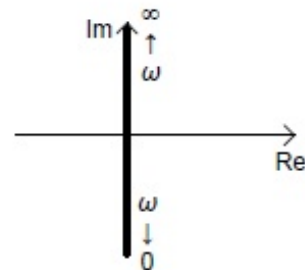

Options :

1. ✗ A

2. ✓ B

3. ✗ C

4. ✗ D

Question Number : 36 Question Type : NAT

The volume enclosed by the surface  $f(x, y) = e^x$  over the triangle bounded by the lines  $x = y$ ;  $x = 0$ ;  $y = 1$  in the  $xy$  plane is \_\_\_\_\_.

Correct Answer :

0.70 to 0.76

Question Number : 37 Question Type : MCQ

Two coins R and S are tossed. The 4 joint events  $H_R H_S, T_R T_S, H_R T_S, T_R H_S$  have probabilities 0.28, 0.18, 0.30, 0.24, respectively, where  $H$  represents head and  $T$  represents tail. Which one of the following is TRUE?

- (A) The coin tosses are independent.
- (B) R is fair, S is not.
- (C) S is fair, R is not.
- (D) The coin tosses are dependent.

Options :

- 1. ✖ A
- 2. ✖ B
- 3. ✖ C
- 4. ✔ D

Question Number : 38 Question Type : NAT

A differential equation  $\frac{di}{dt} - 0.2i = 0$  is applicable over  $-10 < t < 10$ . If  $i(4) = 10$ , then  $i(-5)$  is \_\_\_\_\_.

Correct Answer :

1.6 to 1.7

Question Number : 39 Question Type : MCQ

Consider a signal defined by

$$x(t) = \begin{cases} e^{j10t} & \text{for } |t| \leq 1 \\ 0 & \text{for } |t| > 1 \end{cases}$$

Its Fourier Transform is


- |   |   |
|---|---|
| (A) $\frac{2 \sin(\omega - 10)}{\omega - 10}$ | (B) $2 e^{j10} \frac{\sin(\omega - 10)}{\omega - 10}$ |
| (C) $\frac{2 \sin \omega}{\omega - 10}$       | (D) $e^{j10\omega} \frac{2 \sin \omega}{\omega}$      |

Options :

- 1. ✔ A
- 2. ✖ B
- 3. ✖ C
- 4. ✖ D

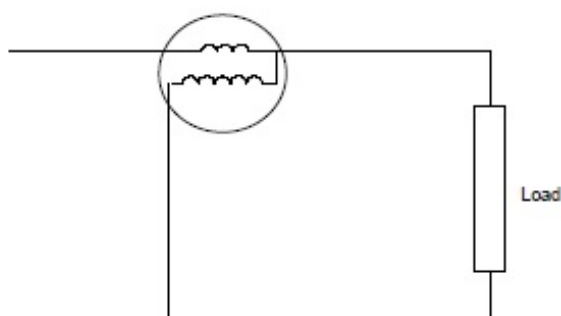Question Number : 40 Question Type : NAT

The coils of a wattmeter have resistances  $0.01\ \Omega$  and  $1000\ \Omega$ ; their inductances may be neglected. The wattmeter is connected as shown in the figure, to measure the power consumed by a load, which draws  $25\text{ A}$  at power factor  $0.8$ . The voltage across the load terminals is  $30\text{ V}$ . The percentage error on the wattmeter reading is \_\_\_\_\_.




Correct Answer :

0.14 to 0.16

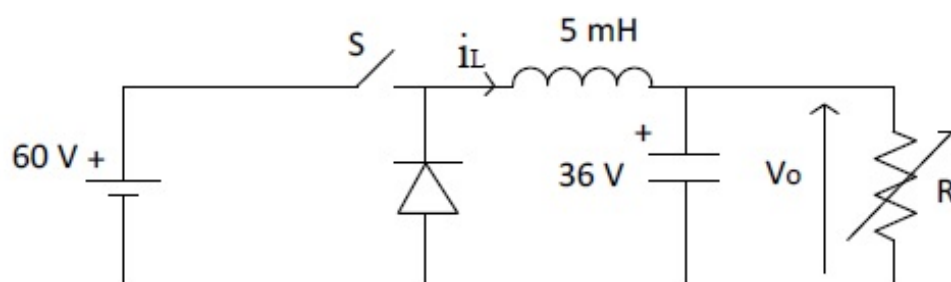Question Number : 41 Question Type : NAT

A buck converter feeding a variable resistive load is shown in the figure. The switching frequency of the switch  $S$  is  $100\text{ kHz}$  and the duty ratio is  $0.6$ . The output voltage  $V_o$  is  $36\text{ V}$ . Assume that all the components are ideal, and that the output voltage is ripple-free. The value of  $R$  (in Ohm) that will make the inductor current ( $i_L$ ) just continuous is \_\_\_\_\_.




Correct Answer :

2480 to 2520

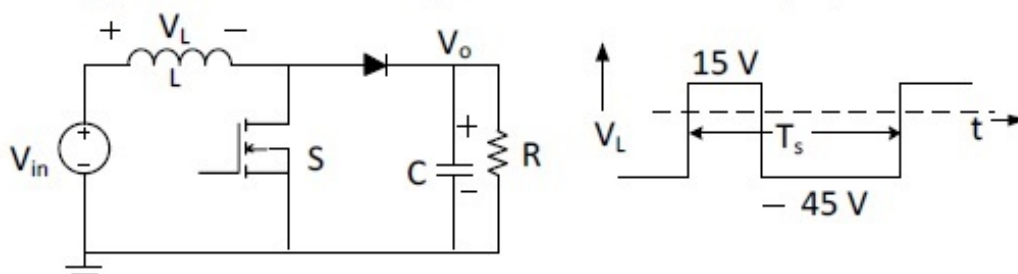Question Number : 42 Question Type : NAT

For the switching converter shown in the following figure, assume steady-state operation. Also assume that the components are ideal, the inductor current is always positive and continuous and switching period is  $T_s$ . If the voltage  $V_L$  is as shown, the duty cycle of the switch  $S$  is \_\_\_\_\_.






Correct Answer :

0.75

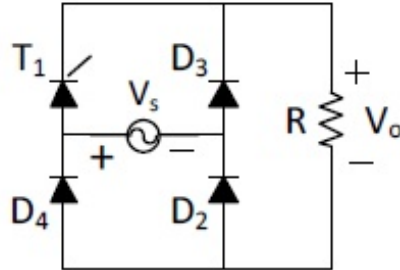Question Number : 43 Question Type : NAT

In the given rectifier, the delay angle of the thyristor  $T_1$  measured from the positive going zero crossing of  $V_s$  is  $30^\circ$ . If the input voltage  $V_s$  is  $100 \sin(100\pi t)$  V, the average voltage across R (in Volt) under steady-state is \_\_\_\_\_.



Correct Answer:

61 to 62

Question Number : 44 Question Type : MCQ

For linear time invariant systems, that are Bounded Input Bounded Output stable, which one of the following statements is TRUE?

- (A) The impulse response will be integrable, but may not be absolutely integrable.
- (B) The unit impulse response will have finite support.
- (C) The unit step response will be absolutely integrable.
- (D) The unit step response will be bounded.

Options :

- 1. ✗ A
- 2. ✗ B
- 3. ✗ C
- 4. ✓ D

Question Number : 45 Question Type : MCQ

The z-Transform of a sequence  $x[n]$  is given as  $X(z) = 2z + 4 - 4/z + 3/z^2$ . If  $y[n]$  is the first difference of  $x[n]$ , then  $Y(z)$  is given by

- (A)  $2z + 2 - 8/z + 7/z^2 - 3/z^3$
- (B)  $-2z + 2 - 6/z + 1/z^2 - 3/z^3$
- (C)  $-2z - 2 + 8/z - 7/z^2 + 3/z^3$
- (D)  $4z - 2 - 8/z - 1/z^2 + 3/z^3$

Options :


- 1. ✓ A
- 2. ✗ B

3. ✖ C

4. ✖ D

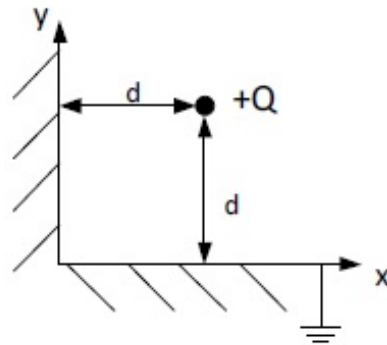Question Number : 46 Question Type : MCQ

Two semi-infinite conducting sheets are placed at right angles to each other as shown in the figure. A point charge of  $+Q$  is placed at a distance of  $d$  from both sheets. The net force on the charge is  $\frac{Q^2}{4\pi\epsilon_0} \frac{K}{d^2}$ , where  $K$  is given by



- (A) 0 (B)  $-\frac{1}{4} \hat{i} - \frac{1}{4} \hat{j}$  (C)  $-\frac{1}{8} \hat{i} - \frac{1}{8} \hat{j}$  (D)  $\frac{1-2\sqrt{2}}{8\sqrt{2}} \hat{i} + \frac{1-2\sqrt{2}}{8\sqrt{2}} \hat{j}$

Options :

1. ✖ A


2. ✖ B

3. ✖ C

4. ✔ D

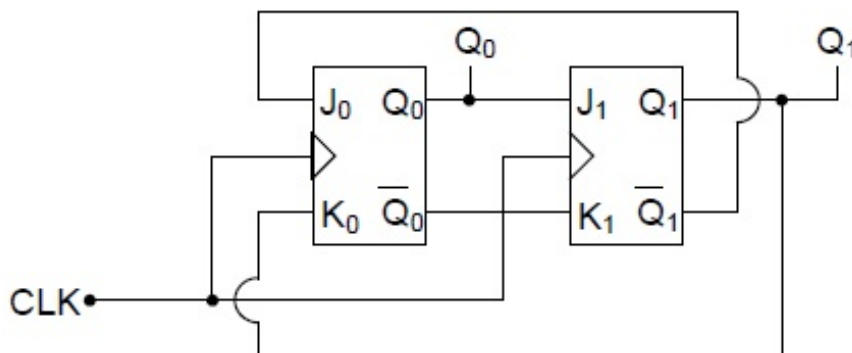Question Number : 47 Question Type : MCQ

In the following sequential circuit, the initial state (before the first clock pulse) of the circuit is  $Q_1 Q_0 = 00$ . The state  $(Q_1 Q_0)$ , immediately after the 333<sup>rd</sup> clock pulse is



- (A) 00 (B) 01 (C) 10 (D) 11

Options :

1. ✖ A


2. ✔ B

3. ✖ C

4. ✖ D

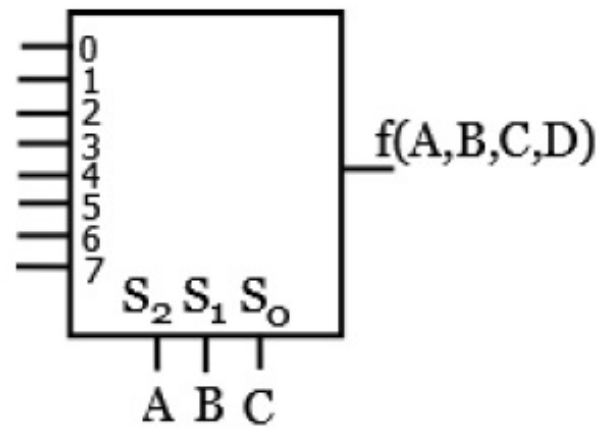Question Number : 48 Question Type : MCQ

A Boolean function  $f(A, B, C, D) = \prod(1,5,12,15)$  is to be implemented using an  $8 \times 1$  multiplexer (A is MSB). The inputs ABC are connected to the select inputs  $S_2 S_1 S_0$  of the multiplexer respectively.



Which one of the following options gives the correct inputs to pins 0,1,2,3,4,5,6,7 in order?


- (A)  $D, 0, D, 0, 0, 0, \bar{D}, D$
- (B)  $\bar{D}, 1, \bar{D}, 1, 1, 1, D, \bar{D}$
- (C)  $D, 1, D, 1, 1, 1, \bar{D}, D$
- (D)  $\bar{D}, 0, \bar{D}, 0, 0, 0, D, \bar{D}$

Options :

- 1. ✗ A
- 2. ✓ B
- 3. ✗ C
- 4. ✗ D

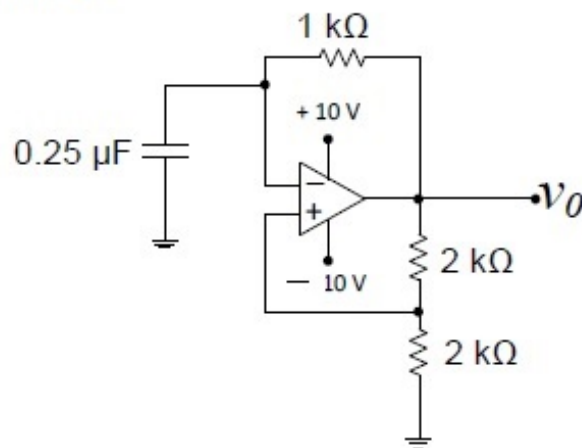Question Number : 49 Question Type : MCQ

The saturation voltage of the ideal op-amp shown below is  $\pm 10$  V. The output voltage  $v_o$  of the following circuit in the steady-state is



- (A) square wave of period 0.55 ms.
- (B) triangular wave of period 0.55 ms.
- (C) square wave of period 0.25 ms.
- (D) triangular wave of period 0.25 ms.

Options :

- 1. ✓ A
- 2. ✗ B
- 3. ✗ C
- 4. ✗ D

Question Number : 50 Question Type : NAT

The incremental costs (in Rupees/MWh) of operating two generating units are functions of their respective powers  $P_1$  and  $P_2$  in MW, and are given by

$$\frac{dC_1}{dP_1} = 0.2P_1 + 50$$

$$\frac{dC_2}{dP_2} = 0.24P_2 + 40$$

where

$$20 \text{ MW} \leq P_1 \leq 150 \text{ MW}$$

$$20 \text{ MW} \leq P_2 \leq 150 \text{ MW}.$$


For a certain load demand,  $P_1$  and  $P_2$  have been chosen such that  $dC_1/dP_1 = 76$  Rs/MWh and  $dC_2/dP_2 = 68.8$  Rs/MWh. If the generations are rescheduled to minimize the total cost, then  $P_2$  is \_\_\_\_\_.

**Correct Answer:**

135 to 137

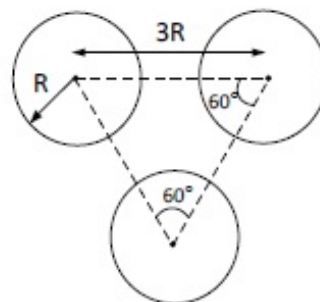**Question Number : 51 Question Type : NAT**

A composite conductor consists of three conductors of radius  $R$  each. The conductors are arranged as shown below. The geometric mean radius (GMR) (in cm) of the composite conductor is  $kR$ . The value of  $k$  is \_\_\_\_\_.




**Correct Answer:**

1.85 to 1.95

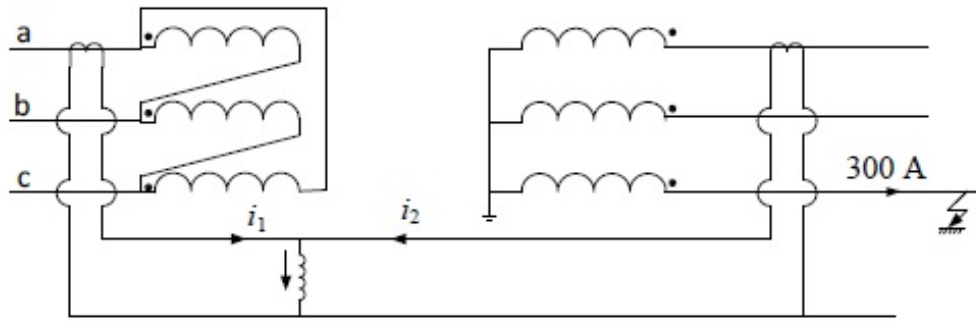**Question Number : 52 Question Type : MCQ**



A 3-phase transformer rated for 33 kV/11 kV is connected in delta/star as shown in figure. The current transformers (CTs) on low and high voltage sides have a ratio of 500/5. Find the currents  $i_1$  and  $i_2$ , if the fault current is 300 A as shown in figure.



(A)  $i_1 = 1/\sqrt{3} \text{ A}, i_2 = 0 \text{ A}$

(B)  $i_1 = 0 \text{ A}, i_2 = 0 \text{ A}$

(C)  $i_1 = 0 \text{ A}, i_2 = 1/\sqrt{3} \text{ A}$


(D)  $i_1 = 1/\sqrt{3} \text{ A}, i_2 = 1/\sqrt{3} \text{ A}$

Options :

1. ✓ A
2. ✗ B
3. ✗ C
4. ✗ D

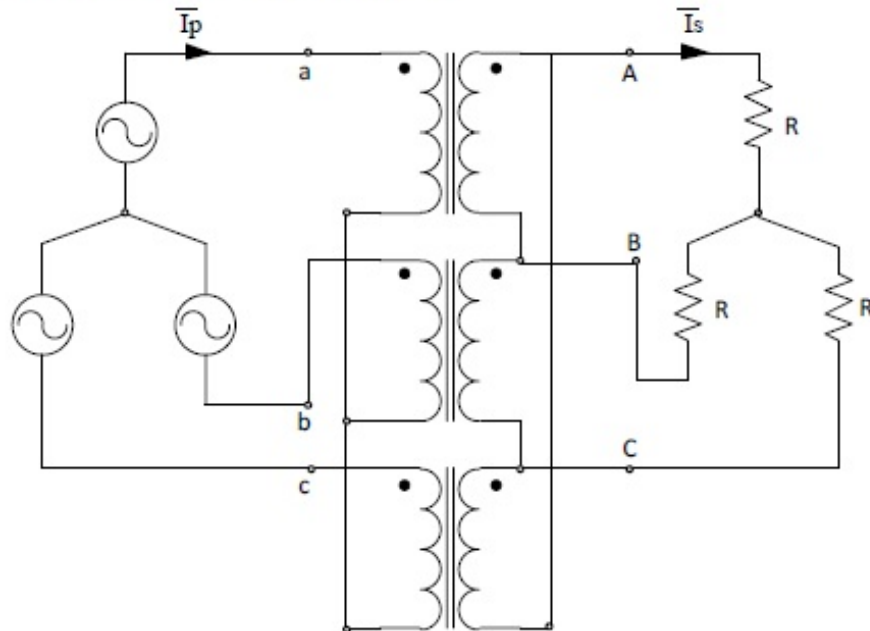Question Number : 53 Question Type : MCQ

A balanced (positive sequence) three-phase AC voltage source is connected to a balanced, star connected load through a star-delta transformer as shown in the figure. The line-to-line voltage rating is 230 V on the star side, and 115 V on the delta side. If the magnetizing current is neglected and  $\bar{I}_s = 100 \angle 0^\circ \text{ A}$ , then what is the value of  $\bar{I}_p$  in Ampere?



(A)  $50 \angle 30^\circ$

(B)  $50 \angle -30^\circ$

(C)  $50 \sqrt{3} \angle 30^\circ$

(D)  $200 \angle 30^\circ$

Options :


1. ✓ A



2. ✖ B
3. ✖ C
4. ✖ D

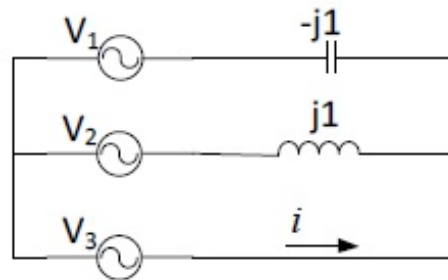Question Number : 54 Question Type : MCQ

In the given network  $V_1 = 100 \angle 0^\circ \text{ V}$ ,  $V_2 = 100 \angle -120^\circ \text{ V}$ ,  $V_3 = 100 \angle +120^\circ \text{ V}$ . The phasor current  $i$  (in Ampere) is




- (A)  $173.2 \angle -60^\circ$       (B)  $173.2 \angle 120^\circ$       (C)  $100.0 \angle -60^\circ$       (D)  $100.0 \angle 120^\circ$

Options :

1. ✔ A
2. ✖ B
3. ✖ C
4. ✖ D

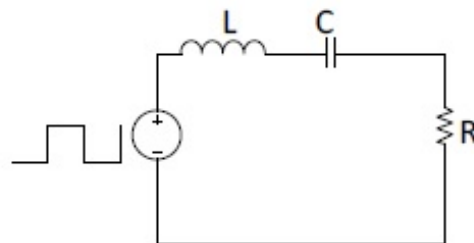Question Number : 55 Question Type : NAT

A symmetrical square wave of 50% duty cycle has amplitude of  $\pm 15 \text{ V}$  and time period of  $0.4\pi \text{ ms}$ . This square wave is applied across a series RLC circuit with  $R = 5 \Omega$ ,  $L = 10 \text{ mH}$ , and  $C = 4 \mu\text{F}$ . The amplitude of the  $5000 \text{ rad/s}$  component of the capacitor voltage (in Volt) is \_\_\_\_\_.



Correct Answer:

190 to 192

Question Number : 56 Question Type : NAT


Two identical coils each having inductance  $L$  are placed together on the same core. If an overall inductance of  $\alpha L$  is obtained by interconnecting these two coils, the minimum value of  $\alpha$  is \_\_\_\_\_.

Correct Answer :

0

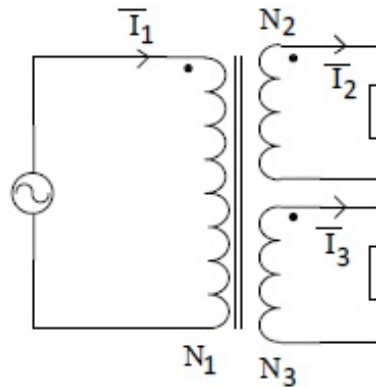Question Number : 57 Question Type : MCQ

A three-winding transformer is connected to an AC voltage source as shown in the figure. The number of turns are as follows:  $N_1 = 100$ ,  $N_2 = 50$ ,  $N_3 = 50$ . If the magnetizing current is neglected, and the currents in two windings are  $\bar{I}_2 = 2 \angle 30^\circ \text{ A}$  and  $\bar{I}_3 = 2 \angle 150^\circ \text{ A}$ , then what is the value of the current  $\bar{I}_1$  in Ampere?



- (A)  $1 \angle 90^\circ$  (B)  $1 \angle 270^\circ$  (C)  $4 \angle 90^\circ$  (D)  $4 \angle 270^\circ$

Options :

1. ✓ A
2. ✗ B
3. ✗ C
4. ✗ D

Question Number : 58 Question Type : NAT

With an armature voltage of 100 V and rated field winding voltage, the speed of a separately excited DC motor driving a fan is 1000 rpm, and its armature current is 10 A. The armature resistance is  $1 \Omega$ . The load torque of the fan load is proportional to the square of the rotor speed. Neglecting rotational losses, the value of the armature voltage (in Volt) which will reduce the rotor speed to 500 rpm is \_\_\_\_\_.

Correct Answer:

47.5

Question Number : 59 Question Type : NAT

A three-phase, 11 kV, 50 Hz, 2 pole, star connected, cylindrical rotor synchronous motor is connected to an 11 kV, 50 Hz source. Its synchronous reactance is  $50 \Omega$  per phase, and its stator resistance is negligible. The motor has a constant field excitation. At a particular load torque, its stator current is 100 A at unity power factor. If the load torque is increased so that the stator current is 120 A, then the load angle (in degrees) at this load is \_\_\_\_\_.

Correct Answer :

-48 to -46

Question Number : 60 Question Type : NAT


A 220 V, 3-phase, 4-pole, 50 Hz inductor motor of wound rotor type is supplied at rated voltage and frequency. The stator resistance, magnetizing reactance, and core loss are negligible. The maximum torque produced by the rotor is 225 % of full load torque and it occurs at 15% slip. The actual rotor resistance is  $0.03 \Omega/\text{phase}$ . The value of external resistance (in Ohm) which must be inserted in a rotor phase if the maximum torque is to occur at start is \_\_\_\_\_.

Correct Answer:

0.16 to 0.18

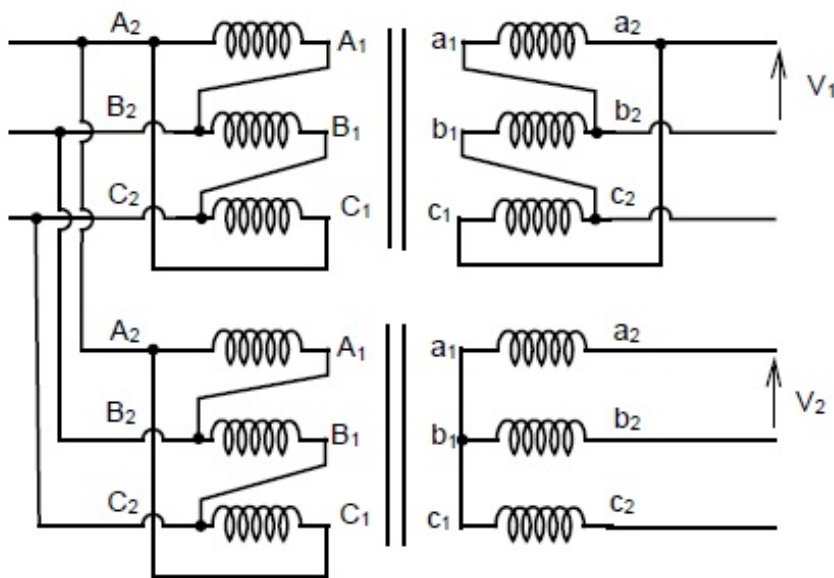Question Number : 61 Question Type : NAT

Two three-phase transformers are realized using single-phase transformers as shown in the figure.



The phase difference (in degree) between voltages  $V_1$  and  $V_2$  is \_\_\_\_\_.

Correct Answer :

30

Question Number : 62 Question Type : MCQ

The following discrete-time equations result from the numerical integration of the differential equations of an un-damped simple harmonic oscillator with state variables  $x$  and  $y$ . The integration time step is  $h$ .

$$\frac{x_{k+1} - x_k}{h} = y_k$$

$$\frac{y_{k+1} - y_k}{h} = -x_k$$

For this discrete-time system, which one of the following statements is TRUE?

- (A) The system is not stable for  $h > 0$
- (B) The system is stable for  $h > \frac{1}{\pi}$
- (C) The system is stable for  $0 < h < \frac{1}{2\pi}$
- (D) The system is stable for  $\frac{1}{2\pi} < h < \frac{1}{\pi}$


Options :

- 1. ✓ A
- 2. ✗ B
- 3. ✗ C
- 4. ✗ D


Question Number : 63 Question Type : MCQ

The unit step response of a system with the transfer function  $G(s) = \frac{1-2s}{1+s}$  is given by which one of the following waveforms?


(A)

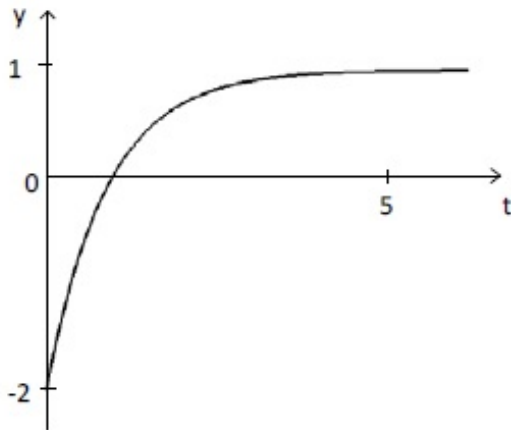


(B)

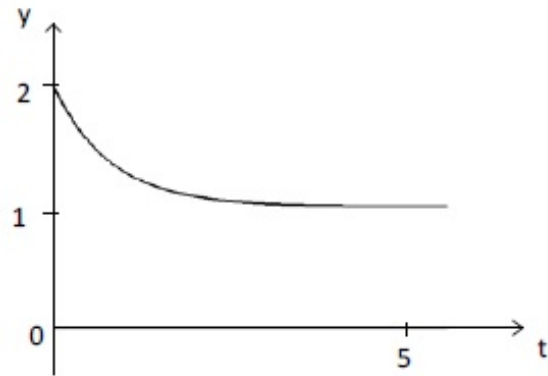

(C)

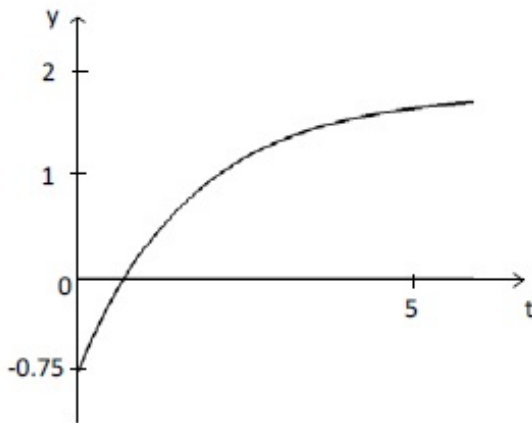

(D)

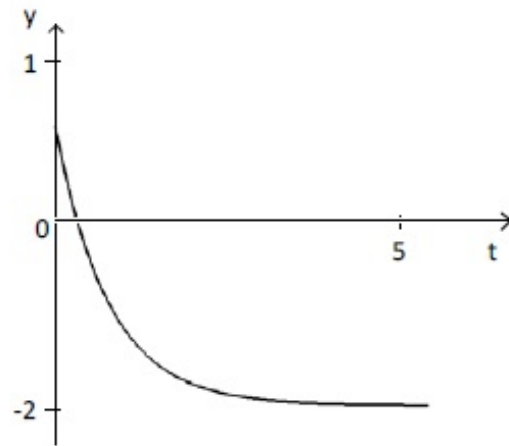

Options :

1. ✓ A
2. ✗ B
3. ✗ C
4. ✗ D

Question Number : 64 Question Type : MCQ

An open loop transfer function  $G(s)$  of a system is

$$G(s) = \frac{K}{s(s+1)(s+2)}$$

For a unity feedback system, the breakaway point of the root loci on the real axis occurs at,

- |                         |                       |
|-------------------------|-----------------------|
| (A) $-0.42$             | (B) $-1.58$           |
| (C) $-0.42$ and $-1.58$ | (D) none of the above |

Options :

1. ✓ A
2. ✗ B
3. ✗ C
4. ✗ D



Question Number : 65 Question Type : MCQ

For the system governed by the set of equations:

$$dx_1/dt = 2x_1 + x_2 + u$$

$$dx_2/dt = -2x_1 + u$$

$$y = 3x_1$$

the transfer function  $Y(s)/U(s)$  is given by

(A)  $3(s+1)/(s^2 - 2s + 2)$

(B)  $3(2s+1)/(s^2 - 2s + 1)$

(C)  $(s+1)/(s^2 - 2s + 1)$

(D)  $3(2s+1)/(s^2 - 2s + 2)$

Options :

1. ✓ A

2. ✗ B

3. ✗ C

4. ✗ D

