

BYJU'S Study Planner for Board Term I (CBSE Grade 12)

Date: 11/11/2021

Subject: Physics

Topic : Current Electricity

Class: Standard XII


-
1. A current of 5 A is passing through a metallic wire of cross sectional area $14 \times 10^{-6} \text{ m}^2$. If the density of the charge carries in the wire is $5 \times 10^{26} \text{ C/m}^3$, the drift speed of the electrons.

 - A. $3.46 \times 10^{-3} \text{ ms}^{-1}$
 - B. $4.46 \times 10^{-3} \text{ ms}^{-1}$
 - C. $5.46 \times 10^{-3} \text{ ms}^{-1}$
 - D. $6.46 \times 10^{-3} \text{ ms}^{-1}$
 2. A hollow cylinder of length 3 m has inner and outer diameters of 4 mm and 8 mm respectively. The resistance of the cylinder is (specific resistance of the material = $2.2 \times 10^{-8} \Omega\text{m}$)


 - A. $1.75 \times 10^{-3} \Omega$
 - B. $1.25 \times 10^{-3} \Omega$
 - C. $1.5 \times 10^{-3} \Omega$
 - D. $1.95 \times 10^{-3} \Omega$

BYJU'S Study Planner for Board Term I (CBSE Grade 12)

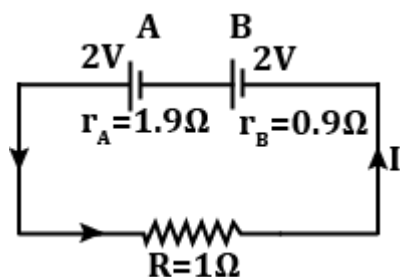3. Two cells A and B each of 2 V are connected in series to an external resistance $R = 1\ \Omega$ as shown in figure. If the internal resistance of A is $r_A = 1.9\ \Omega$ and that of B is $r_B = 0.9\ \Omega$, then the potential difference between the terminals of A is



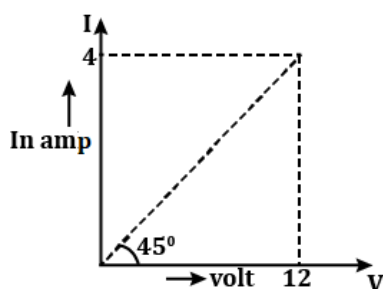
- A. 1.75 V
- B. 1.5 V
- C. 1.25 V
- D. zero
4. The variation of current and voltage in a conductor has been shown in figure. The conductance of the conductor is (Give your answer in Ω^{-1}).



- A. $\frac{1}{2}$
- B. $\frac{1}{5}$
- C. $\frac{1}{3}$
- D. $\frac{1}{4}$

BYJU'S Study Planner for Board Term I (CBSE Grade 12)

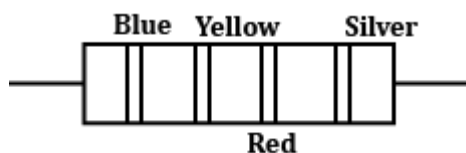
5. The resistance of a metal wire is 10Ω . A current of 30 mA is flowing in it at 20°C . If the potential difference across its ends is constant and its increased to 120°C , then the current flowing in the wire will be in (mA) (temperature coefficient of resistance is $5 \times 10^{-3} \text{ }^\circ\text{C}^{-1}$).
- A. 10
- B. 15
- C. 20
- D. 40
6. In an experiment with potentiometer, to measure the internal resistance of a cell. When it is shunted by 5Ω the null point obtained is at 2 m from one end. When cell is shunted by 20Ω , the null point is obtained at 3 m from the same end. The internal resistance of cell is
- A. 8Ω
- B. 6Ω
- C. 4Ω
- D. 2Ω
7. The colour coding on a resistor from the left are blue, yellow, red and silver as shown in figure. The value of resistance is



- A. $6400\Omega \pm 20$
- B. $6400\Omega \pm 10$
- C. $4600\Omega \pm 10$
- D. $6400\Omega \pm 5$

BYJU'S Study Planner for Board Term I (CBSE Grade 12)

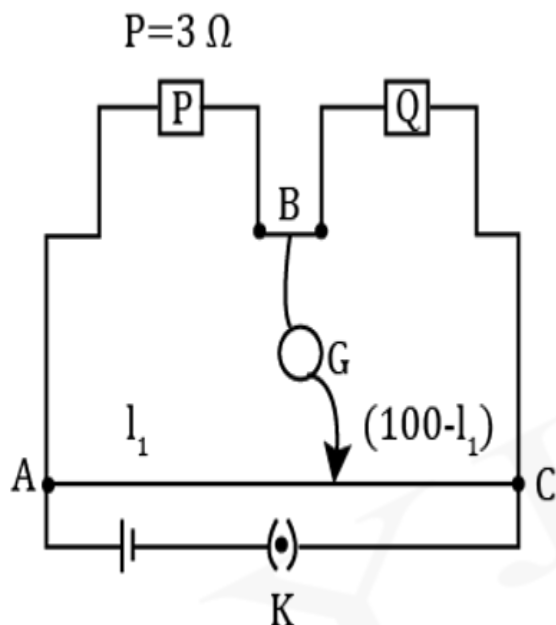
8. In a meter bridge experiment, resistances are connected as shown in figure. The balancing length l_1 is 55 cm. Now an unknown resistance x is connected in series with P and the new balancing length is found to be 75 cm. The value of x is



- A. $\frac{54}{13}\ \Omega$
 B. $\frac{20}{11}\ \Omega$
 C. $\frac{48}{11}\ \Omega$
 D. $\frac{11}{48}\ \Omega$

BYJU'S Study Planner for Board Term I (CBSE Grade 12)

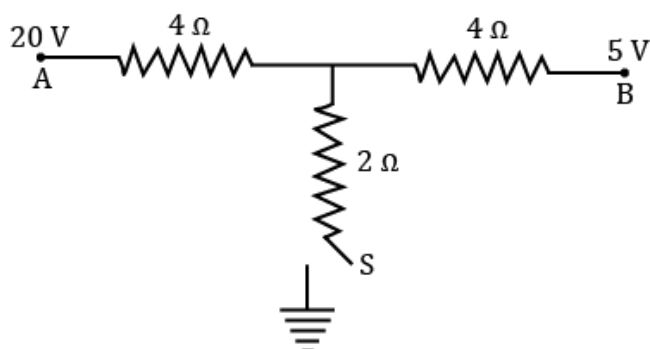9. As the switch S is closed in the circuit shown in figure, current passing through it will be



- A. 4.5 A
 - B. 6.0 A
 - C. $8/25$ A
 - D. $25/8$ A
10. Resistance of a wire is 8Ω . It is stretched in such a way that it experiences a longitudinal strain of 400%. The new resistance is
- A. 400Ω
 - B. 300Ω
 - C. 200Ω
 - D. 100Ω

BYJU'S Study Planner for Board Term I (CBSE Grade 12)

11. In the question given below, a statement of Assertion (A) is given followed by a corresponding statement of Reason (R) just below it. Of the statements mark the correct answer.

Assertion (A): Potentiometer is much better than a voltmeter for measuring emf of cell.

Reason (R): A potentiometer draws no current while measuring emf of a cell.

- A. Both 'A' and 'R' are true and 'R' is the correct explanation of 'A'.
 - B. Both 'A' and 'R' are true and 'R' is not the correct explanation of 'A'
 - C. 'A' is true and 'R' is false
 - D. 'A' is false and 'R' is true
12. In the question given below, a statement of Assertion (A) is given followed by a corresponding statement of Reason (R) just below it. Of the statements mark the correct answer.

Assertion (A): In meterbridge experiment a high resistance is connected in series with the galvanometer.

Reason (R): As resistance increases, current through the circuit increases.

- A. Both 'A' and 'R' are true and 'R' is the correct explanation of 'A'.
- B. Both 'A' and 'R' are true and 'R' is not the correct explanation of 'A'
- C. 'A' is true and 'R' is false
- D. 'A' is false and 'R' is true

BYJU'S Study Planner for Board Term I (CBSE Grade 12)

13. In the question given below, a statement of Assertion (A) is given followed by a corresponding statement of Reason (R) just below it. Of the statements mark the correct answer.

Assertion (A): Terminal voltage of a cell is greater than emf of the cell, during charging of the cell.

Reason (R): The emf of a cell is always greater than its terminal voltage.

- A. Both 'A' and 'R' are true and 'R' is the correct explanation of 'A'.
 - B. Both 'A' and 'R' are true and 'R' is not the correct explanation of 'A'
 - C. 'A' is true and 'R' is false
 - D. 'A' is false and 'R' is true
14. In the question given below, a statement of Assertion (A) is given followed by a corresponding statement of Reason (R) just below it. Of the statements mark the correct answer.

Assertion (A): At any junction of a network , the algebraic sum of various currents is zero.

Reason (R): At steady state , there is no accumulation of charges at the junction.

- A. Both 'A' and 'R' are true and 'R' is the correct explanation of 'A'.
- B. Both 'A' and 'R' are true and 'R' is not the correct explanation of 'A'
- C. 'A' is true and 'R' is false
- D. 'A' is false and 'R' is true

BYJU'S Study Planner for Board Term I (CBSE Grade 12)


15. Assertion (*A*): A piece of copper and other of germanium are cooled from room temperature to 100 K. Conductivity of copper increases and that of germanium decreases.

Reason (*R*): Copper has positive temperature coefficient where as germamium has negative temperature coefficient.

Study both the statements carefully and then

Select your answers, according to the codes given below

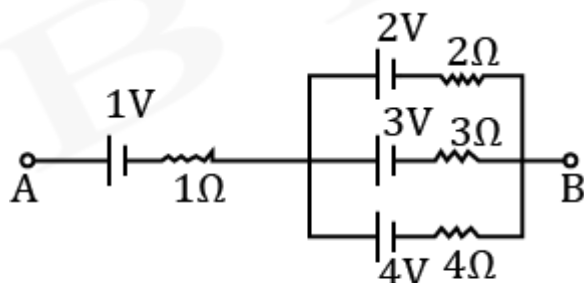- A.** Both *A* and *R* are true and *R* is the correct explanation of *A*.
 - B.** Both *A* and *R* are true and *R* is not the correct explanation of *A*
 - C.** *A* is true and *R* is false
 - D.** *A* is false and *R* is true
16. The circuit given below consists of cells with their internal resistance,




- (i) The equivalent emf between the terminals *A* and *B* is

- A.** $\frac{24}{13}$ V
- B.** $\frac{37}{13}$ V
- C.** $\frac{36}{13}$ V
- D.** $\frac{49}{13}$ V

BYJU'S Study Planner for Board Term I (CBSE Grade 12)

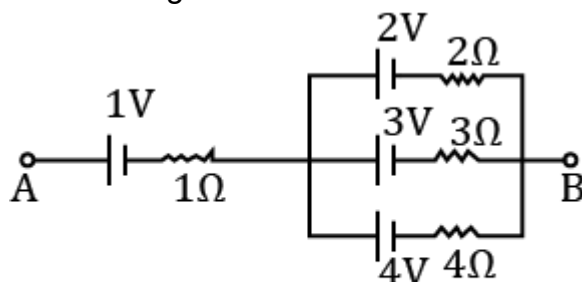
17. The circuit given below consists of cells with their internal resistance



- (ii) The equivalent internal resistance of the combination is

- A. $\frac{24}{13} \Omega$
- B. $\frac{13}{24} \Omega$
- C. $\frac{25}{13} \Omega$
- D. $\frac{13}{12} \Omega$

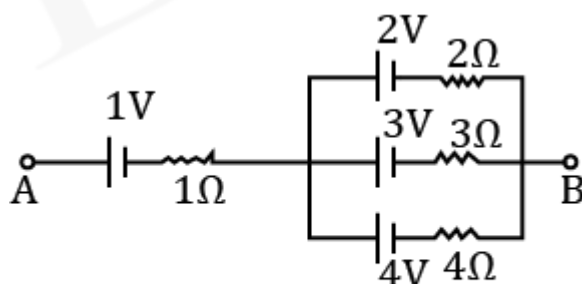18. The circuit given below consists of cells with their internal resistance




- (iii) If the polarity of cell of 4 V is reversed, the equivalent emf between the terminals A and B is

- A. $\frac{1}{13} \text{ V}$
- B. $\frac{37}{13} \text{ V}$
- C. $\frac{25}{13} \text{ V}$
- D. $\frac{12}{13} \text{ V}$

BYJU'S Study Planner for Board Term I (CBSE Grade 12)

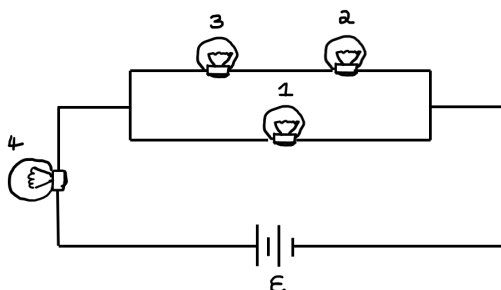
19. All bulbs consume same power. The resistance of bulb 1 is $36\ \Omega$.



(i) What is the resistance of bulb 3 ?

- A.** $4\ \Omega$
- B.** $9\ \Omega$
- C.** $12\ \Omega$
- D.** $18\ \Omega$

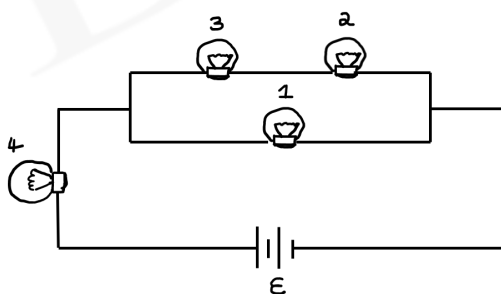20. All bulbs consume same power. The resistance of bulb 1 is $36\ \Omega$.



(ii) What is the voltage output of the battery , if the power of each bulb is 4 W ?

- A.** 12 V
- B.** 16 V
- C.** 24 V
- D.** 32 V