

Practice Challenge - Objective

Subject: Phy

Topic : Electricity Exam Preparation

1

Class: X


Time: 00:20 hrs

1. What resistance must be connected in parallel to a $4\ \Omega$ resistance to make the effective resistance equal to $2.4\ \Omega$?
 - A. $6\ \Omega$
 - B. $7\ \Omega$
 - C. $5\ \Omega$
 - D. $3\ \Omega$

2. Two bulbs are marked as 'A' having rating 60W, 220V & 'B' having rating 100W, 220V. They are connected in parallel to a 220 V source. Which of the two will glow brighter?
 - A. Bulb B.
 - B. Bulb A.
 - C. Both will glow with same brightness.
 - D. Bulb A glows and B does not glow.

Practice Challenge - Objective

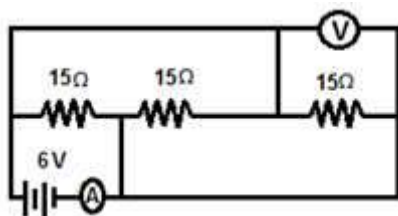3. What are the ammeter (A) and voltmeter (V) readings in the circuit?




- A. $0A, 0V$
- B. $10A, 15V$
- C. $0.6A, 6V$
- D. $1.2A, 6V$
4. An electric heater of resistance $8\ \Omega$ draws a current of $15\ A$ from the service mains operated for $2\ h$. What is the cost of the energy to operate it for 30 days at Rs 3.00 per kWh?
- A. Rs. 108
- B. Rs. 324
- C. Rs. 360
- D. Rs. 420
5. Two conducting wires of the same material and of equal lengths and equal diameters are first connected in series and then parallel in a circuit across the same potential difference. The ratio of heat produced in series and parallel combinations would be:
- A. 1:4
- B. 4:1
- C. 2:1
- D. 1:2

Practice Challenge - Objective

6. How much electrical energy flows through a wire in 1 second when the power is 1 kW?

A. 1400 J
B. 1000 J
C. 800 J
D. 400 J

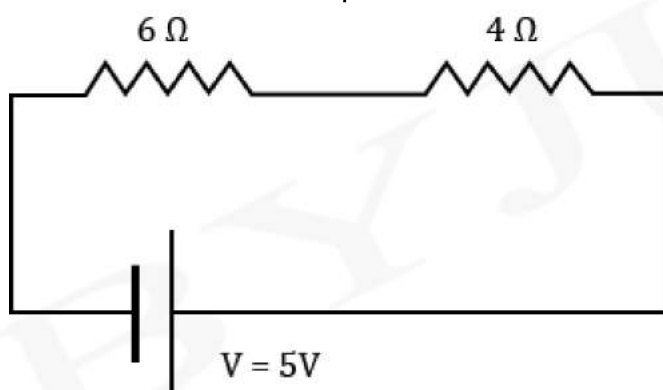7. Calculate the heat dissipated in the circuit in 30 seconds.



A. 30 J
B. 45 J
C. 75 J
D. 125 J

Practice Challenge - Objective

8. In an electrical circuit, two resistors of $2\ \Omega$ and $4\ \Omega$ respectively are connected in series to a $6\ \text{V}$ battery. The heat dissipated by the $4\ \Omega$ resistor in $5\ \text{s}$ will be:
- A. $5\ \text{J}$
 - B. $10\ \text{J}$
 - C. $20\ \text{J}$
 - D. $30\ \text{J}$
9. A toaster-oven is rated at $1.4\ \text{kW}$ at $220\ \text{V}$. Which of the following fuse will be best suited for this appliance?
- A. $2.85\ \text{A}$
 - B. $5.45\ \text{A}$
 - C. $3.20\ \text{A}$
 - D. $6.50\ \text{A}$
10. Heat energy dissipated across a conductor carrying current I , having resistance R for a time t , is given by:
- A. IR
 - B. I^2R
 - C. I^2R^2t
 - D. I^2Rt