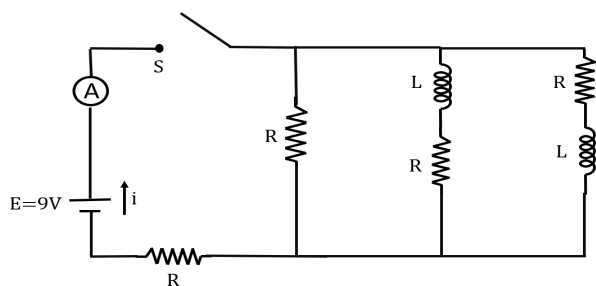


Topic : EMI, AC and EM Waves

1. The figure shows a circuit that contains four identical resistors with resistance $R = 2.0 \Omega$. Two identical inductors with inductance $L = 2.0 \text{ mH}$ and an ideal battery with emf $E = 9 \text{ V}$. The current (i) just after the switch ' s ' is closed will be:



- A. 9 A
- B. 3 A
- C. 2.25 A
- D. 3.37 A


2. Match List I with List II.

List I	List II
	<i>i.</i> Radioactive decay of nucleus
<i>a.</i> Source of microwave frequency	<i>ii.</i> Magnetron
<i>b.</i> Source of infrared frequency	<i>iii.</i> Inner shell electrons
<i>c.</i> Source of Gamma Rays	<i>iv.</i> Vibration of atoms and molecules
<i>d.</i> Source of X-rays	<i>v.</i> LASER
	<i>vi.</i> RC circuit

Choose the correct answer from the option given below:

- A.** (a)-(ii), (b)-(iv), (c)-(i), (d)-(iii)
- B.** (a)-(vi), (b)-(iv), (c)-(i), (d)-(v)
- C.** (a)-(ii), (b)-(iv), (c)-(vi), (d)-(iii)
- D.** (a)-(vi), (b)-(v), (c)-(i), (d)-(iv)

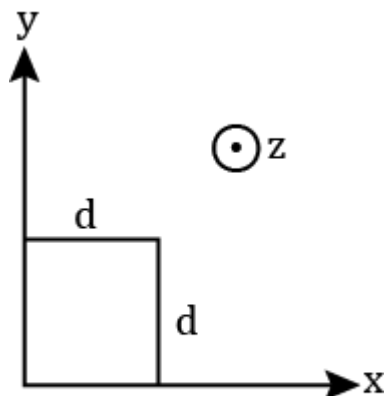3. The magnetic field in a region is given by $\vec{B} = B_0 \left(\frac{x}{a}\right) \hat{k}$. A square loop of side d is placed with its edges along the x and y axes. The loop is moved with a constant velocity $\vec{v} = v_0 \hat{i}$. The emf induced in the loop is:



- A. $\frac{B_0 v_0 d^2}{2a}$
- B. $\frac{B_0 v_0 d^2}{a}$
- C. $\frac{B_0 v_0 d}{2a}$
- D. $\frac{B_0 v_0^2 d}{2a}$
4. Two identical antennas mounted on identical towers are separated from each other by a distance of 45 km. What should nearly be the minimum height of receiving antenna to receive the signals in line of sight? (Assume radius of earth is 6400 km)
- A. 19.77 m
- B. 79.1 m
- C. 158.2 m
- D. 39.55 m

5. What happens to the inductive reactance and the current in a purely inductive circuit if the frequency is halved?
- Both, including reactance and current will be doubled
 - Both, including reactance and current will be halved
 - Inductive reactance will be halved and current will be doubled
 - Inductive reactance will be doubled and current will be halved
6. The time taken for the magnetic energy to reach 25% of its maximum value, when a solenoid of resistance R and inductance L is connected to a battery, is -
- $\frac{L}{R} \ln 2$
 - $\frac{L}{R} \ln 10$
 - Infinite
 - $\frac{L}{R} \ln 5$
7. A planer loop of wire rotates in a uniform magnetic field. Initially, at $t = 0$, the plane of the loop is perpendicular to the magnetic field. If it rotates with a period of 10 s about an axis in its plane, then the magnitude of induced emf will be maximum and minimum, respectively at:
- 2.5 s and 7.5 s
 - 2.5 s and 5.0 s
 - 5.0 s and 7.5 s
 - 5.0 s and 10.0 s


8. An inductor coil stores 64 J of magnetic field energy and dissipates energy at the rate of 640 W when a current of 8 A is passed through it. If this coil is joined across an ideal battery, find the time constant of the circuit, in seconds.

- A. 0.2
- B. 0.4
- C. 0.8
- D. 0.80

9. A light beam is described by $E = 800 \sin \omega \left(t - \frac{x}{c} \right)$. An electron is allowed to move normal to the propagation of light beam with a speed of $3 \times 10^7 \text{ ms}^{-1}$. What is the maximum magnetic force exerted on the electron ?

- A. $1.28 \times 10^{-18} \text{ N}$
- B. $12.8 \times 10^{-18} \text{ N}$
- C. $12.8 \times 10^{-17} \text{ N}$
- D. $1.28 \times 10^{-21} \text{ N}$

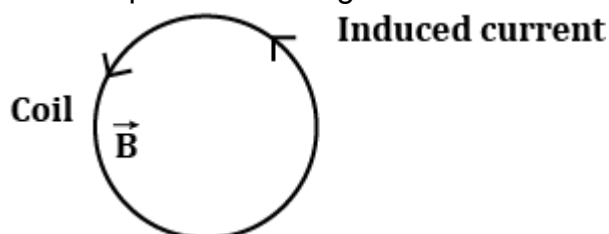
10. A coil is placed in a magnetic field \vec{B} as shown below:



A current is induced in the coil because \vec{B} is

- A. outward and increasing with time
- B. outward and decreasing with time
- C. parallel to the plane of coil and increasing with time
- D. parallel to the plane of coil and decreasing with time

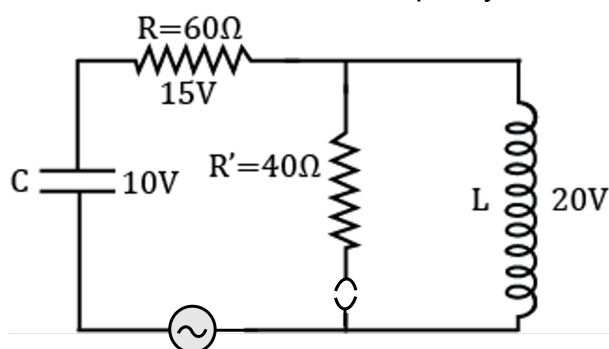
11. The angular frequency of alternating current in a LCR circuit is 100 rad/s . The components connected are shown in the figure. Find the value of inductance of the coil and capacity of condenser.




- A. 0.8 H and $250 \mu\text{F}$
- B. 0.8 H and $150 \mu\text{F}$
- C. 1.33 H and $250 \mu\text{F}$
- D. 1.33 H and $150 \mu\text{F}$
12. An alternating current is given by the equation, $i = i_1 \sin \omega t + i_2 \cos \omega t$. The RMS value of current will be :

- A. $\frac{1}{2}(i_1^2 + i_2^2)^{\frac{1}{2}}$
- B. $\frac{1}{\sqrt{2}}(i_1^2 + i_2^2)^{\frac{1}{2}}$
- C. $\frac{1}{\sqrt{2}}(i_1 + i_2)^2$
- D. $\frac{1}{\sqrt{2}}(i_1 + i_2)$

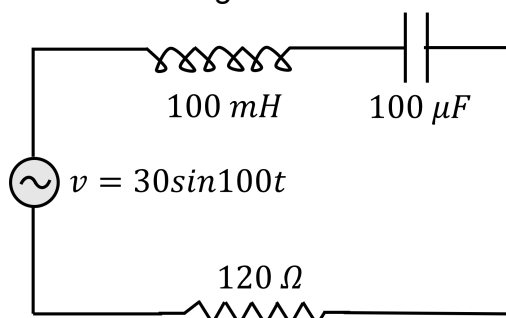13. Find the peak current and the resonant frequency of the following circuit as shown in the figure.



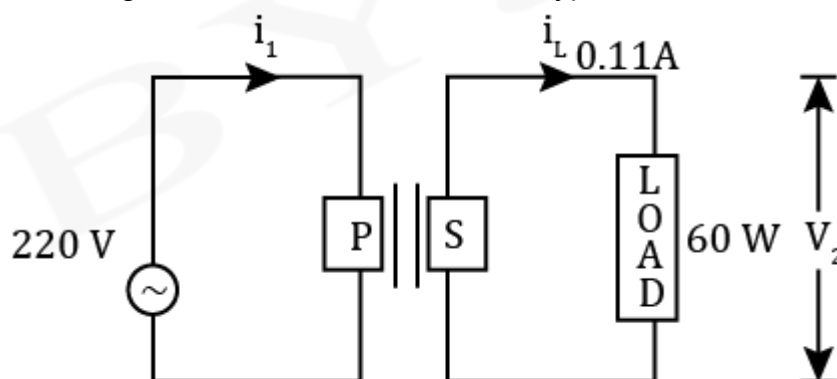- A. 0.2 A and 100 Hz
 - B. 2 A and 50 Hz
 - C. 2 A and 100 Hz
 - D. 0.2 A and 50 Hz
14. For the given circuit, comment on the type of transformer used.



- A. Step down transformer
- B. Auxilliary transformer
- C. Step up transformer
- D. Auto transformer

15. In a series LCR resonance circuit, if we change the resistance only, from a lower to higher value:
- A.** The resonance frequency will increase.
 - B.** The quality factor will increase.
 - C.** The quality factor and the resonance frequency will remain constant.
 - D.** The bandwidth of resonance circuit will increase.
16. An AC source rated 220 V, 50 Hz is connected to a resistor. The time taken by the current to change from its maximum to the rms value is:
- A.** 0.25 ms
 - B.** 25 ms
 - C.** 2.5 ms
 - D.** 2.5 s

17. Match List I with list II

List-I	List- II
(a) Phase difference between current and voltage in a purely resistive AC circuit	(i) $\pi/2$; current leads voltage
(b) Phase difference between current and voltage in a pure inductive AC circuit	(ii) zero
(c) Phase difference between current and voltage in a pure capacitive AC circuit	(iii) $\pi/2$; current lags voltage
(d) Phase difference between current and voltage in an LCR series circuit	(iv) $\tan^{-1}\left(\frac{X_C - X_L}{R}\right)$

- A.** (a) – (ii), (b) – (iii), (c) – (iv), (d) – (i)
- B.** (a) – (i), (b) – (iii), (c) – (iv), (d) – (ii)
- C.** (a) – (ii), (b) – (iv), (c) – (iii), (d) – (i)
- D.** (a) – (ii), (b) – (iii), (c) – (i), (d) – (iv)






18. In a series *LCR* circuit, the inductive reactance (X_L) is $10\ \Omega$ and the capacitive reactance (X_C) is $4\ \Omega$. The resistance (R) in the circuit is $6\ \Omega$. Find the power factor of the circuit.

- A.** $\frac{1}{\sqrt{2}}$
- B.** $\frac{\sqrt{3}}{2}$
- C.** $\frac{1}{2}$
- D.** $\frac{1}{2\sqrt{2}}$

19. For a series LCR circuit with $R = 100 \Omega$, $L = 0.5 \text{ mH}$ and $C = 0.1 \text{ pF}$ connected across $220 \text{ V} - 50 \text{ Hz}$ AC supply, the phase angle between current and supplied voltage and the nature of the circuit is :

- A.** 0° , resistive circuit
- B.** $\approx 90^\circ$, predominantly inductive circuit
- C.** 0° , resonance circuit
- D.** $\approx 90^\circ$, predominantly capacitive circuit

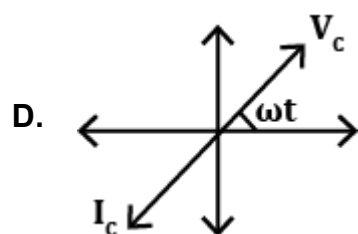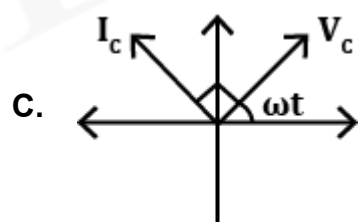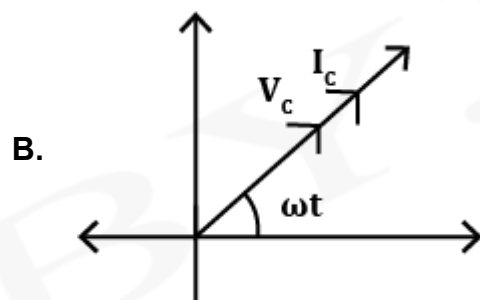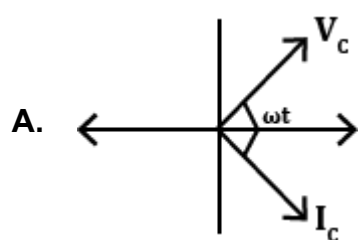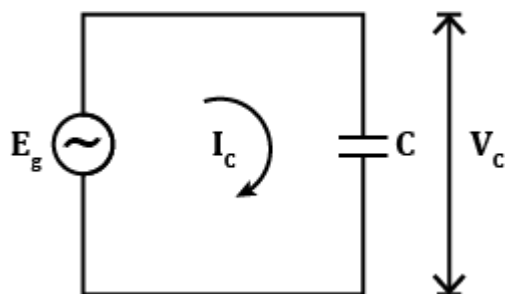20. In a circuit consisting of a capacitance and a generator with alternating emf $E_g = E_g \sin \omega t$, where V_C and I_C are the voltage and current. Correct phasor diagram for such circuit is :



21. In amplitude modulation, the message signal $V_m(t) = 1 \sin(2\pi \times 10^5 t)$ volts and carrier signal $V_C(t) = 20 \sin(2\pi \times 10^7 t)$ volts. The modulated signal now contains the message signal with lower side band and upper side band frequency. Therefore the bandwidth of modulated signal is α kHz. The value of α is :
- 200 kHz
 - 50 kHz
 - 100 kHz
 - 0 kHz
22. A 10Ω resistance is connected across 220 V–50 Hz AC supply. The time taken by the current to change from its maximum value to the *RMS* value is
- 2.5 ms
 - 1.5 ms
 - 3.0 ms
 - 4.5 ms
23. If a message signal of frequency f_m is amplitude modulated with a carrier signal of frequency f_c and radiated through an antenna , the wavelength of the corresponding signal in air is :
- [Given , c = speed of electromagnetic wave in vacuum/air]
- $\frac{c}{f_c + f_m}$
 - $\frac{c}{f_c - f_m}$
 - $\frac{c}{f_m}$
 - $\frac{c}{f_c}$

24. A signal of 0.1 kW is transmitted in a cable. The attenuation of cable is -5 dB per km and cable length is 20 km. The power received at receiver is 10^{-x} W. The value of x is .

$$\left[\text{Gain in } dB = 10 \log_{10} \left(\frac{P_0}{P_1} \right) \right]$$

25. An audio signal $v_m = 20 \sin 2\pi(1500t)$ amplitude modulates a carrier $v_c = 80 \sin 2\pi(100,000t)$. The value of percent modulation is

26. Given below are two statements :

Statement I : A speech signal of 2 kHz is used to modulate a carrier signal of 1 MHz. The bandwidth requirement for the signal is 4 kHz.

Statement II : The sideband frequencies are 1002 kHz and 998 kHz.

In the light of the above statements, choose the correct answer from the options given below.

- A. Both statement I and statement II are false.
 - B. Statement I is false, but statement II is true.
 - C. Statement I is true, but statement II is false.
 - D. Both statement I and statement II are true.
27. The maximum and minimum amplitude of an amplitude modulated wave is 16 V and 8 V respectively. The modulation index for this amplitude modulated wave is $x \times 10^{-2}$. The value of x is _____. (up to two significant figures)
28. If the highest frequency modulating a carrier is 5 kHz, then the number of AM broadcast stations accommodated in a 90 kHz bandwidth are _____.

29. A carrier signal $C(t) = 25 \sin(2.512 \times 10^{10}t)$ is amplitude modulated by a message signal $m(t) = 5 \sin(1.57 \times 10^8t)$ and transmitted through an antenna. What will be bandwidth of the modulated signal?

- A. 1987.5 MHz
- B. 2.01 GHz
- C. 50 MHz
- D. 8 GHz

30. In a plane electromagnetic wave, the directions of electric field and magnetic field are represented by \hat{k} and $2\hat{i} - 2\hat{j}$, respectively. What is the unit vector along direction of propagation of the wave ?

- A. $\frac{1}{\sqrt{2}}(\hat{i} + \hat{j})$
- B. $\frac{1}{\sqrt{2}}(\hat{j} + \hat{k})$
- C. $\frac{1}{\sqrt{5}}(\hat{i} + 2\hat{j})$
- D. $\frac{1}{\sqrt{5}}(2\hat{i} + \hat{j})$