



## Alternating Current- L2

1. A coil has negligible resistance and an inductive reactance of  $20\ \Omega$  at  $50\text{ Hz}$ . If an AC source of  $200\text{ V}$  and  $100\text{ Hz}$  frequency is connected across the coil, the rms current in the coil will be

- A.  $2.0\text{ A}$
- B.  $5.0\text{ A}$
- C.  $7.0\text{ A}$
- D.  $10.0\text{ A}$

We know that,

$$X_L = \omega L = 2\pi f L$$

$$\Rightarrow 20 = 2\pi(50)L$$

$$\Rightarrow L = \frac{1}{5\pi}\text{ H}$$

When the coil is connected across the AC source,


$$\therefore X'_L = 2\pi(100) \times \frac{1}{5\pi} = 40\ \Omega$$

Now,

$$i_{rms} = \frac{V_{rms}}{X'_L} = \frac{200}{40} = 5.0\text{ A}$$

Hence, option (B) is the correct answer.

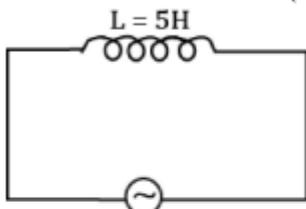2. An inductor of inductance,  $L = 5 \text{ H}$  is connected to an AC source having voltage,  $V = 10 \sin\left(10t + \frac{\pi}{6}\right)$ . Find the inductive reactance.



- A.  $20 \Omega$
- B.  $30 \Omega$
- C.  $50 \Omega$
- D.  $70 \Omega$

3. A capacitor of capacitive reactance,  $12 \Omega$  is connected with an AC source having voltage,  $V = 3 \sin(\omega t + \pi/6)$ . Find the expression of instantaneous current in the circuit.

- A.  $0.35 \sin(\omega t + 2\pi/3)$
- B.  $0.25 \sin(\omega t + 2\pi/3)$
- C.  $0.57 \sin(\omega t - 2\pi/3)$
- D.  $0.15 \sin(\omega t - 2\pi/3)$

$$I_0 = \frac{V_0}{X_C} = \frac{3}{12} = 0.25 \text{ A}$$

For a purely capacitive circuit, current leads ahead the voltage by  $\pi/2$ .

Therefore, instantaneous current in the circuit,

$$I = 0.25 \sin(\omega t + \pi/6 + \pi/2)$$

$$\Rightarrow I = 0.25 \sin(\omega t + 2\pi/3)$$

Hence, option (B) is the correct answer.

4. An inductor of inductance,  $L = 5 \text{ H}$  is connected to an AC source having voltage,  $V = 10 \sin\left(10t + \frac{\pi}{6}\right)$ . Find the peak value of current in the circuit.

- A. 0.1 A
- B. 0.2 A
- C. 0.3 A
- D. 0.4 A

Given:

Inductance,  $L = 5 \text{ H}$

Voltage,  $V = 10 \sin\left(10t + \frac{\pi}{6}\right)$

So, peak value of current in the circuit,

$$i_0 = \frac{V_0}{X_L} = \frac{V_0}{\omega L} = \frac{10}{10 \times 5} = 0.2 \text{ A}$$

Hence, option (B) is the correct answer.

5. An inductor of 1 H and a capacitor of  $1 \mu\text{F}$  have equal reactance when connected to the same AC source at the same condition. The value of reactance is -

A.  $10^4 \Omega$

B.  $10^2 \Omega$

C.  $10^3 \Omega$

D.  $10^5 \Omega$

It is given that,  $X_L = X_C$

$$\Rightarrow \omega L = \frac{1}{\omega C}$$

$$\Rightarrow \omega^2 = \frac{1}{LC} = \frac{1}{1 \times 10^{-6}}$$

$$\therefore \omega = 10^3 \text{ rad/s}$$

Now,

$$X_L = \omega L = 10^3 \times 1 = 10^3 \Omega$$

$$\therefore X_L = X_C = 10^3 \Omega$$

Hence, option (C) is the correct answer.