



## Alternating Current-L2


1. A coil has negligible resistance and an inductive reactance of  $20\ \Omega$  at  $50\text{ Hz}$ .

If an AC source of  $200\text{ V}$  and  $100\text{ Hz}$  frequency is connected across the coil, the rms current in the coil will be

- A.  $2.0\text{ A}$
- B.  $5.0\text{ A}$
- C.  $7.0\text{ A}$
- D.  $10.0\text{ A}$

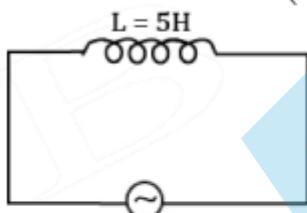2. An inductor of inductance,  $L = 5\text{ H}$  is connected to an AC source having

voltage,  $V = 10 \sin\left(10t + \frac{\pi}{6}\right)$ . Find the inductive reactance.



- A.  $20\ \Omega$
- B.  $30\ \Omega$
- C.  $50\ \Omega$
- D.  $70\ \Omega$

3. A capacitor of capacitive reactance,  $12 \Omega$  is connected with an AC source having voltage,  $V = 3 \sin(\omega t + \pi/6)$ . Find the expression of instantaneous current in the circuit.

- A.**  $0.35 \sin(\omega t + 2\pi/3)$
- B.**  $0.25 \sin(\omega t + 2\pi/3)$
- C.**  $0.57 \sin(\omega t - 2\pi/3)$
- D.**  $0.15 \sin(\omega t - 2\pi/3)$

4. An inductor of  $1 \text{ H}$  and a capacitor of  $1 \mu\text{F}$  have equal reactance when connected to the same AC source at the same condition. The value of reactance is -

- A.**  $10^4 \Omega$
- B.**  $10^2 \Omega$
- C.**  $10^3 \Omega$
- D.**  $10^5 \Omega$

5. An inductor of  $1 \text{ H}$  and a capacitor of  $1 \mu\text{F}$  have equal reactance when connected to the same AC source at the same condition. The value of reactance is -

- A.**  $10^4 \Omega$
- B.**  $10^2 \Omega$
- C.**  $10^3 \Omega$
- D.**  $10^5 \Omega$

1. (B)
2. (C)
3. (B)
4. (B)
5. (C)