




## Alternating Current-L4

1. In an AC circuit, the power factor


- A. is unity when the circuit contains an ideal resistor only.
- B. is zero when the circuit contains an ideal inductor only.
- C. Both options (A) and (B)
- D. None of these

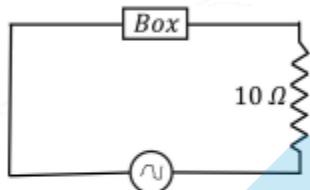2. In the circuit shown in the figure, the power factor of the box is 0.5 and the power factor of the circuit is  $\sqrt{3}/2$ . Current leads the voltage. Find the effective resistance of the box.




- A.  $1 \Omega$
- B.  $3 \Omega$
- C.  $5 \Omega$
- D.  $7 \Omega$

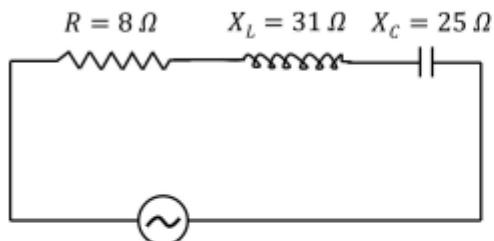3. The given AC RLC circuit is connected to an AC source of 110 V; 50 Hz. The power factor of the circuit is -




- A. 0.56
- B. 0.64
- C. 0.80
- D. 0.33

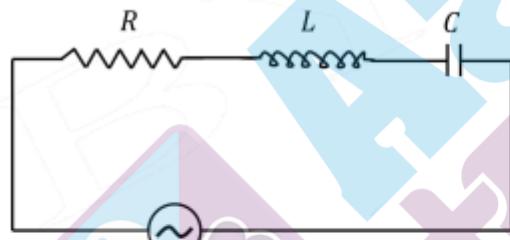4. For the given AC RLC circuit, at a particular frequency ( $f$ ) of the AC source, the current leads the voltage by  $45^\circ$ . The relation between  $R$ ,  $L$  and  $C$  is -



- A.  $C = \frac{1}{2\pi f(2\pi fL - R)}$
- B.  $C = \frac{1}{2\pi f(2\pi fL + R)}$
- C.  $C = \frac{1}{\pi f(2\pi fL - R)}$
- D.  $C = \frac{1}{\pi f(2\pi fL + R)}$

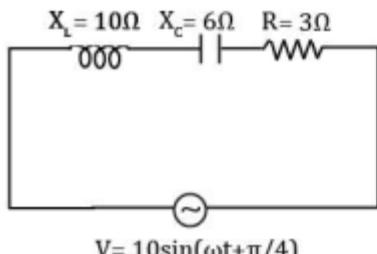5. For the given AC LCR circuit, at a particular frequency of the AC source, the expression for current ( $i$ ) as a function of time ( $t$ ) will be -



- A.**  $i = 4 \sin(\omega t + 8^\circ)$
- B.**  $i = 4 \sin(\omega t - 8^\circ)$
- C.**  $i = 2 \sin(\omega t - 8^\circ)$
- D.**  $i = 2 \sin(\omega t + 8^\circ)$

1. (C)
2. (C)
3. (C)
4. (B)
5. (C)