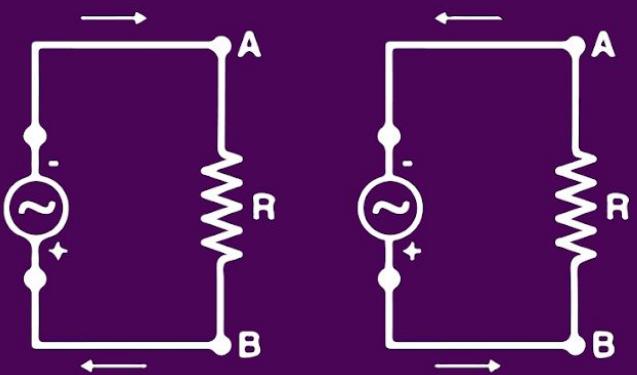


**BONUS
SESSION**



ALTERNATING CURRENT - L2

PHYSICS





<https://t.me/neetaakashdigital>



CONTENTS

Rms value of A sinusoidal AC


Phasor diagram

Pure resistive ac circuit

Pure Inductive ac circuit

Pure capacitive ac circuit

$$i_{rms} = \sqrt{\langle i^2 \rangle}$$

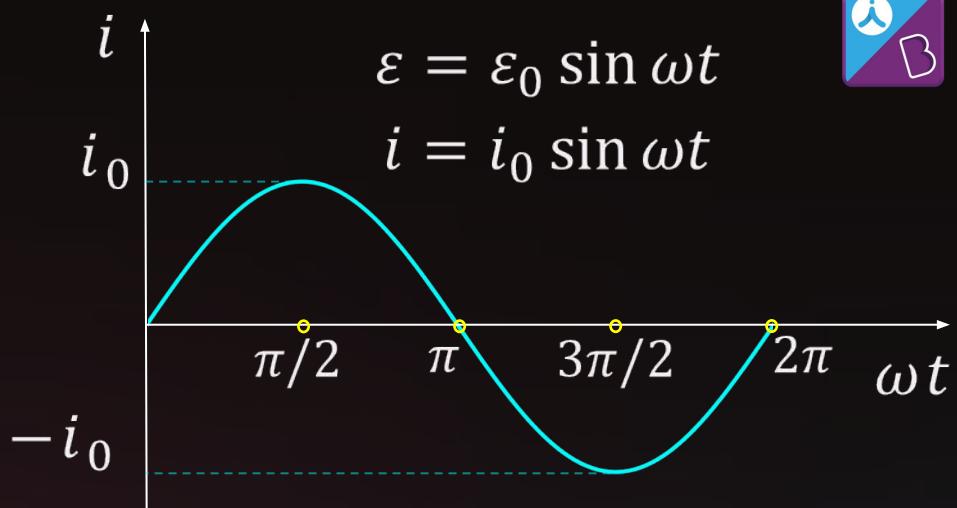


$$i_{rms} = \sqrt{\langle i^2 \rangle}$$

$$i_{rms} = \sqrt{\langle i_0^2 \sin^2 \omega t \rangle}$$


$$i_{rms}^2 = \frac{1}{T} \int_0^T i_0^2 \sin^2 \omega t \, dt = \frac{i_0^2}{T} \int_0^T \sin^2 \omega t \, dt$$

$$i_{rms}^2 = \frac{i_0^2}{T} \int_0^T \frac{1 - \cos 2\omega t}{2} \, dt \quad \left(\sin^2 \theta = \frac{1 - \cos 2\theta}{2} \right)$$
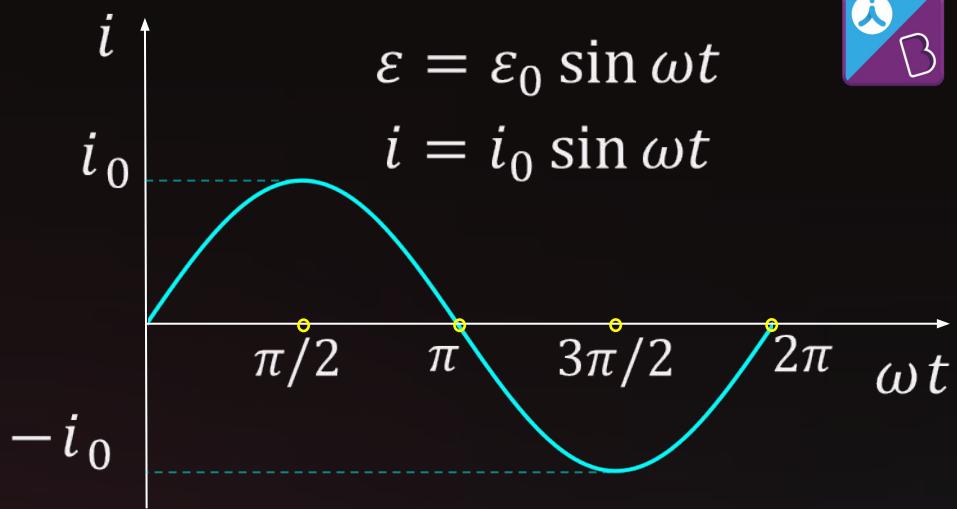
$$i_{rms}^2 = \frac{i_0^2}{2T} \left(t - \frac{\sin 2\omega t}{2\omega} \right)_0^T$$


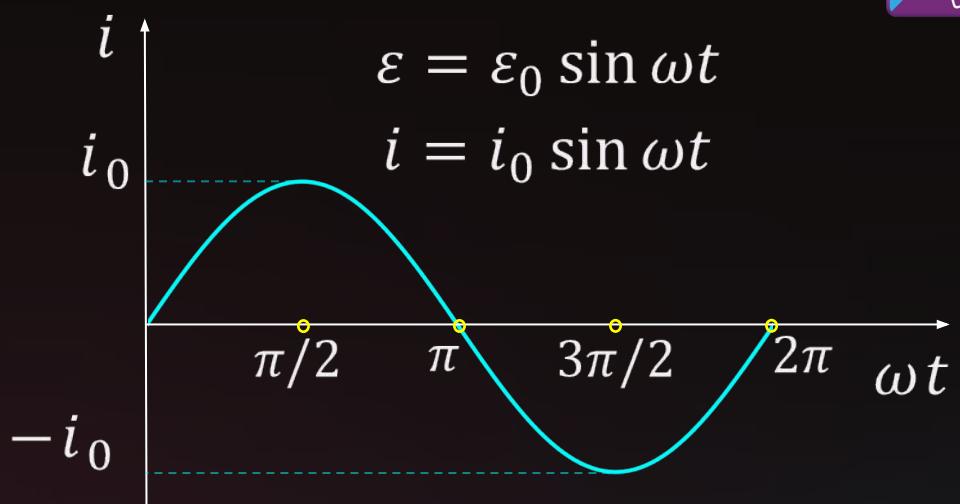
$$i_{rms} = \sqrt{ \langle i^2 \rangle }$$




$$i_{rms} = \sqrt{ \langle i^2 \rangle }$$


$$i_{rms}^2 = \frac{i_0^2}{2T} \left(t - \frac{\sin 2\omega t}{2\omega} \right)_0^T \quad \left(T = \frac{2\pi}{\omega} \right)$$

$$i_{rms}^2 = \frac{i_0^2}{2T} \left(\left(T - \frac{\sin 2\omega \left(\frac{2\pi}{\omega} \right)}{2\omega} \right) - (0 - \sin 0) \right) = \frac{i_0^2}{2T} T$$

$$i_{rms}^2 = \frac{i_0^2}{2}$$

AC

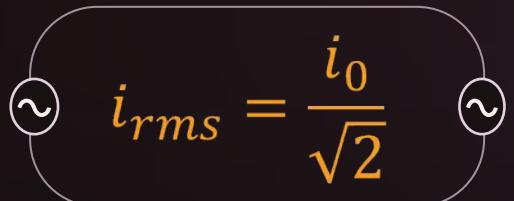

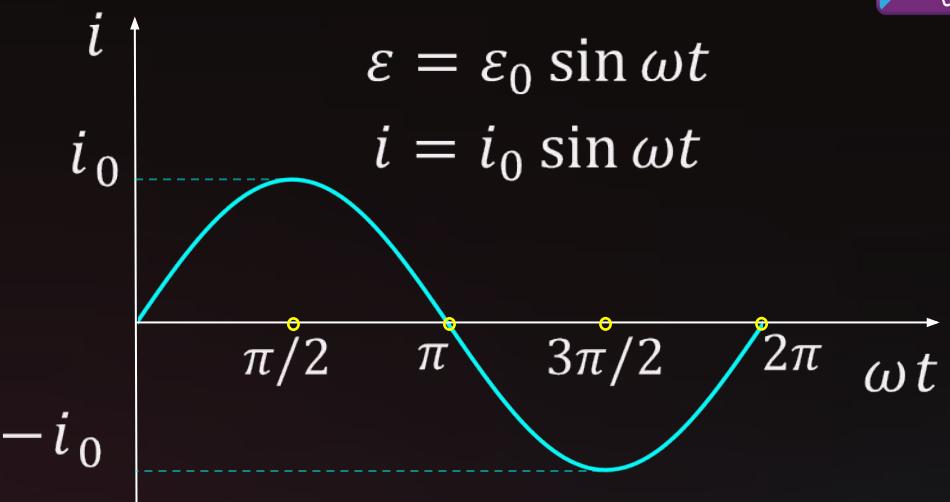


$$i_{rms} = \frac{i_0}{\sqrt{2}}$$

$$(i_{av})_{half\ cycle} = \frac{2i_0}{\pi}$$

$$\varepsilon_{rms} = \frac{\varepsilon_0}{\sqrt{2}}$$
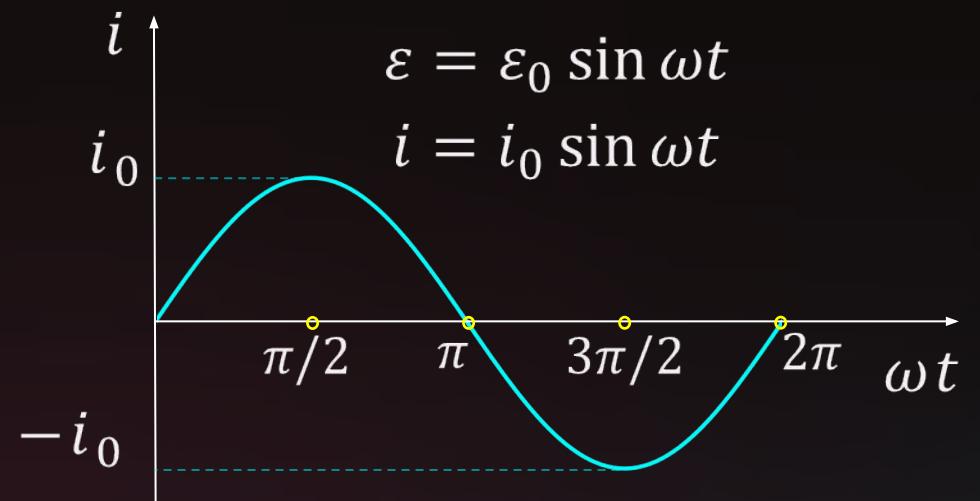
$$(\varepsilon_{av})_{half\ cycle} = \frac{2\varepsilon_0}{\pi}$$





Household current \rightarrow sinusoidal AC ($\varepsilon = \varepsilon_0 \sin \omega t$)
220 V, 50 Hz

Significance OF Rms value



Household current \rightarrow sinusoidal AC ($\varepsilon = \varepsilon_0 \sin \omega t$)
220 V, 50 Hz

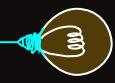
$$\varepsilon_{rms} = 220 \text{ V}$$

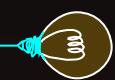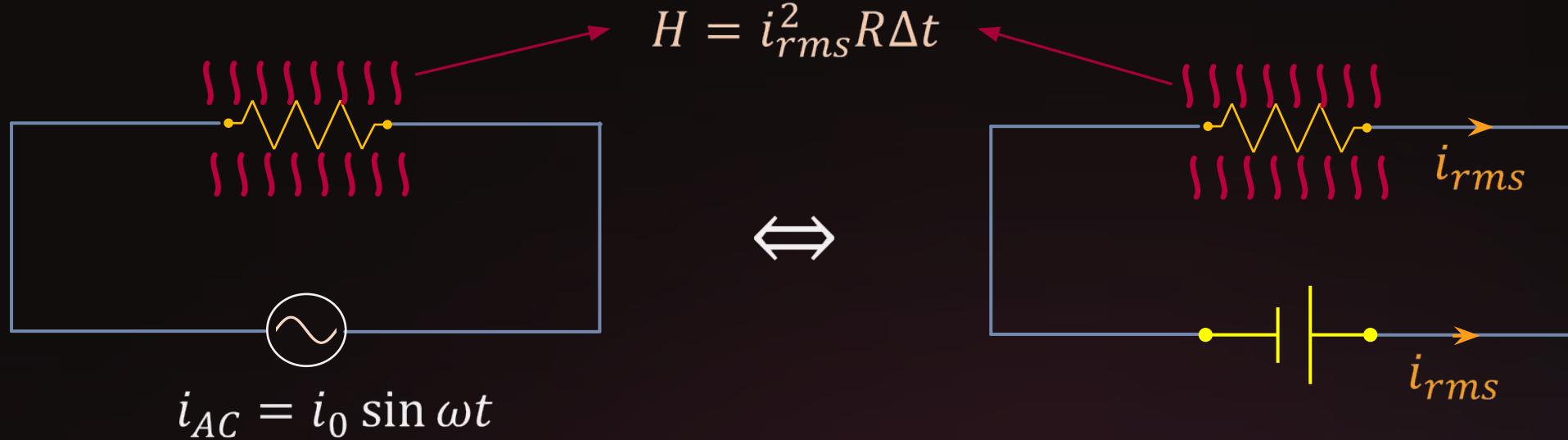

$$\varepsilon_{av} = 0 \text{ V}$$


$$\varepsilon_0 = \sqrt{2} \varepsilon_{rms}$$

$$\varepsilon_0 = \sqrt{2} \times 220 = 311.12 \text{ V} \approx 311 \text{ V}$$

If problem states only ε (not $\varepsilon_0, \varepsilon_{rms}, \varepsilon_{av}$)
then, consider it as ε_{rms}

Significance OF Rms value




RMS value of a given AC can be defined as that DC value which produces same heat in a resistance which the AC produces in that resistance in same duration.

i_{rms} is the effective DC value of a given AC


Significance OF Rms value



$$H = i_{rms}^2 R \Delta t$$

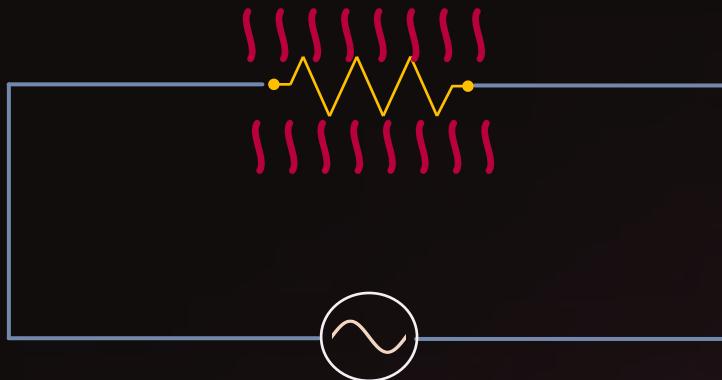

$$i_{AC} = i_0 \sin \omega t$$

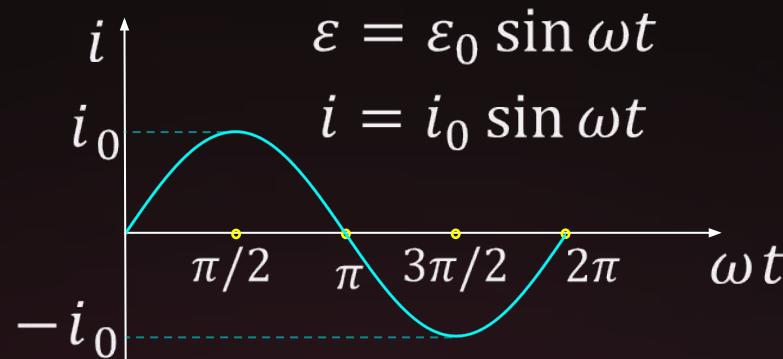

 DC devices cannot measure alternating current or emf. Normal Ammeter, Voltmeter will show **only zero** for AC


 Hot Wire Ammeter & Hot Wire Voltmeter are used to measure AC. They measure RMS value of i & ϵ .



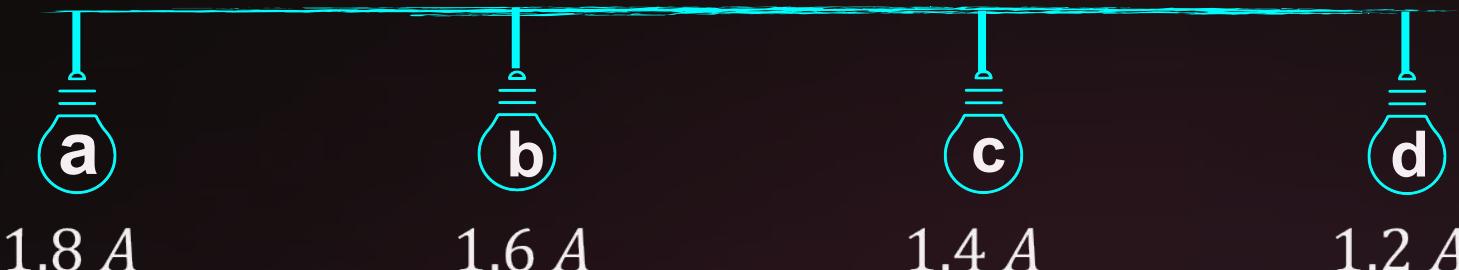Question



If the voltage of a source in an AC circuit is represented by the equation, $E = 220\sqrt{2}\sin(314t)$. Calculate the peak value of the current if the net resistance of the circuit is $220\ \Omega$. Take $\sqrt{2} = 1.4$





DISCUSSION



Given,

$$\text{Voltage, } \varepsilon = 220\sqrt{2}\sin(314t)$$



DISCUSSION



Given,

$$\text{Voltage, } \varepsilon = 220\sqrt{2}\sin(314t)$$

Comparing with $\varepsilon = \varepsilon_o \sin \omega t$, we get,

$$\varepsilon_o = 220\sqrt{2} \text{ V}$$

So, peak value of current

$$i_o = \frac{\varepsilon_o}{R} = \frac{220\sqrt{2}}{220}$$


$$i_o = 1.4 \text{ A}$$



ANSWER



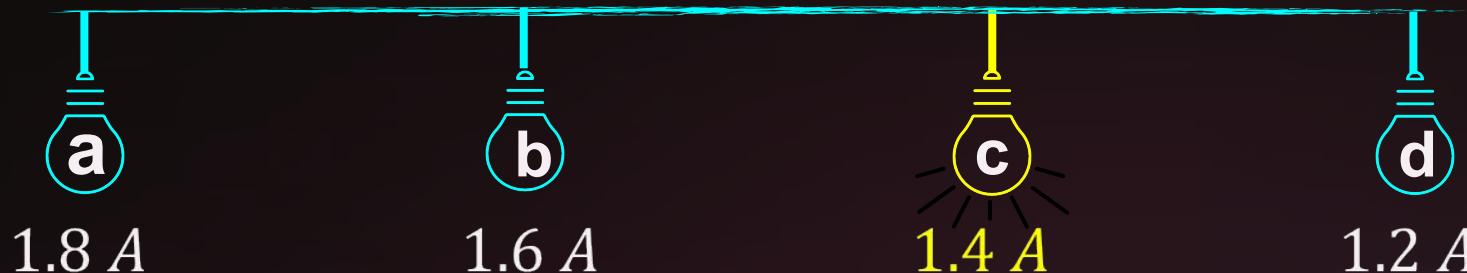If the voltage of a source in an AC circuit is represented by the equation, $E = 220\sqrt{2}\sin(314t)$. Calculate the peak value of the current if the net resistance of the circuit is $220\ \Omega$. Take $\sqrt{2} = 1.4$



Example




Find I_{rms} for the following :-

(i) $i = i_o + i_o \sin \omega t$

Shortcut To Find RMS Value



For Full Cycle

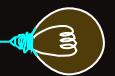
$$\overline{\sin \omega t} = 0$$


$$\overline{\cos \omega t} = 0$$


$$\overline{\sin^2 \omega t} = \frac{1}{2}$$


$$\overline{\cos^2 \omega t} = \frac{1}{2}$$

Example



Find I_{rms} for the following :-

(i) $i = i_o + i_o \sin \omega t$

Homework



Find I_{rms} for the following :-

$$(ii) \ i = i_1 \sin \omega t + i_2 \cos \omega t$$

CIRCUITS




I. An AC source connected only to:



Resistor




An Inductor

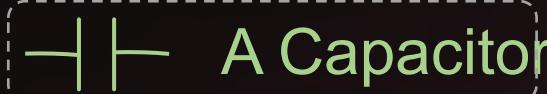


A Capacitor

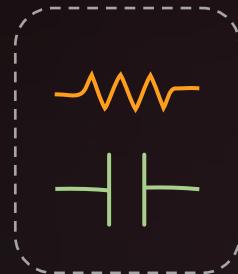
II. An AC source connected to more than one element.




RC
Circuit

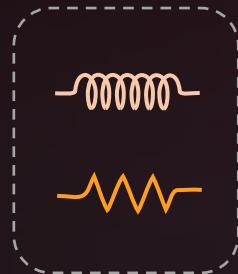

LR
Circuit

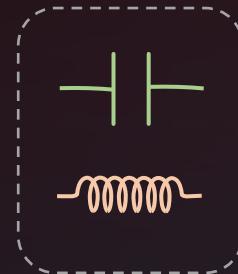

LC
Circuit

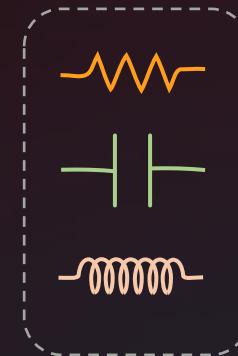

LCR
Circuit


Circuit



Apply KVL :

$$\varepsilon - iR = 0 \quad \Rightarrow \quad i = \frac{\varepsilon}{R}$$
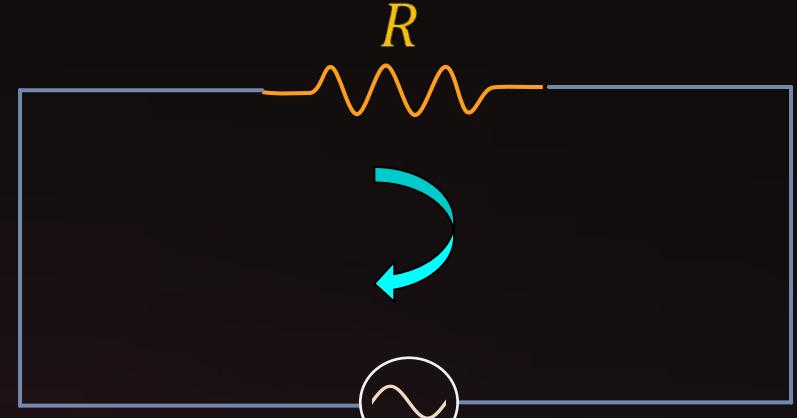
$$i = \frac{\varepsilon_0 \sin \omega t}{R}$$




$$\varepsilon = \varepsilon_0 \sin \omega t$$

Circuit



Apply KVL ;

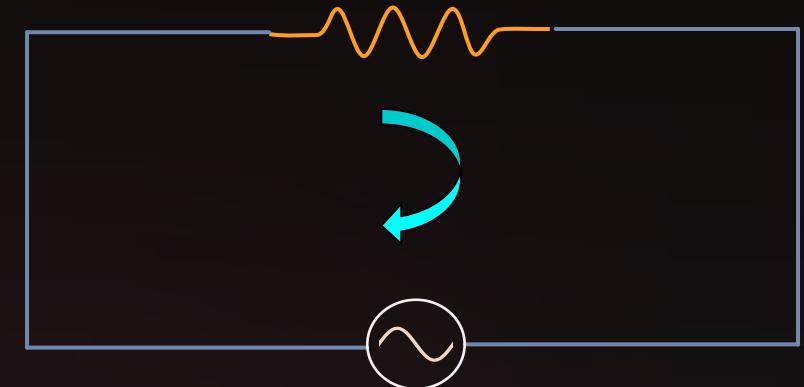

Peak voltage



Peak current

Current is **in phase** with potential

diagram




A diagram that represents AC and voltage of same frequency as rotating vectors (phasors)

along with proper phase angle between them.

$$\varepsilon = \varepsilon_0 \sin \omega t$$

$$i = i_0 \sin(\omega t + \phi)$$

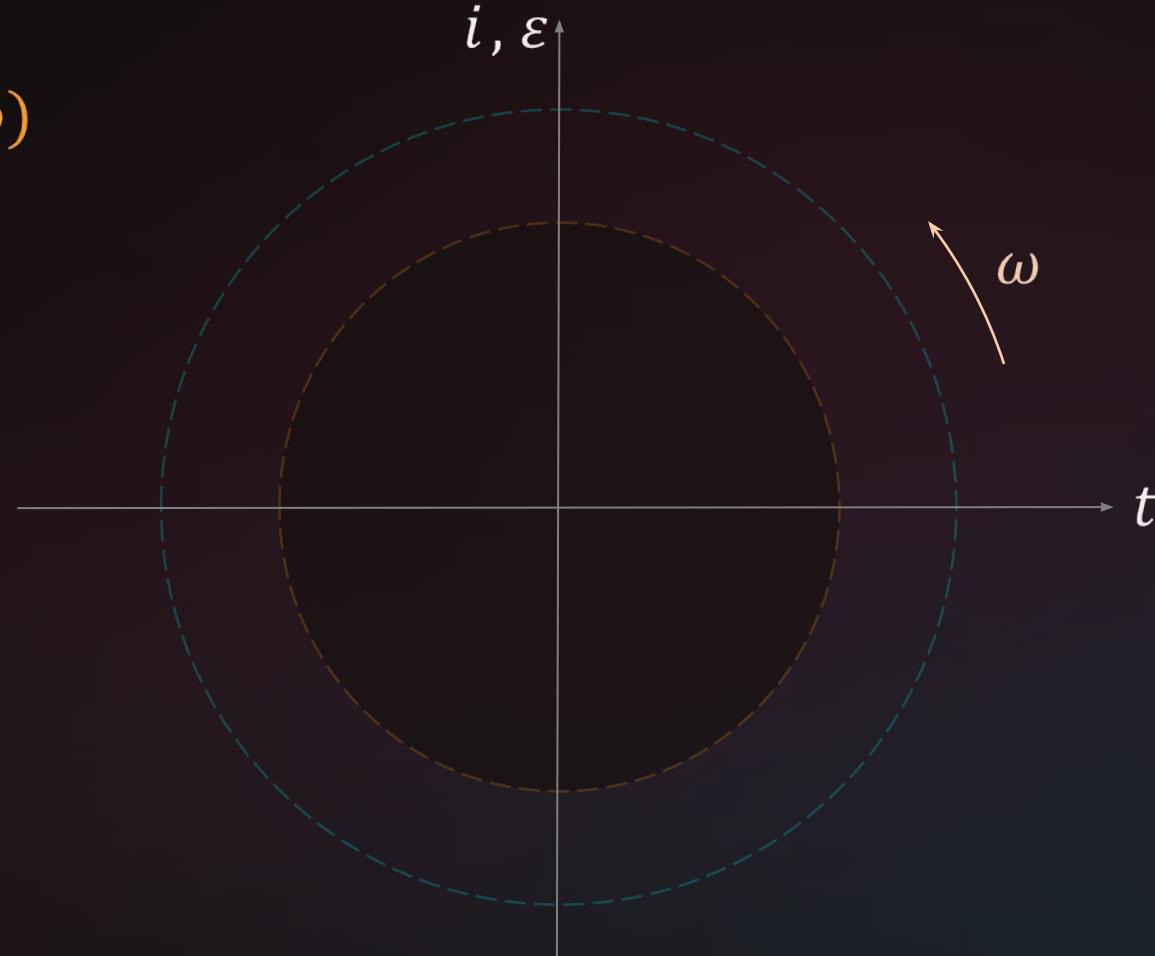


diagram



A diagram that represents AC and voltage of same frequency as rotating vectors (phasors) along with proper phase angle between them.

Phase difference

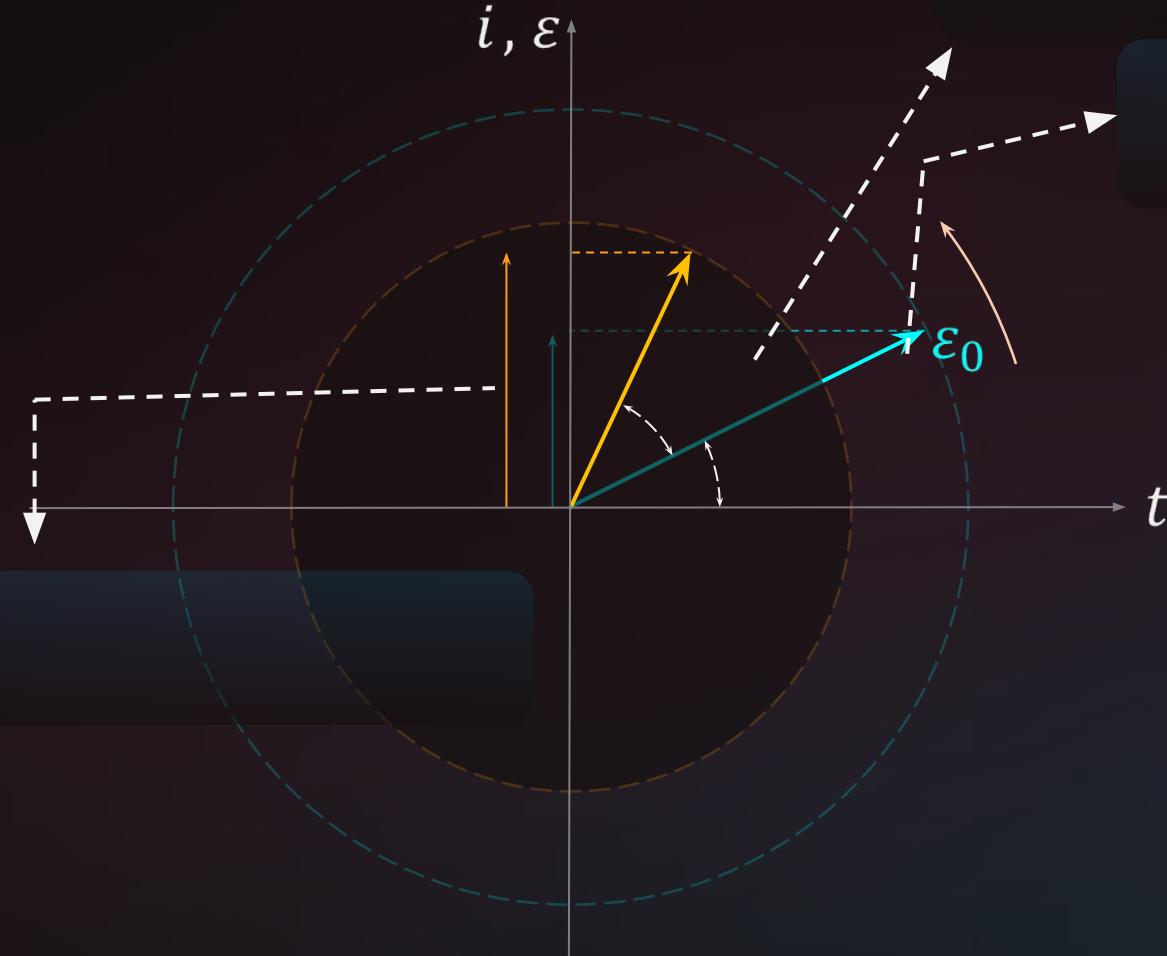


Circuit





Current is **in phase** with potential

Phasor diagram

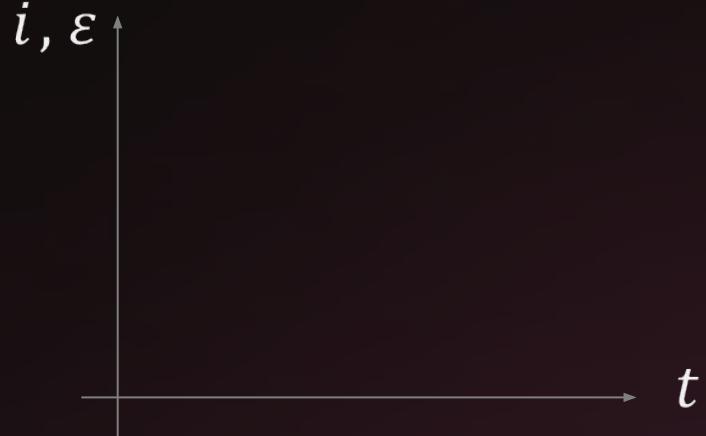

$$i = i_0 \sin \omega t$$

Wave diagram

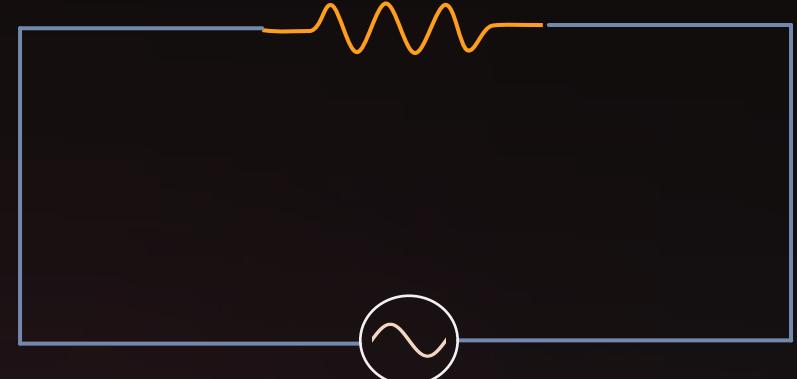 


Circuit




Current is in phase with potential

Phasor diagram

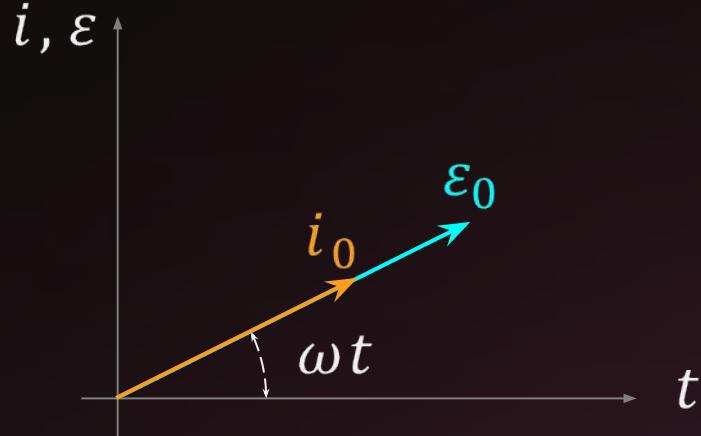


R

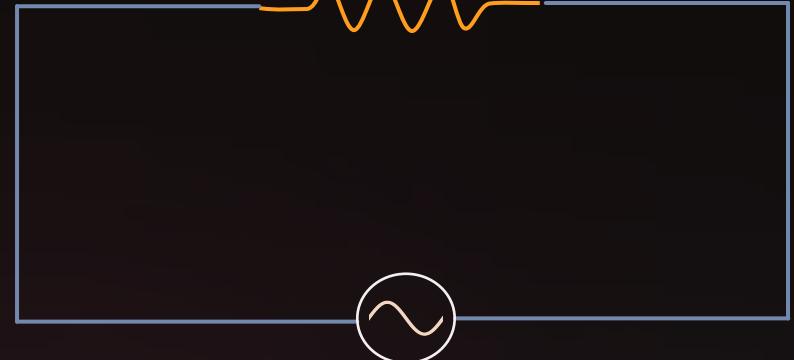

$$\varepsilon = \varepsilon_0 \sin \omega t$$
$$i = i_0 \sin \omega t$$


Wave diagram

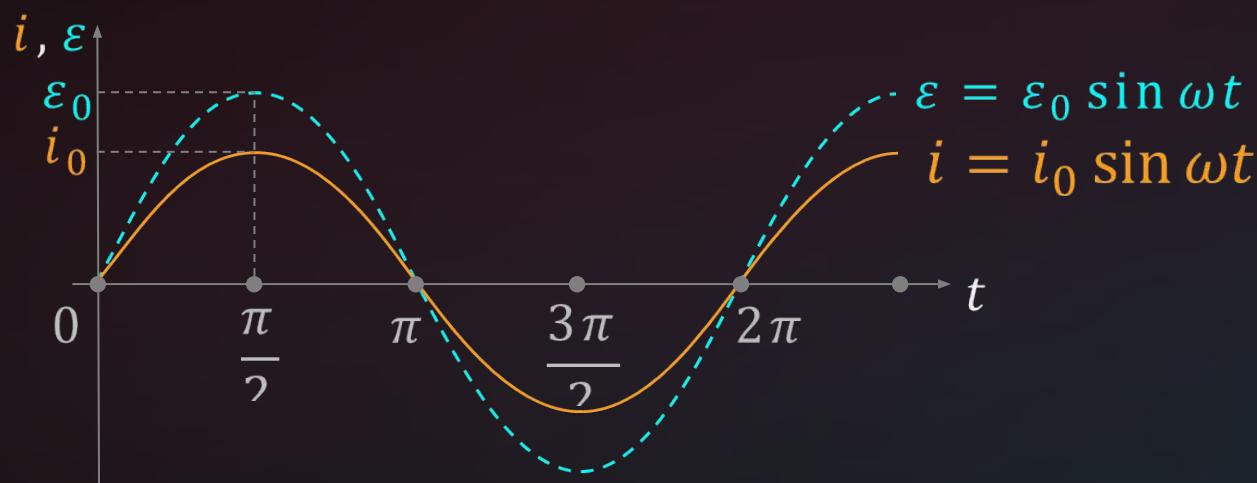

Circuit

Potential drop across
inductance,
Apply KVL ;

$$V_L = L \frac{di}{dt}$$

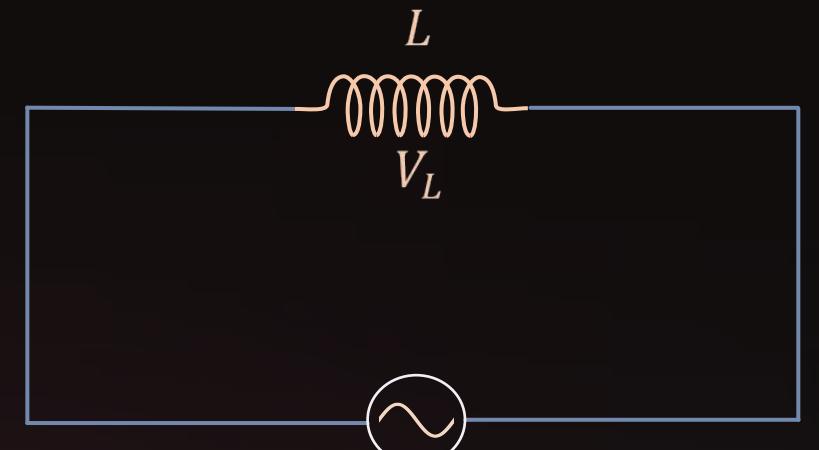

Circuit

Potential drop across inductance,
Apply KVL ;


$$\mathcal{E} - V_L = 0$$

$$V_L = L \frac{di}{dt}$$

$$L \frac{di}{dt} = \mathcal{E} \Rightarrow di = \frac{\mathcal{E}}{L} dt$$

$$i = \int di = \int \frac{\mathcal{E}_0 \sin \omega t}{L} dt$$
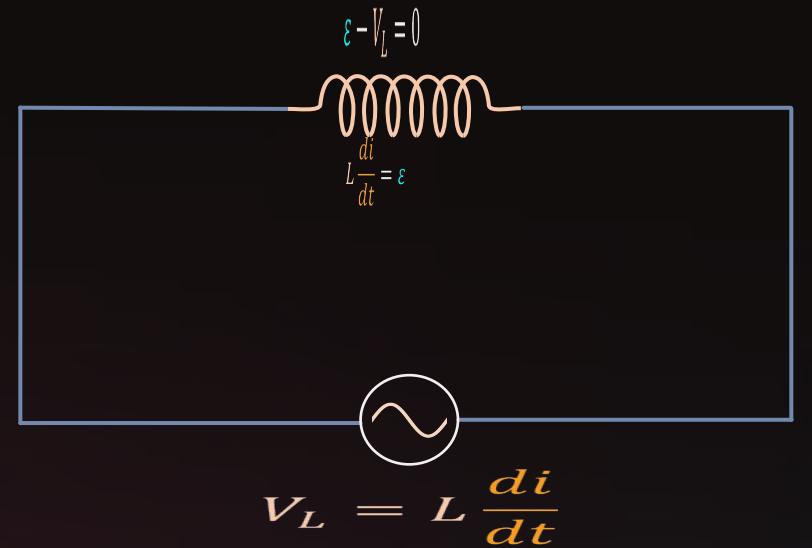
$$i = \frac{\mathcal{E}_0}{L} \frac{(-\cos \omega t)}{\omega} = -\frac{\mathcal{E}_0}{L\omega} \cos \omega t$$




$$V_L = L \frac{di}{dt}$$



Circuit
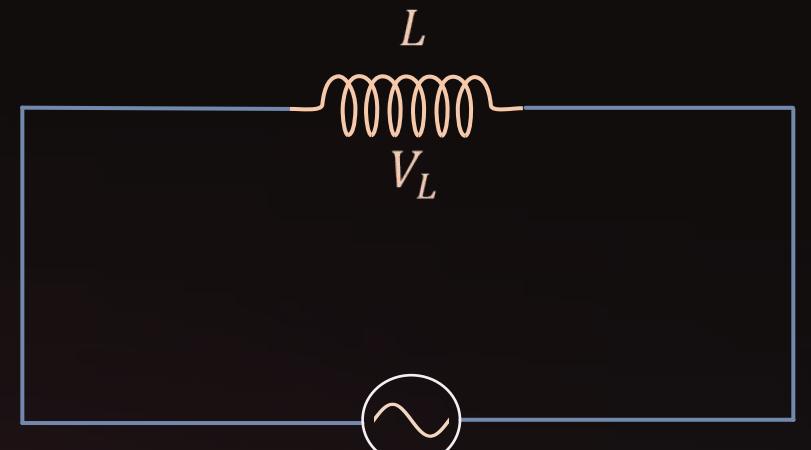
$$i = \frac{\varepsilon_0}{L} \frac{(-\cos \omega t)}{\omega} = -\frac{\varepsilon_0}{L\omega} \cos \omega t$$



Circuit



$$i = \frac{\varepsilon_0}{L} \frac{(-\cos \omega t)}{\omega} = -\frac{\varepsilon_0}{L\omega} \cos \omega t$$

$$i = -\frac{\varepsilon_0}{L\omega} \sin \left(\frac{\pi}{2} - \omega t \right) = \frac{\varepsilon_0}{L\omega} \sin \left(\omega t - \frac{\pi}{2} \right)$$


$$i = i_0 \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$i_0 = \frac{\varepsilon_0}{L\omega} = \frac{\varepsilon_0}{X_L}$$

$$X_L = L\omega$$

Inductive reactance

SI Unit : Ohm (Ω)

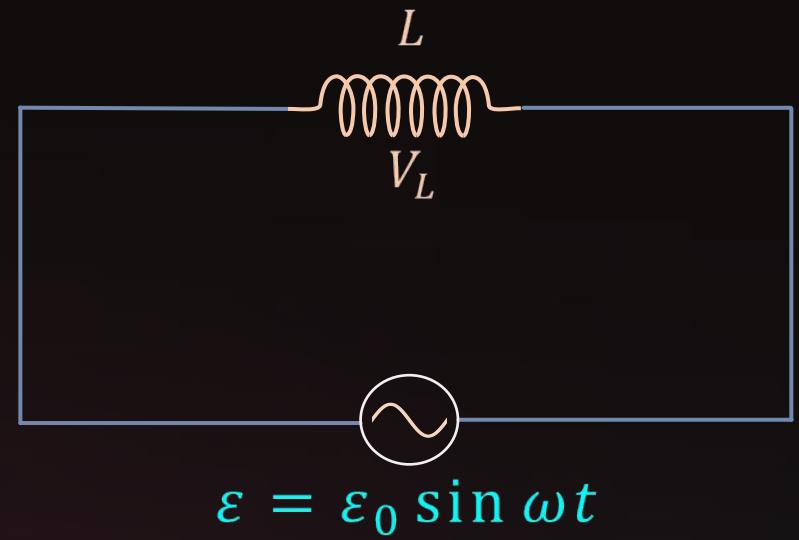

Circuit



$$\text{Phase difference } (\phi) = \left(\omega t - \frac{\pi}{2} \right) - \omega t = -\frac{\pi}{2}$$




Current lags potential by 90°



Phasor diagram



Wave diagram

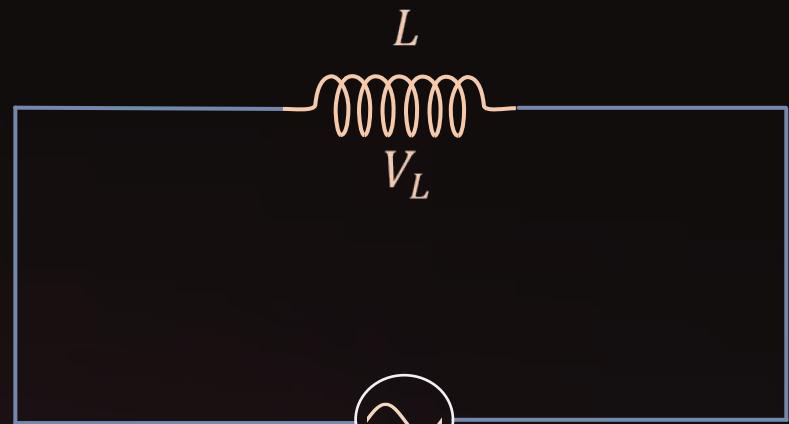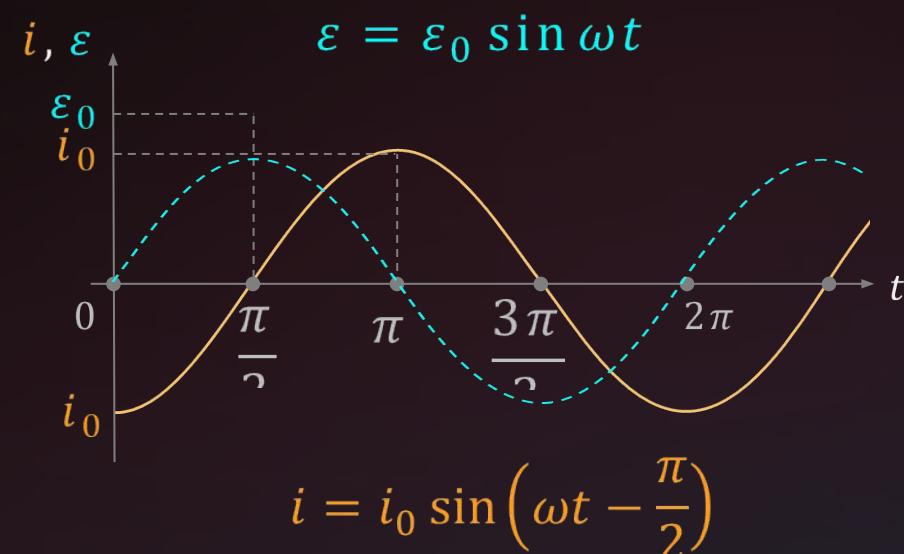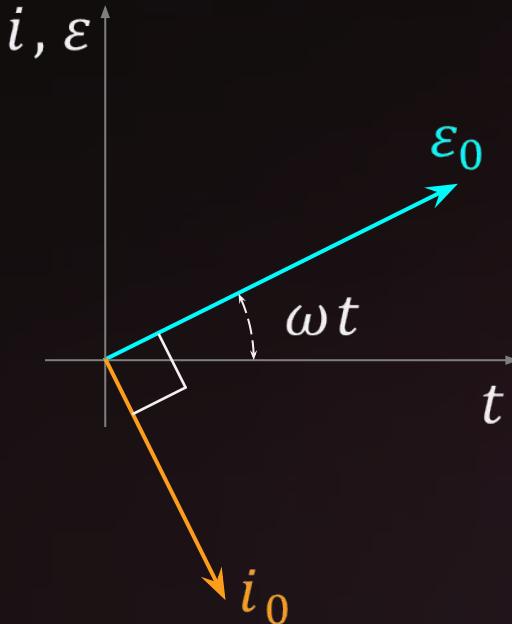

$$\epsilon = \epsilon_0 \sin \omega t$$


$$i = i_0 \sin \left(\omega t - \frac{\pi}{2} \right)$$

Circuit



X_L v/s frequency (f)

$$X_L = L\omega$$

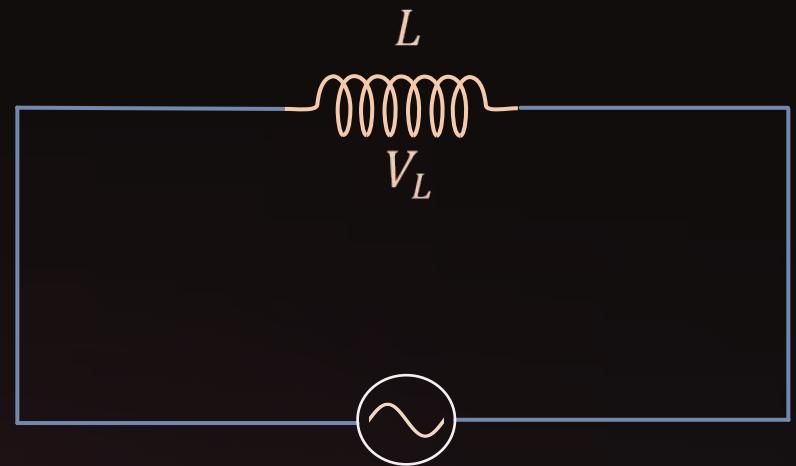

$$\varepsilon = \varepsilon_0 \sin \omega t$$

$$i = i_0 \sin \left(\omega t - \frac{\pi}{2} \right)$$



Circuit



X_L v/s frequency (f)

$$X_L = L\omega$$
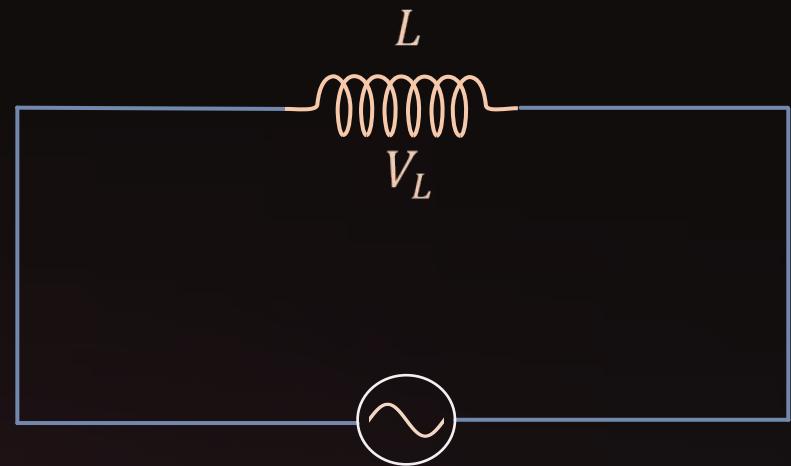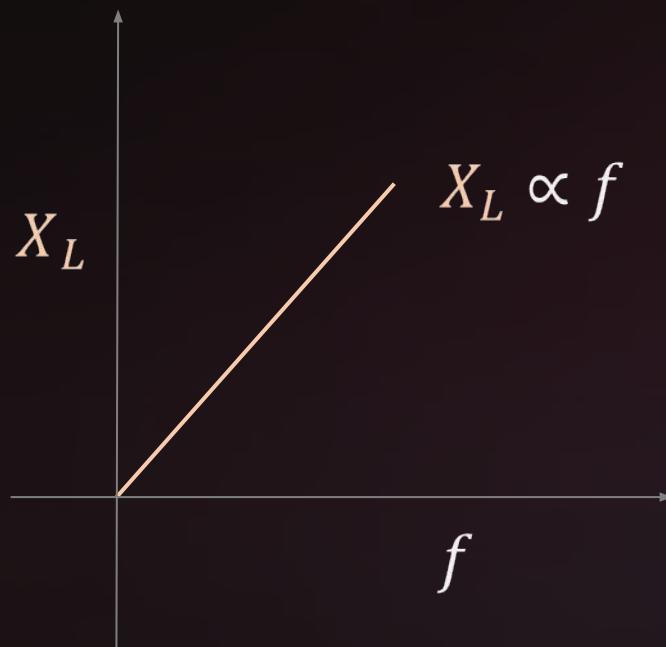
$$X_L = L \times 2\pi f \quad (\because \omega = 2\pi f)$$



$$\varepsilon = \varepsilon_0 \sin \omega t$$
$$i = i_0 \sin \left(\omega t - \frac{\pi}{2} \right)$$



Question



Find i_{avg} and i_{rms} of given circuit.



$$i_{avg} = 0$$



$$i_{avg} = \frac{1}{\pi} A$$



$$i_{avg} = 0$$



$$i_{avg} = \frac{2}{\pi} A$$


$$i_{rms} = 0$$

$$i_{rms} = \frac{0.5}{\sqrt{2}} A$$

$$i_{rms} = \frac{0.5}{\sqrt{2}} A$$

$$i_{rms} = 0$$

$$L = 2 H$$

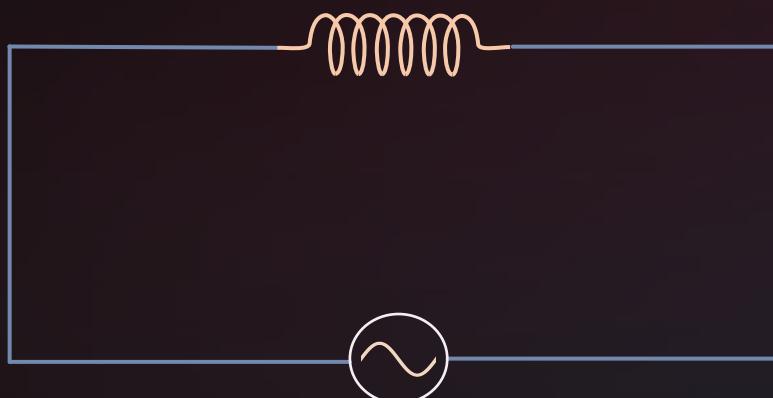

$$\varepsilon = 10 \sin(10t + 30^\circ)$$



Y




$$\varepsilon = \varepsilon_0 \sin(\omega t + \phi)$$

$$\varepsilon_0 = 10 \text{ V}$$

$$\omega = 10 \text{ s}^{-1}$$

$$i_0 = \frac{\varepsilon_0}{X_L}$$

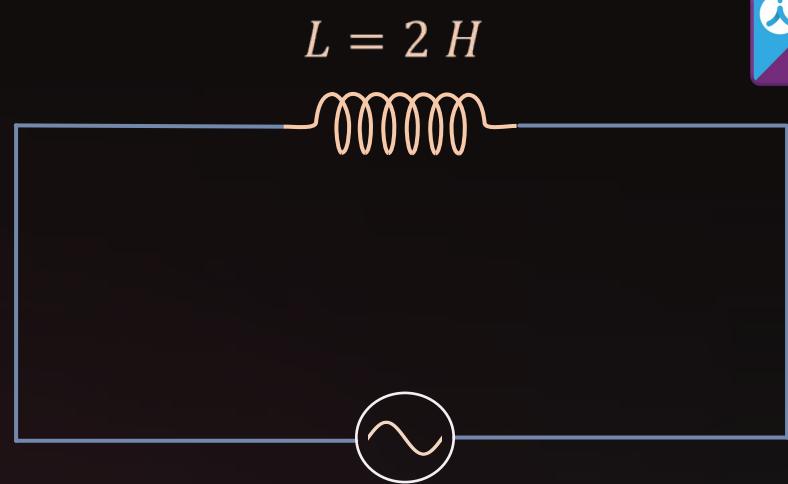

$$\varepsilon = 10 \sin(10t + 30^\circ)$$



Y



$$\varepsilon = \varepsilon_0 \sin(\omega t + \phi)$$

$$\varepsilon_0 = 10 \text{ V}$$

$$\omega = 10 \text{ s}^{-1}$$


$$i_0 = \frac{\varepsilon_0}{X_L}$$

$$i_0 = \frac{\varepsilon_0}{L\omega}$$

$$i_0 = \frac{10}{2 \times 10} = 0.5 \text{ A}$$

$$i_{avg} = 0 \quad (\text{For full cycle of AC } i_{av} = 0)$$
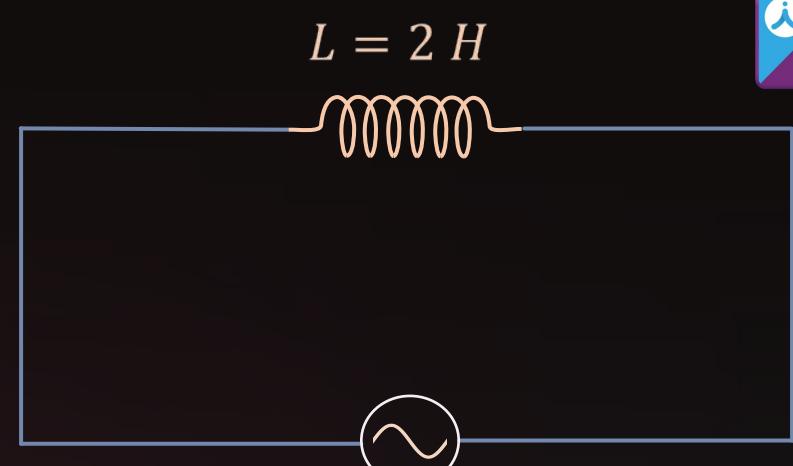
$$i_{rms} = \frac{i_0}{\sqrt{2}} = \frac{0.5}{\sqrt{2}} \text{ A}$$



$$\varepsilon = 10 \sin(10t + 30^\circ)$$



ANSWER



Find i_{avg} and i_{rms} of given circuit.

a

$$i_{avg} = 0$$

$$i_{rms} = 0$$

b

$$i_{avg} = \frac{1}{\pi} A$$

$$i_{rms} = \frac{0.5}{\sqrt{2}} A$$

c

$$i_{avg} = 0$$


$$i_{rms} = \frac{0.5}{\sqrt{2}} A$$

d

$$i_{avg} = \frac{2}{\pi} A$$

$$i_{rms} = 0$$

$$L = 2 H$$

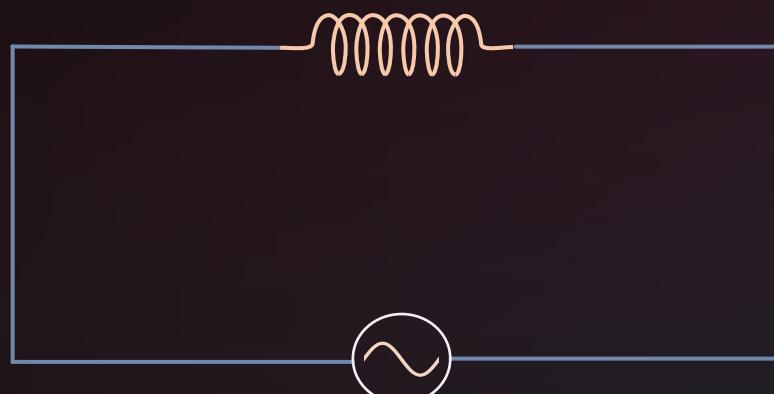


$$\varepsilon = 10 \sin(10t + 30^\circ)$$

PURE CAPACITIVE AC Circuit



Potential drop across
capacitance,
Apply KVL ;

$$V_C = \frac{q}{C}$$

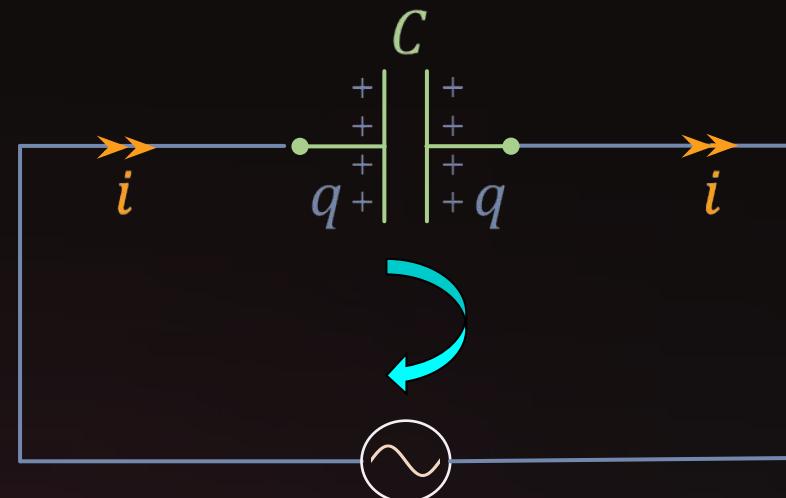

$$\varepsilon = \varepsilon_0 \sin \omega t$$

PURE CAPACITIVE AC Circuit




Potential drop across
capacitance,
Apply KVL ;

$$\varepsilon - V_C = 0$$

$$\frac{q}{C} = \varepsilon \Rightarrow q = C\varepsilon_0 \sin \omega t$$

$$i = \frac{dq}{dt} = \frac{d(C\varepsilon_0 \sin \omega t)}{dt}$$

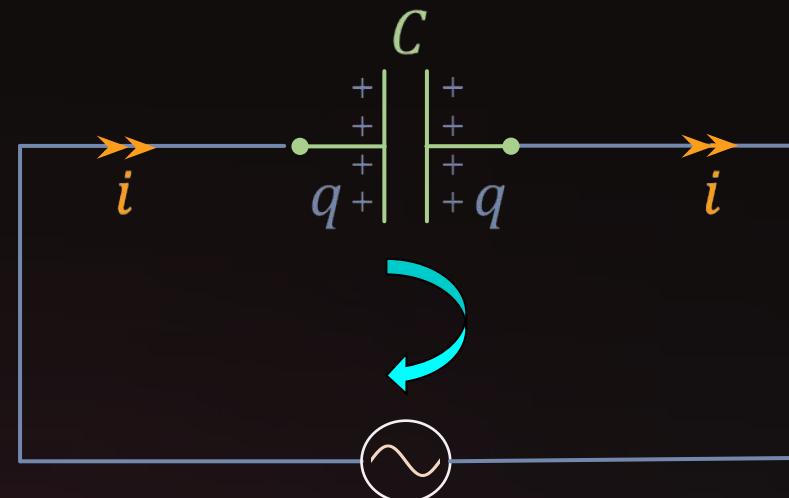
$$i = C\omega\varepsilon_0 \cos \omega t$$



PURE CAPACITIVE AC Circuit


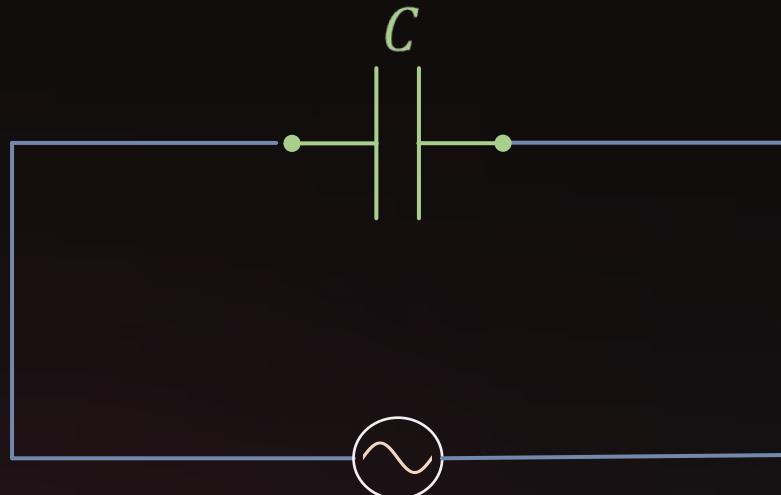
$$i = C\omega \varepsilon_0 \cos \omega t$$



$$\varepsilon = \varepsilon_0 \sin \omega t$$

PURE CAPACITIVE AC Circuit



$$i = C\omega \varepsilon_0 \cos \omega t$$

$$i = \left(\frac{\varepsilon_0}{\frac{1}{C\omega}} \right) \sin \left(\omega t + \frac{\pi}{2} \right)$$

ε_0 $\frac{1}{C\omega}$ i_0


$$i = i_0 \sin \left(\omega t + \frac{\pi}{2} \right)$$

$$i_0 = \frac{\varepsilon_0}{\frac{1}{C\omega}} = \frac{\varepsilon_0}{X_C}$$



$$X_C = \frac{1}{C\omega}$$

Capacitive reactance
SI Unit : Ohm Ω

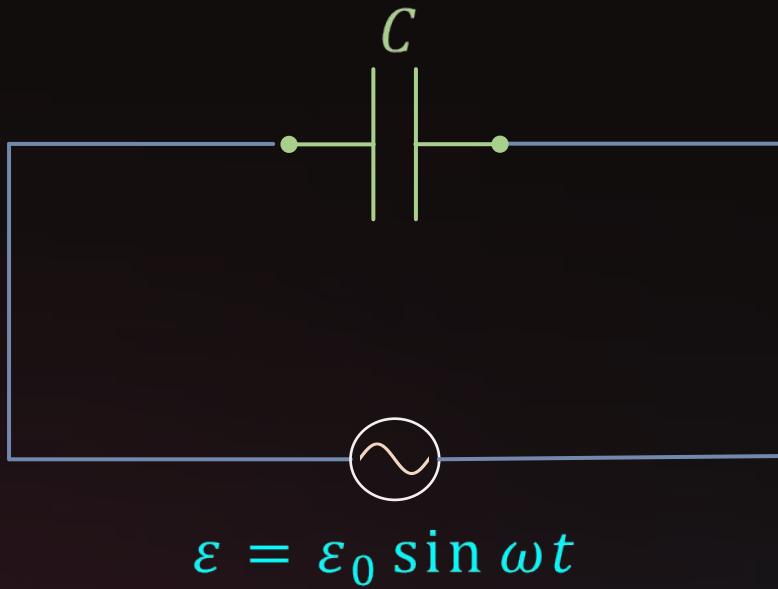


PURE CAPACITIVE AC Circuit




$$\text{Phase difference } (\phi) = \left(\omega t + \frac{\pi}{2} \right) - \omega t = \frac{\pi}{2}$$


Current **leads** potential by 90°

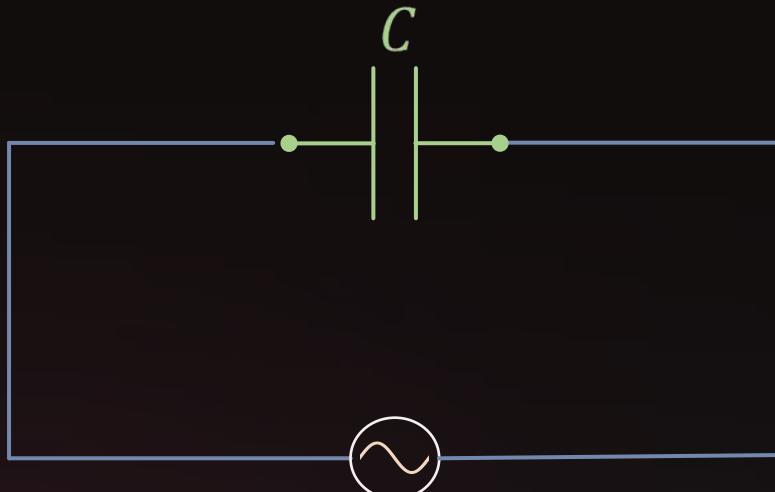

Phasor diagram

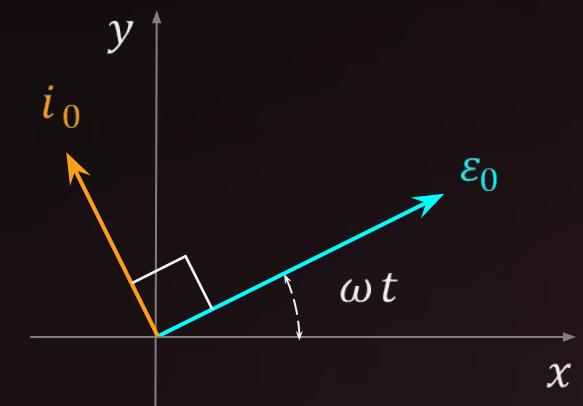

Wave diagram


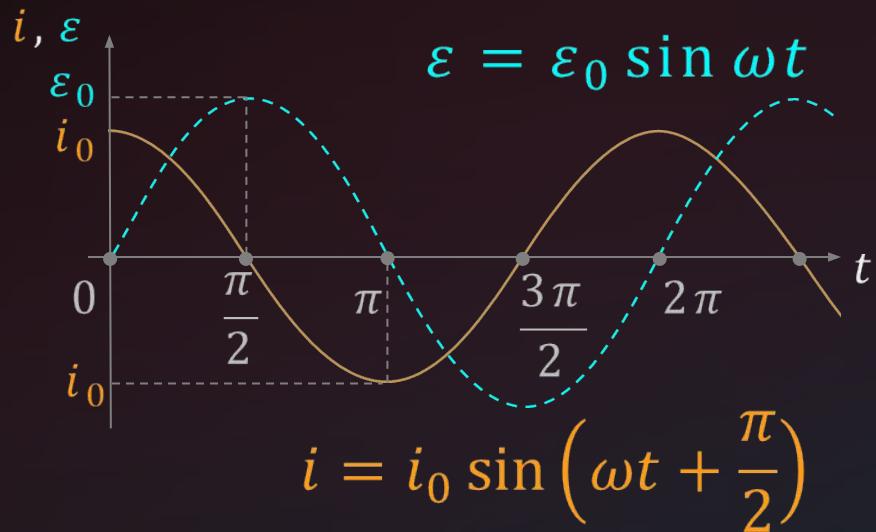


$$\varepsilon = \varepsilon_0 \sin \omega t$$
$$i = i_0 \sin \left(\omega t + \frac{\pi}{2} \right)$$

PURE CAPACITIVE AC Circuit



💡 X_C v/s frequency (f)

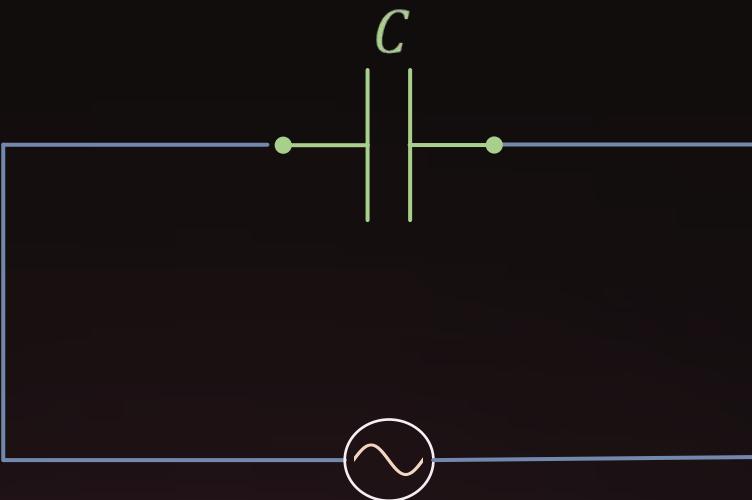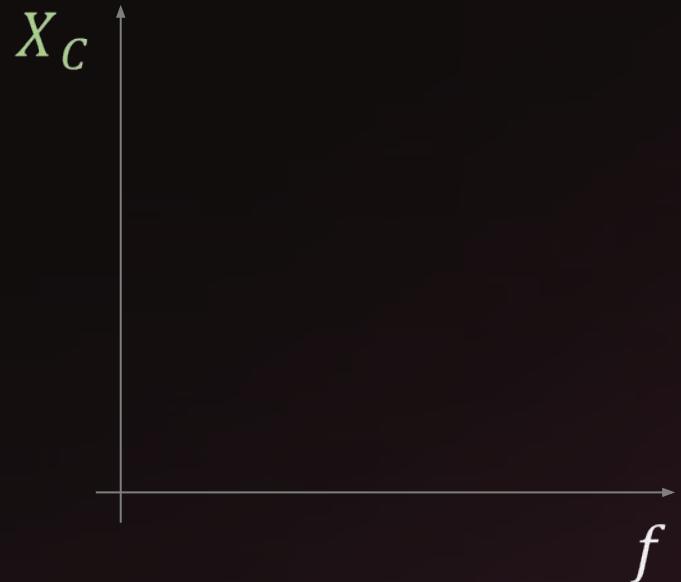

$$\varepsilon = \varepsilon_0 \sin \omega t$$
$$i = i_0 \sin \left(\omega t + \frac{\pi}{2} \right)$$


PURE CAPACITIVE AC Circuit




X_C v/s frequency (f)

$$X_C = \frac{1}{C\omega} \quad (\because \omega = 2\pi f)$$

$$X_C = \frac{1}{C \times 2\pi f}$$

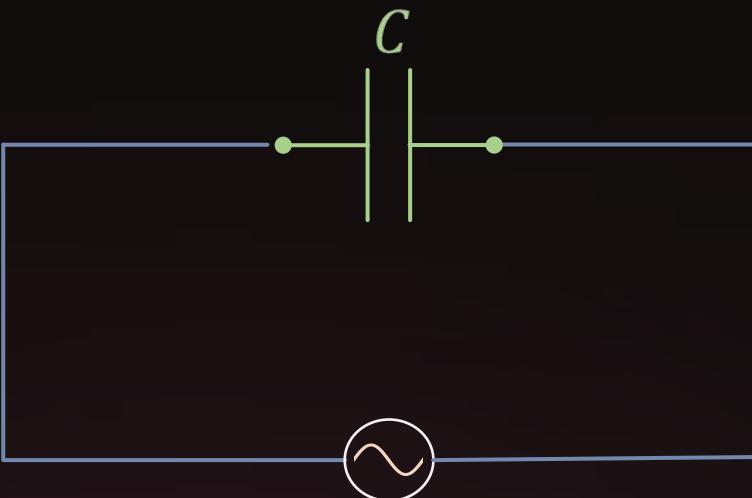
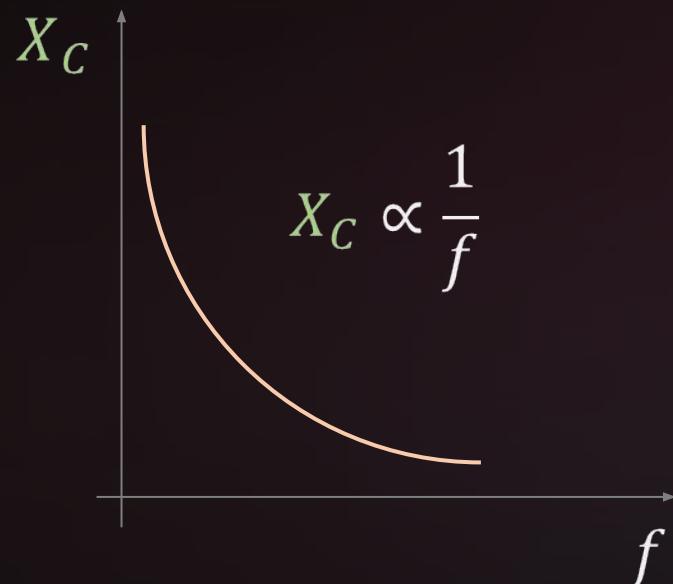
$$\begin{aligned} \varepsilon &= \varepsilon_0 \sin \omega t \\ i &= i_0 \sin \left(\omega t + \frac{\pi}{2} \right) \end{aligned}$$



CIRCUITS



Element	Current (emf: $\varepsilon = \varepsilon_0 \sin \omega t$)	ϕ	X (Reactance)
Resistor	$\frac{\varepsilon_0}{R} \sin \omega t$	0	R
Inductor	$\frac{\varepsilon_0}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$	$-\frac{\pi}{2}$	ωL
Capacitor	$\frac{\varepsilon_0}{1/\omega C} \sin \left(\omega t + \frac{\pi}{2} \right)$	$\frac{\pi}{2}$	$\frac{1}{\omega C}$



Question



Current in a pure capacitive circuit of $C = 5 \mu F$ is $5 \sin(50t + 30^\circ)$. Find the equation for emf.

a

$$2 \times 10^6 \sin(50t)$$

b

$$2 \times 10^4 \sin(50t - 60^\circ)$$

c

$$2 \times 10^4 \sin(50t + 90^\circ)$$

d

$$2 \times 10^4 \sin(50t)$$




Y

$$i = i_0 \sin(\omega t + \phi)$$

$$i_0 = 5 \text{ A}$$

$$\omega = 50 \text{ s}^{-1}$$

$$C = 5 \mu\text{F}$$

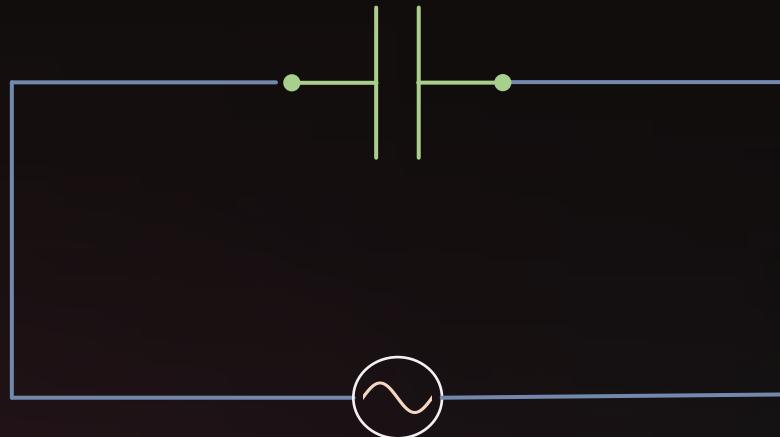

$$i = 5 \sin(50t + 30^\circ)$$



Y

$$i = i_0 \sin(\omega t + \phi)$$

$$i_0 = 5 \text{ A}$$

$$\omega = 50 \text{ s}^{-1}$$

$$\varepsilon_0 = i_0 X_C = i_0 \frac{1}{\omega C}$$

$$\varepsilon_0 = 5 \frac{1}{50 \times 5 \times 10^{-6}}$$

$$\varepsilon_0 = 2 \times 10^4 \text{ V}$$


Current leads potential by 90°

$$\varepsilon = \varepsilon_0 \sin(\omega t + \phi - 90^\circ)$$

$$\varepsilon = 2 \times 10^4 \sin(50t + 30 - 90^\circ)$$

$$\varepsilon = 2 \times 10^4 \sin(50t - 60^\circ)$$

$$C = 5 \mu\text{F}$$

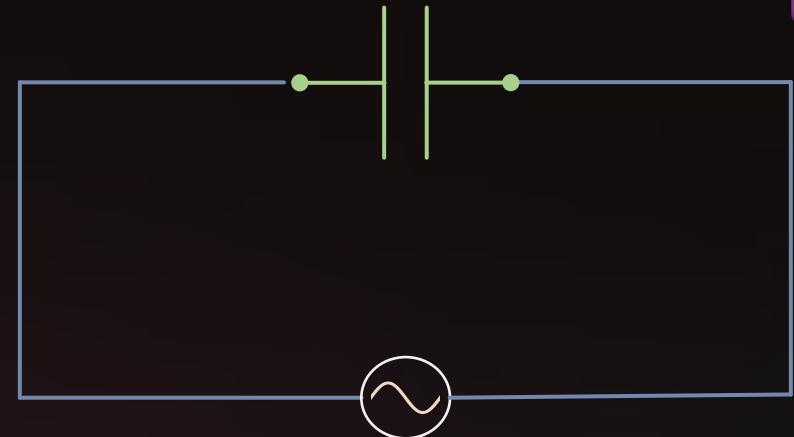

$$i = 5 \sin(50t + 30^\circ)$$





ANSWER



Current in a pure capacitive circuit of $C = 5 \mu F$ is $5 \sin(50t + 30^\circ)$. Find the equation for emf.

a

$$2 \times 10^6 \sin(50t)$$

b

$$2 \times 10^4 \sin(50t - 60^\circ)$$

c

$$2 \times 10^4 \sin(50t + 90^\circ)$$

d

$$2 \times 10^4 \sin(50t)$$