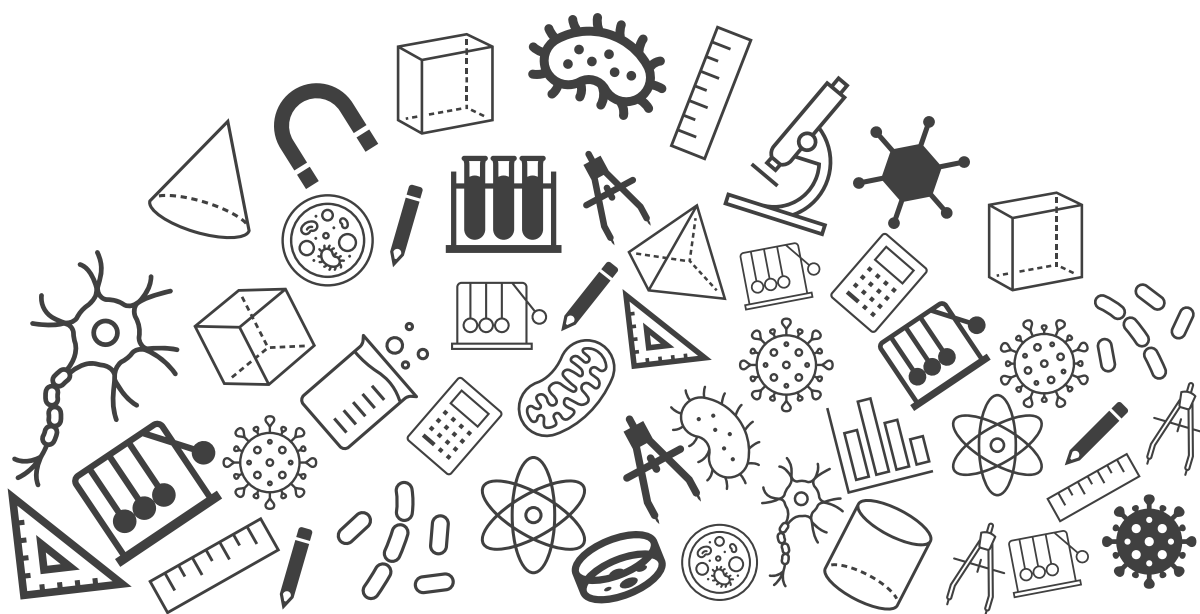





Grade 10: Science

Exam Important Questions





Electricity

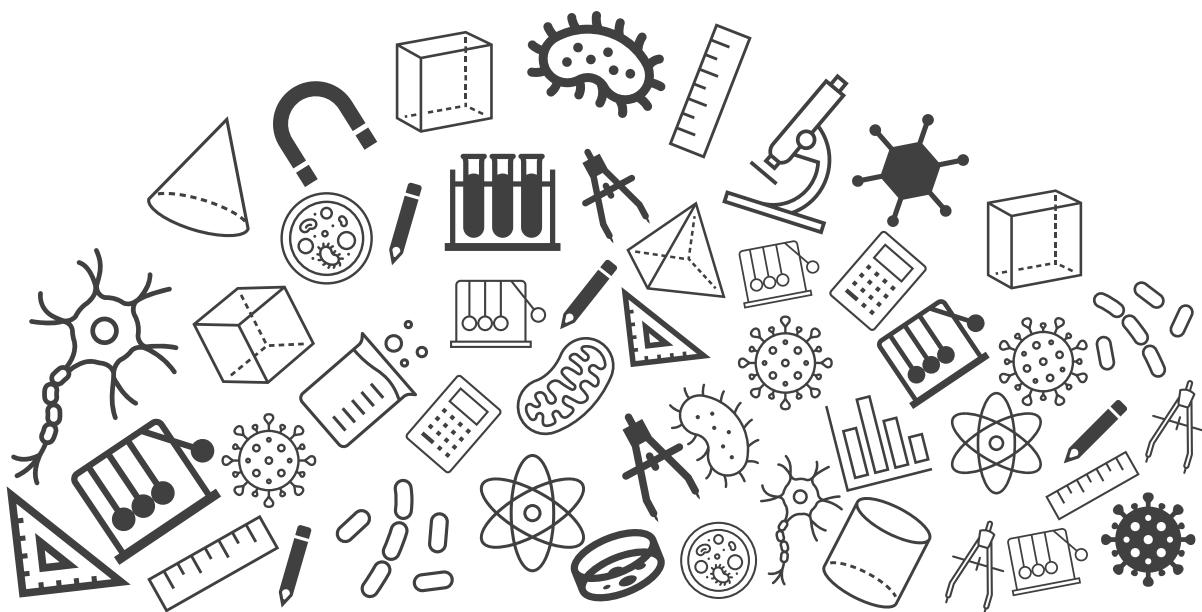


Electricity

1. Define one ohm. A resistance of 6 ohms is connected in series with another resistance of 4 ohms.
A potential difference of 20 volts is applied across the combination.
Calculate the current through the circuit and potential difference across the 6 ohm resistance.

[4 Marks]

Solution:

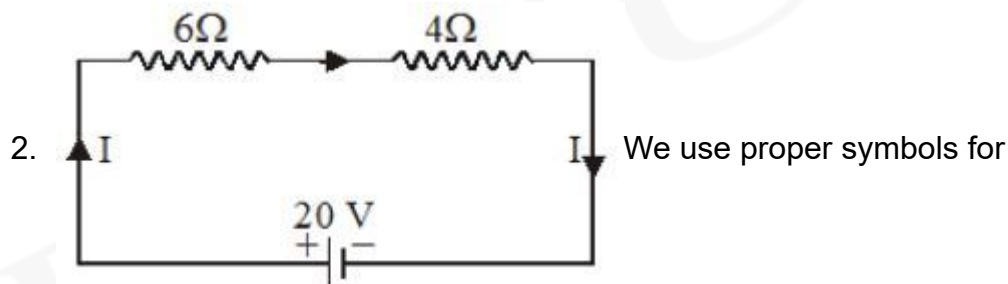1. 1 ohm is the resistance of a conductor, for which a current of 1 A flows through it on application of 1 V of potential difference across it. [1 Mark]



electrical components.

Potential difference, $V = 20\text{ V}$

Total circuit resistance:

$$R = R_1 + R_2$$

$$R = 10\ \Omega \quad [1\text{ Mark}]$$

From Ohm's law,

$$I = \frac{V}{R}$$

$$I = \frac{20\text{ V}}{10\ \Omega} = 2\text{ A} \quad [1\text{ Mark}]$$

This current will flow through each of the resistors.

Potential difference across $6\ \Omega$ resistance can be found by applying ohm's law for it.

$$V_1 = IR_1$$

$$V_1 = 2 \times 6 = 12\text{ V} \quad [1\text{ MARK}]$$

Electricity

2. In a premise, 5 bulbs each of 100 W, 2 fans each of 60 W, 2 A.Cs each of 1.5 kW are used for 5 h per day. Find:
- total power consumed per day,
 - total power consumed in 30 days.
 - total electric energy consumed in 30 days.
 - the cost of electricity at the rate of Rs 6.25 per unit.

[5 Marks]

[Electric Power]

Solution:

Power consumed by

$$5 \text{ bulbs} = 5 \times 100 = 500 \text{ W}$$

$$2 \text{ fans} = 2 \times 60 = 120 \text{ W}$$

$$2 \text{ A.C} = 2 \times 1.5 \times 1000 = 3000 \text{ W}$$

$$(a) \text{ Total power consumed per day} = 3620 \text{ W [1 Mark]}$$

$$(b) \text{ Total power consumed in 30 days, } P = 30 \times \frac{3620}{1000} = 108.6 \text{ kw [1 Mark]}$$

(c) Electric energy is used for 5 h per day.

$$\text{Total electrical energy consumed in 30 days} = P \times t = 108.6 \times 5 = 543 \text{ kWh [1 Mark]}$$

$$(d) \text{ Cost of electricity} = \text{Total electrical energy consumed (in kWh)} \times \text{Cost of 1 unit (1 kWh)} = 543 \times 6.25 = \text{Rs. 3393.75 [2 Mark]}$$

Electricity

3. Two lamps, one rated 100 W at 220 V, and the other 60 W at 220 V, are connected in parallel to an electric mains supply. What current is drawn from the line if the supply voltage is 220 V?

[3 Marks]

[NCERT Exercise]

[Electric Power & Combination of resistors]

Solution:

Both the bulbs are connected in parallel.

Therefore, the potential difference across each of them will be 220 V, because no division of voltage occurs in a parallel circuit.

Current drawn by the bulb of rating 100 W is given by,

$$Power = Voltage \times Current$$

$$Current = \frac{Power}{Voltage} = \frac{100}{220} A \text{ [1 Mark]}$$

Current drawn by the bulb of rating 60 W is given by,

$$Power = Voltage \times Current$$

$$Current = \frac{Power}{Voltage} = \frac{60}{220} A \text{ [1 Mark]}$$

$$\text{Hence, current drawn from the line} = \frac{100}{220} + \frac{60}{220} = 0.727 A \text{ [1 Mark]}$$

4. When a 12 V battery is connected across an unknown resistor, there is a current of 2.5 mA in the circuit. Find the value of the resistance of the resistor.

[2 marks]

[NCERT Exercise]

[Ohm's law]

Solution:

Resistance (R) of a resistor is given by Ohm's law as,

$$V = IR$$

$$R = \frac{V}{I} \quad (1 \text{ Mark})$$

Where, potential difference, $V = 12 \text{ V}$

Current in the circuit, $I = 2.5 \text{ mA} = 2.5 \times 10^{-3} \text{ A}$

$$R = \frac{12}{2.5 \times 10^{-3}} = 4.8 \times 10^3 \Omega = 4.8 \text{ k}\Omega \quad (1 \text{ Mark})$$

Therefore, the resistance of the resistor is $4.8 \text{ k}\Omega$.

Electricity

5. A copper wire has diameter 2 mm and resistivity of $3.14 \times 10^{-7} \Omega m$. What will be the length of this wire to make its resistance 10Ω ?

[3 Marks]

Solution:

Given,

$$\text{Diameter, } d = 2 \text{ mm} = 0.002 \text{ m}$$

$$\text{Resistivity, } \rho = 3.14 \times 10^{-7} \Omega m$$

$$\text{Resistance, } R = 10 \Omega$$

[1 Mark]

We know that

$$R = \rho \frac{l}{A}$$

$$\therefore l = \frac{RA}{\rho}$$

Also,

Area of cross-section of the wire,

$$A = \pi \left(\frac{d}{2} \right)^2$$

$$\begin{aligned} \therefore l &= \frac{R\pi \left(\frac{d}{2} \right)^2}{\rho} \\ &= \frac{10 \times 3.14 \times \left(\frac{0.002}{2} \right)^2}{3.14 \times 10^{-7}} \\ &= \frac{10 \times 3.14 \times (0.001)^2}{3.14 \times 10^{-7}} \\ &= \frac{10 \times 3.14 \times (10)^{-6}}{3.14 \times 10^{-7}} \\ &= \frac{10 \times 3.14 \times 10}{3.14} = 100 \text{ m} \end{aligned}$$

\therefore length of the wire = 100 m

[2 Marks]

Electricity

6. A hot plate of an electric oven connected to a 220 V line has two resistance coils A and B, each of 24Ω resistances, which may be used separately, in series, or in parallel. What are the currents in the three cases?

[3 Marks]

[NCERT Exercise]

[Combination of resistors]

Solution:

Supply voltage, $V = 220\text{ V}$

Resistance of one coil, $R = 24\Omega$

(i) Coils are used separately

According to Ohm's law, $V = I_1 R_1$

Where, I_1 is the current flowing through the coil

$$I_1 = \frac{V}{R_1} = \frac{220}{24} = 9.166\text{ A}$$

Therefore, 9.16 A current will flow through the coil when used separately.

[1 mark]

(ii) Coils are connected in series

Total resistance, $R_2 = 24\Omega + 24\Omega = 48\Omega$

According to Ohm's law, $V = I_2 R_2$

Where, I_2 is the current flowing through the series circuit

$$I_2 = \frac{V}{R_2} = \frac{220}{48} = 4.58\text{ A}$$

Therefore, 4.58 A current will flow through the circuit when the coils are connected in series. [1 mark]

(iii) Coils are connected in parallel

Total resistance, $R_3 = \frac{1}{\frac{1}{24} + \frac{1}{24}} = \frac{24}{2} = 12\Omega$

According to Ohm's law, $V = I_3 R_3$

Where, I_3 is the current flowing through the circuit $I_3 = \frac{V}{R_3} = \frac{220}{12} = 18.33\text{ A}$

Therefore, 18.33 A current will flow through the circuit when coils are connected in parallel. [1 mark]

Electricity

7. An electric lamp of $100\ \Omega$, a toaster of resistance $50\ \Omega$, and a water filter of resistance $500\ \Omega$ are connected in parallel to a $220\ \text{V}$ source. What is the resistance of an electric iron connected to the same source that takes as much current as all three appliances, and what is the current through it?

[3 Marks]

[Previous Year question : 2016]

[Combination of Resistors]

Electricity

Solution:

Given information


Resistance of electric lamp (R_1) = $100\ \Omega$

Resistance of toaster (R_2) = $50\ \Omega$

Resistance of water filter (R_3) = $500\ \Omega$

Potential difference of the source (V) = 220 V

[1 Mark]

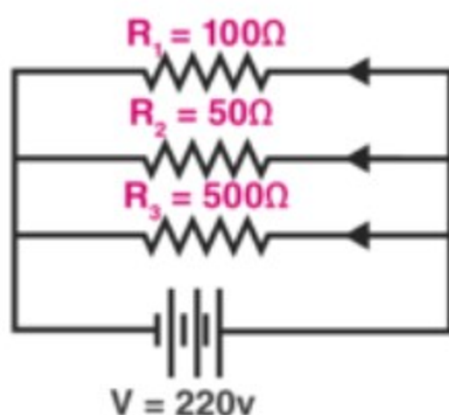

Total resistance (R) can be calculated as:

$$1/R = 1/R_1 + 1/R_2 + 1/R_3$$

$$= 1/100 + 1/50 + 1/100 = 16/500$$

$$R = 500/16\ \Omega = 31.25\ \Omega$$

[1 Mark]

According to the Ohm's law, $V = IR$

$$220 = I \times 31.25 \Rightarrow I = 220 / 31.25 = 7.04\text{ A}$$

[1 Mark]

Therefore, the resistance is $31.25\ \Omega$ and the current is 7.04 A .

Electricity

8. Show how would you join three resistors, each of resistance $9\ \Omega$ so that the equivalent resistance of the combination is (i) $13.5\ \Omega$ (ii) $6\ \Omega$.

[2marks]

[Previous Year Question : 2015]


[Combination of Resistors]

Electricity

Solution:

(i) To get an equivalent resistance of 13.5Ω and 6Ω , the resistances should be connected as shown in the figures:

For 13.5Ω :

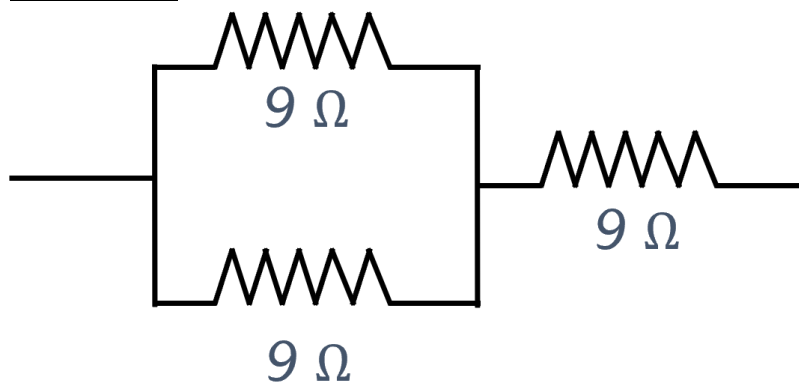


$$\text{So, } 1/R_P = 1/R_1 + 1/R_2$$

$$= 1/9 + 1/9$$

$$= 2/9 \Rightarrow R_P = 9/2 \Omega = 4.5 \Omega$$

$$R_P + R_3 = 9 \Omega + 4.5 \Omega = 13.5 \Omega \quad [1\text{mark}]$$

For 6Ω :

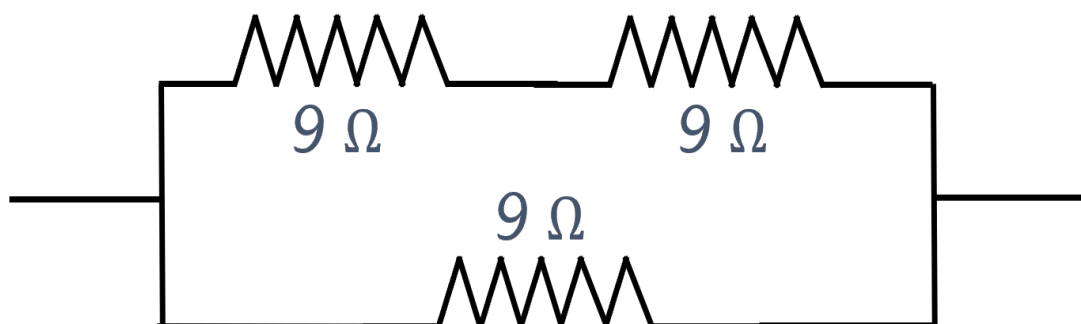

$$R_s = 9 + 9 = 18 \Omega$$

Now both the resistors are in parallel with each other so,

$$= 1/18 + 1/9$$

$$= 3/18$$

$$1/R = 1/6 \Omega$$

$$R = 6 \Omega$$

[1mark]

Electricity

9. Which uses more energy, a 250 W TV set in 1 h, or a 1200 W toaster in 10 minutes?

[2 marks]

[NCERT Exercise]

[Heating effect of electric current]

Solution:

Energy consumed by an electrical appliance is given by the expression, $H = Pt$

Where power of the appliance = P and time = t

Energy consumed by a TV set of power 250 W in 1 h =

$$250 \times 3600 = 9 \times 10^5 J$$

Energy consumed by a toaster of power 1200 W in 10 minutes = 1200×600

$$= 7.2 \times 10^5 J$$

Therefore, the energy consumed by a 250 W TV set in 1 h is more than the energy consumed by a toaster of power 1200 W in 10 minutes.

[2 marks]

10. Explain why is the tungsten used almost exclusively for filament of electric lamps?

[1 mark]

[NCERT Exercise]

[Resistivity]

Solution:

Tungsten is an alloy which has a very high melting point and very high resistivity so it does not burn or melt easily at a high temperature.

[1 mark]